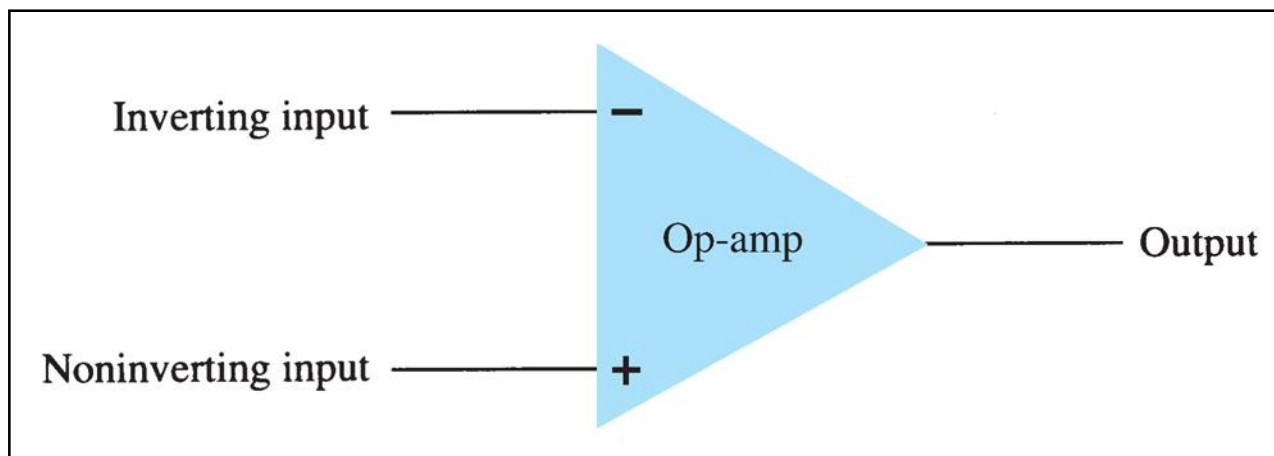


# Operational Amplifiers

Boylestad  
**Chapter 10**



# Operational Amplifier Basics




**Operational amplifier (Op-amp):** A high gain differential amplifier with a high input impedance (typically in  $M\Omega$ ) and low output impedance (less than  $100\Omega$ ).

Note the op-amp has two inputs and one output.



# Op-amp Operation Types

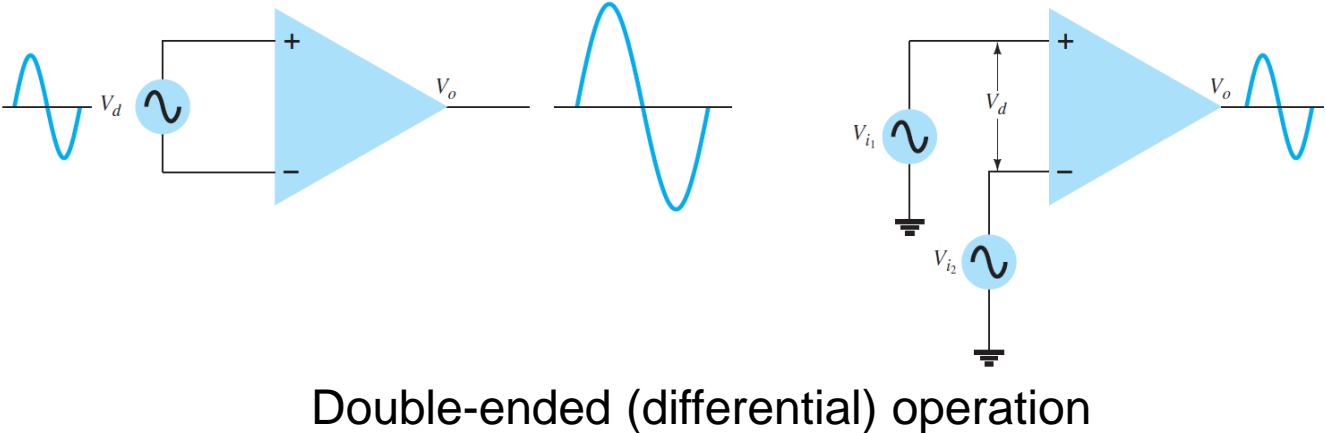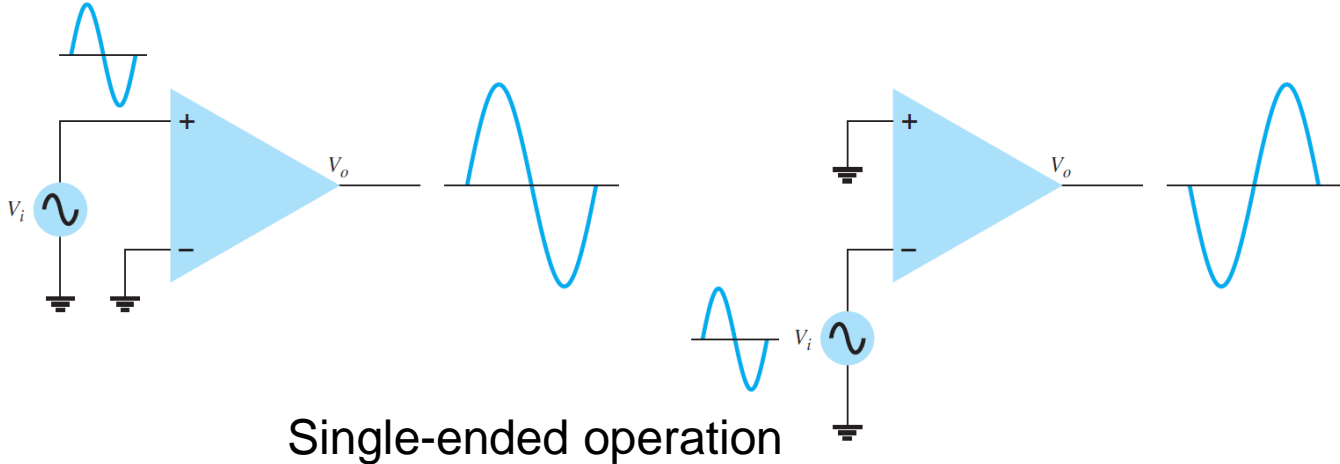


# Differential Amplifiers

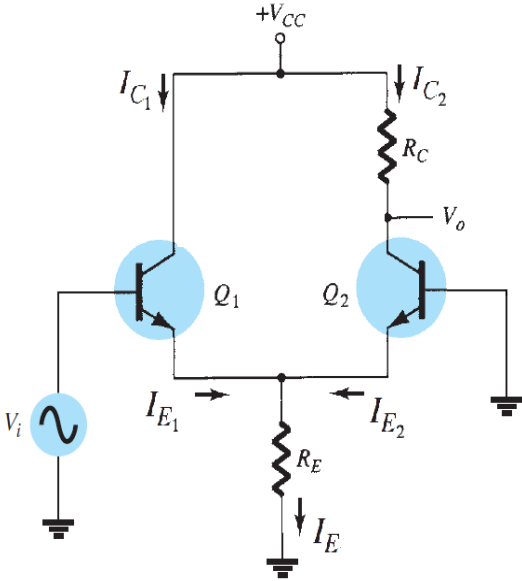

# Differential Amplifiers

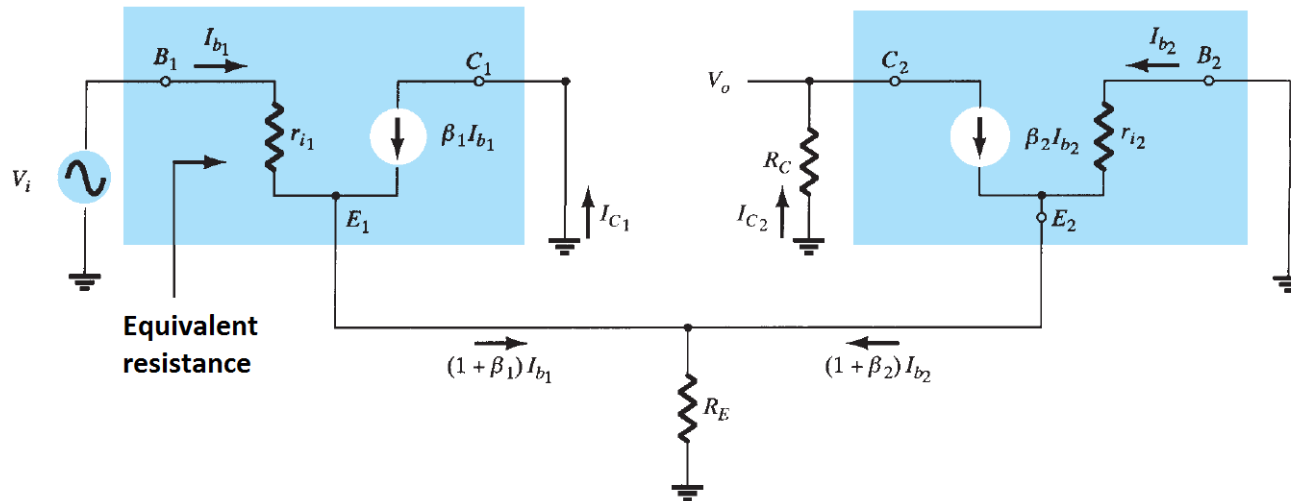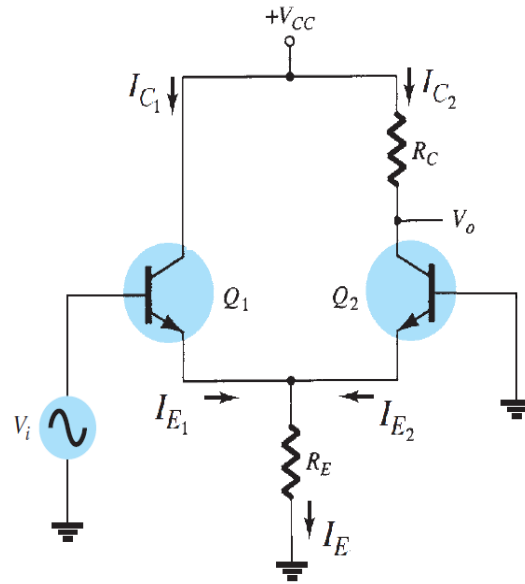

# Differential Amplifiers

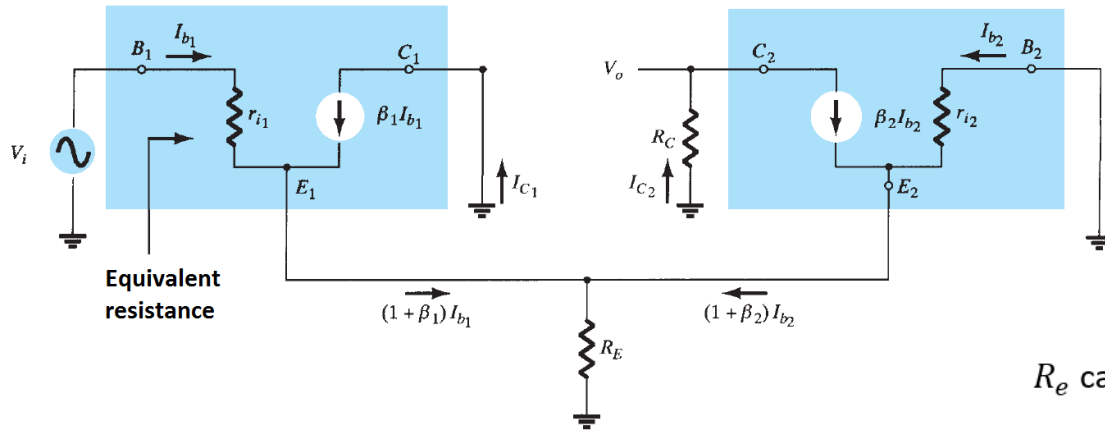

$R_e$  can be neglected if  $R_e \gg \beta r_e$

$$I_{b1} = I_{b2} = I_b \text{ (matched)}$$

$$\beta_1 = \beta_2 = \beta \text{ (matched)}$$


$$I_{c1} = I_{c2} = I_c \text{ (matched)}$$

$$V_i \approx I_b \beta r_e + I_b \beta r_e = 2I_b \beta r_e$$


$$V_o = -I_c R_C \text{ but } I_c = \beta I_b$$

$$V_o = -\beta I_b R_C$$


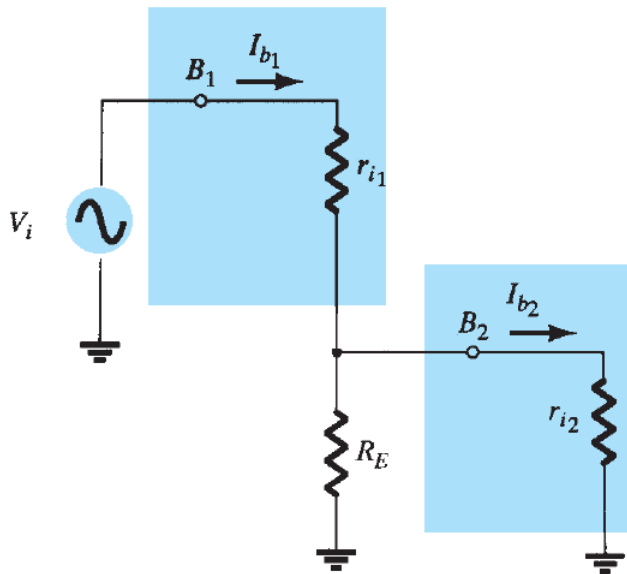
$$\text{Differential voltage gain } A_{vd} = -\frac{R_C}{2r_e}$$



# Differential Amplifiers

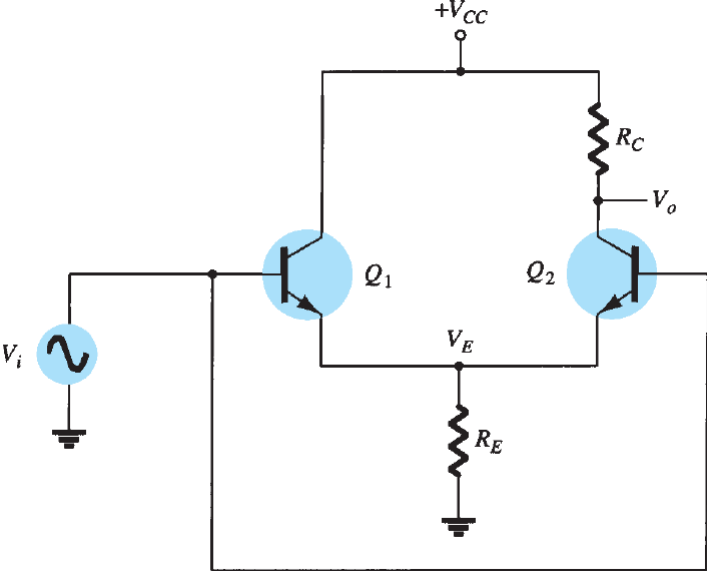


# Differential Amplifiers

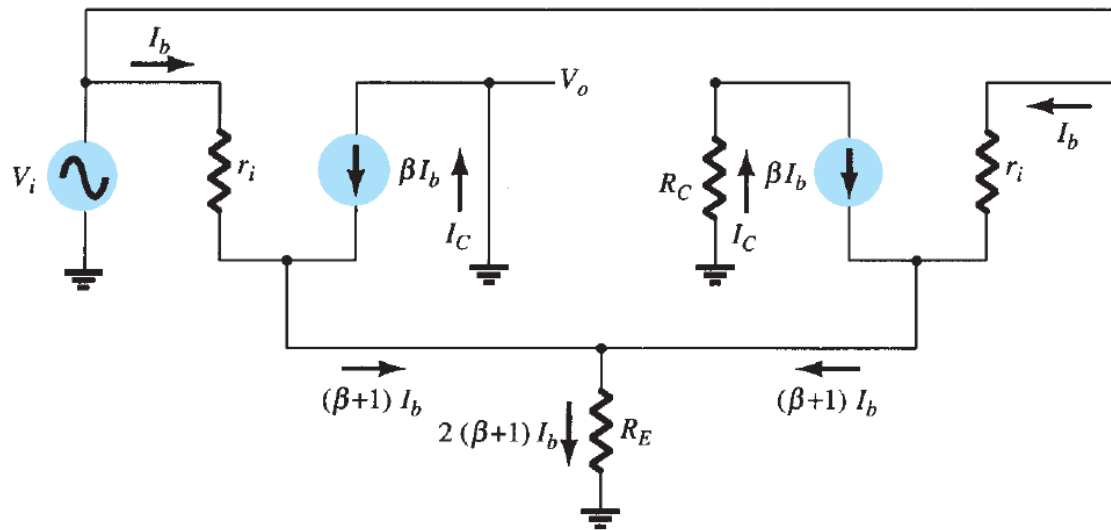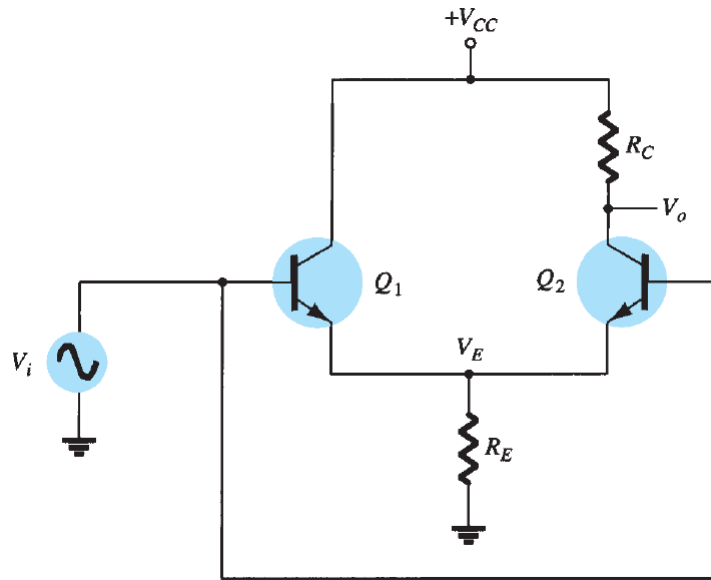



# Differential Amplifiers

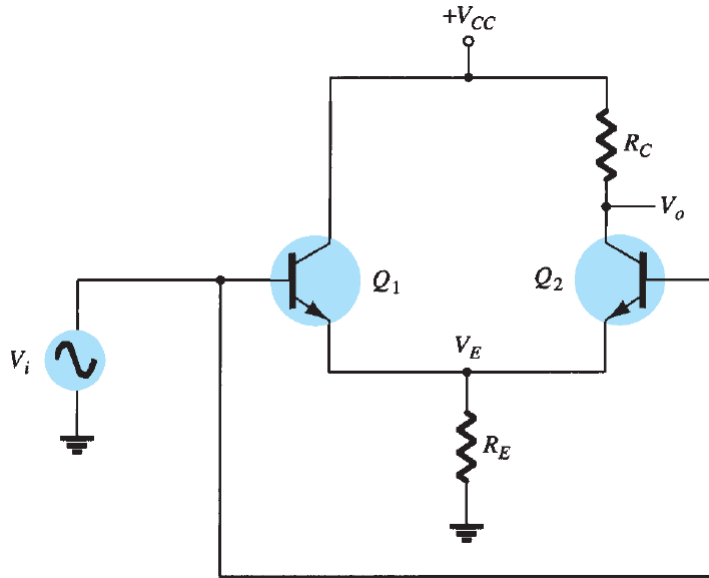


$$V_i \approx I_b \beta r_e + 2(\beta + 1)I_b R_E$$

$$V_i \approx I_b \beta (r_e + 2R_E)$$

$$V_o = -I_c R_c = -\beta I_b R_c$$

$$A_{v_c} = \frac{V_o}{V_i} = -\frac{\beta I_b R_c}{\beta I_b (r_e + 2R_E)}$$

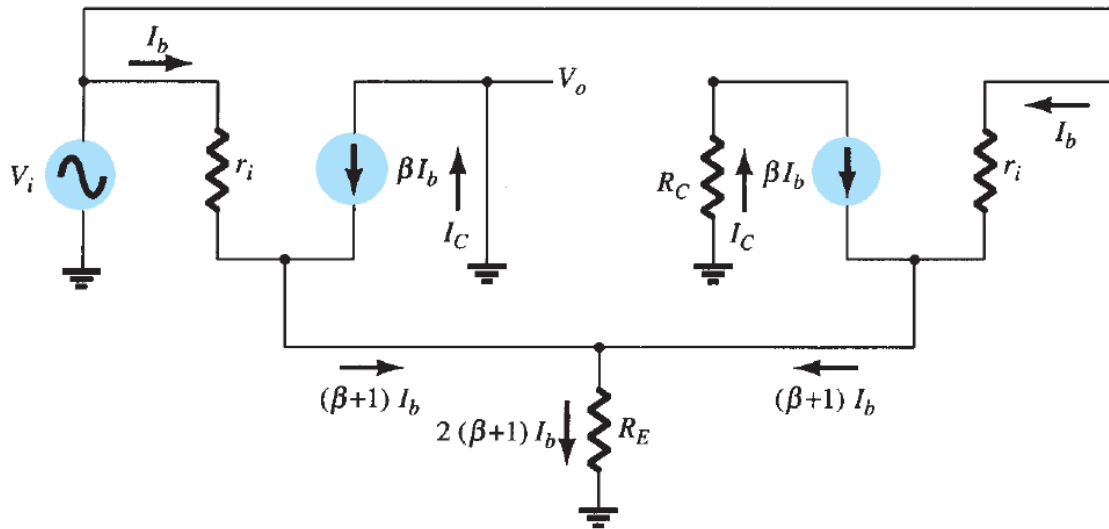
Common-mode voltage gain  $A_{v_c} = -\frac{R_c}{r_e + 2R_E}$



Remember  $A_{v_d} = -\frac{R_c}{2r_e}$

$$|A_{v_d}| \gg |A_{v_c}|$$

# Differential Amplifiers

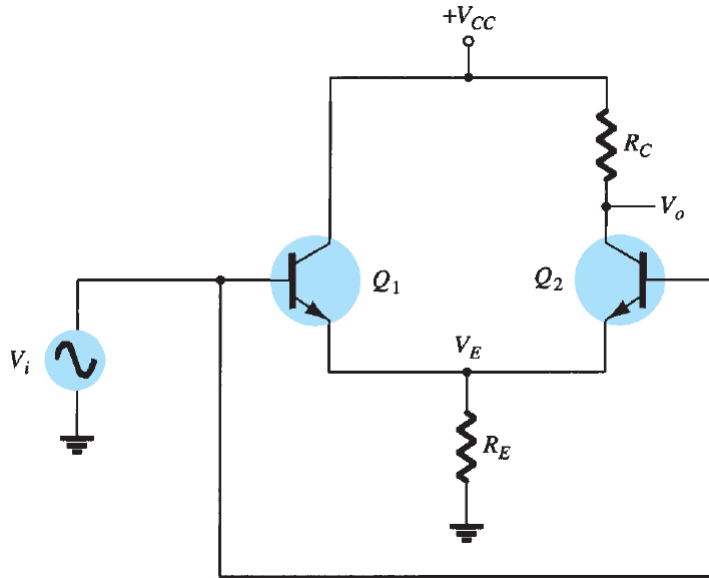


$$V_i \approx I_b \beta r_e + 2(\beta + 1)I_b R_E$$

$$V_i \approx I_b \beta (r_e + 2R_E)$$

$$V_o = -I_c R_C = -\beta I_b R_C$$

$$A_{v_c} = \frac{V_o}{V_i} = -\frac{\beta I_b R_C}{\beta I_b (r_e + 2R_E)}$$

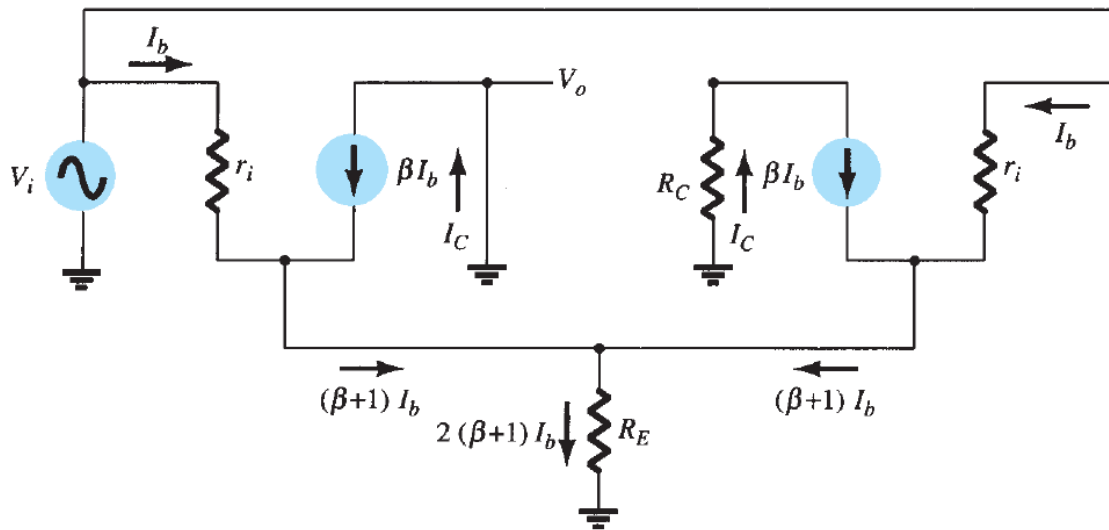Common-mode voltage gain  $A_{v_c} = -\frac{R_C}{r_e + 2R_E}$



Remember  $A_{v_d} = -\frac{R_C}{2r_e}$

$$|A_{v_d}| \gg |A_{v_c}|$$

The circuit amplifies the difference but suppresses the common signal


# Increasing $R_E$

To decrease the common-mode voltage gain:


$$A_{v_c} = -\frac{R_C}{r_e + 2R_E}$$

We should increase  $R_E$

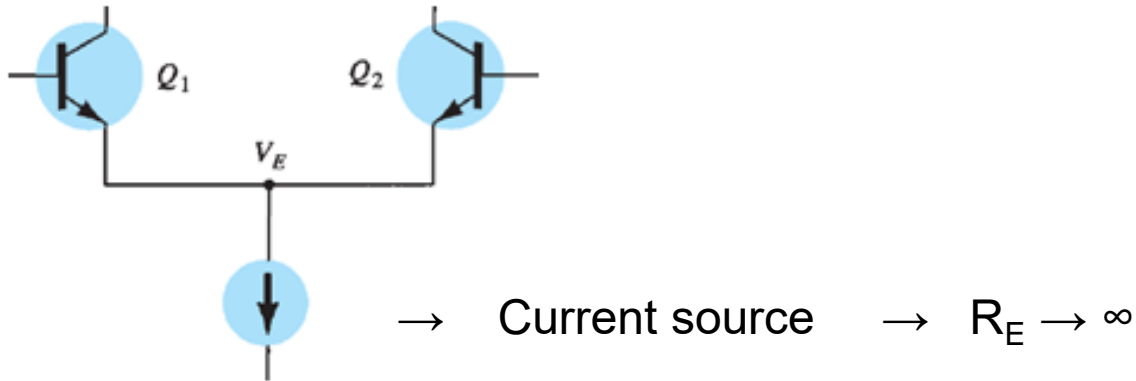To increase  $R_E$  we can add a current source instead of  $R_E$


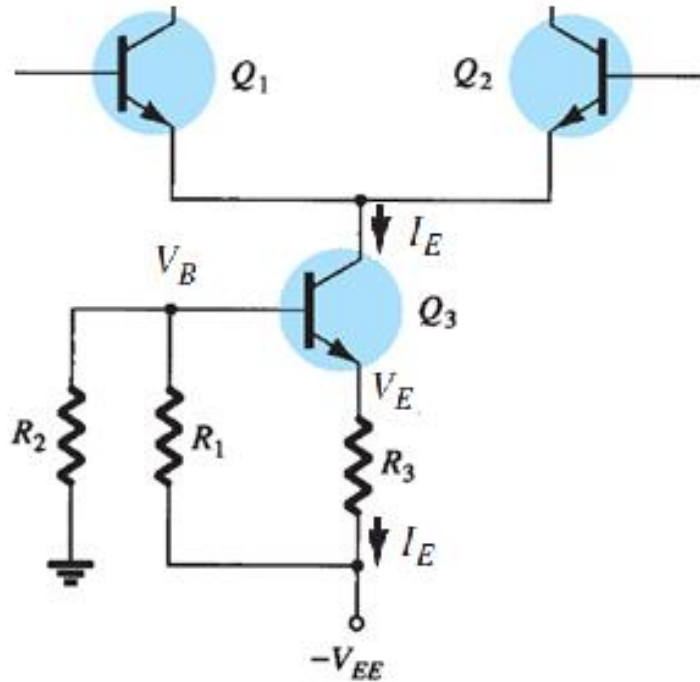
# Increasing $R_E$ – Constant Current Source




$$V_B = -\frac{R_2}{R_1 + R_2} V_{EE}$$

$$I_E = \frac{V_{EE} - V_E}{R_E} \quad V_E = V_B - 0.7$$

Constant  $I_E$

# Increasing $R_E$ – Current Mirror

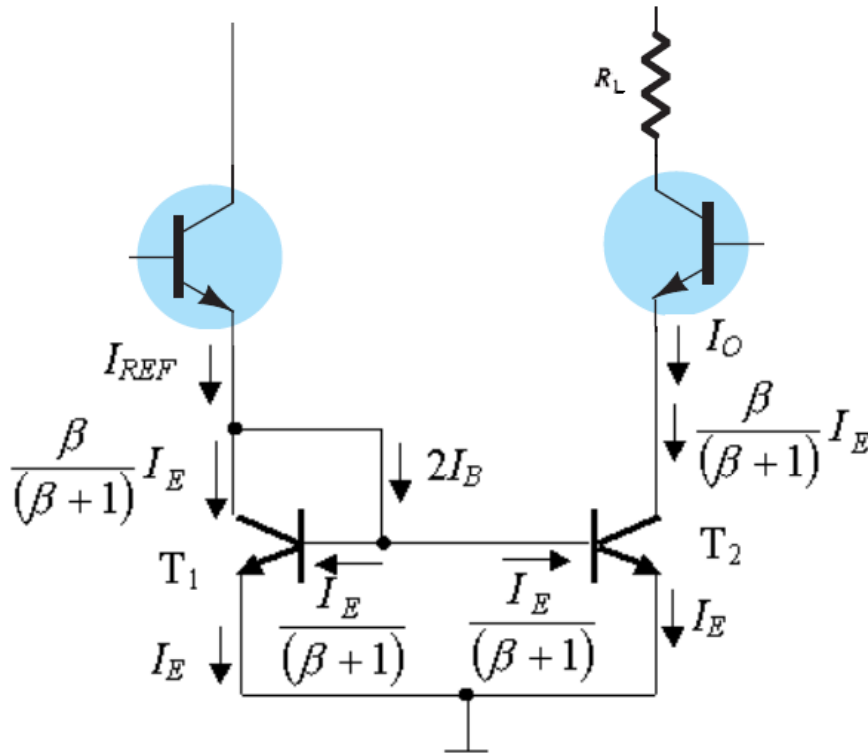


$T_1$  and  $T_2$  form  
a current mirror

$$I_{REF} = \frac{\beta}{\beta+1} I_E + 2 \frac{I_E}{\beta+1} = \frac{\beta+2}{\beta+1} I_E$$

$$I_O = \frac{\beta}{\beta+1} I_E$$

$$I_O = \frac{1}{1+2/\beta} I_{REF} \cong I_{REF}$$

# Using MOS Transistors

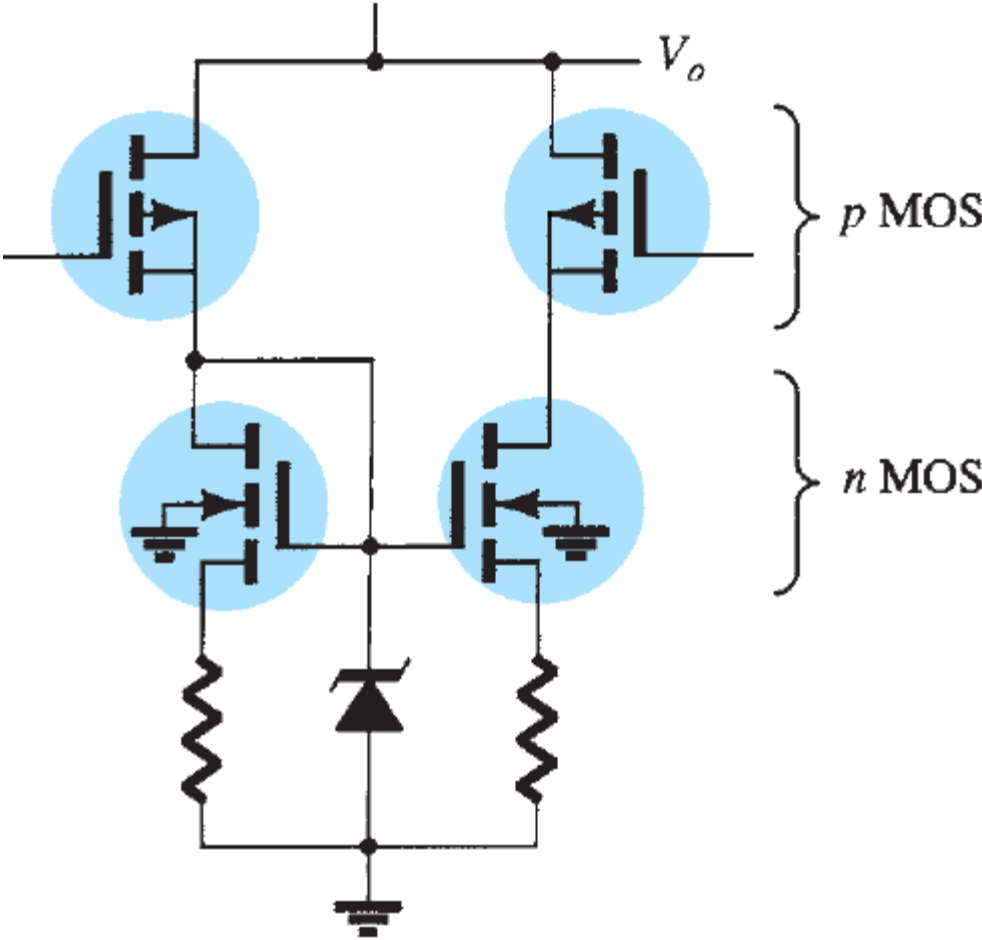

# Op-Amp Gain

Op-Amps can be connected in *open-loop* or *closed-loop* configurations.

**Open-loop:** A configuration with no feedback from the op-amp output back to its input. Op-amp open-loop gain typically exceeds 10,000.

**Closed-loop:** A configuration that has a negative feedback path from the op-amp output back to its input. **Negative feedback** reduces the gain and improves many characteristics of the op-amp.


- Closed-loop gain is always lower than open-loop gain.

# Inverting Op-Amp

The input signal is applied to the **inverting (-) input**

The **non-inverting input (+)** is grounded

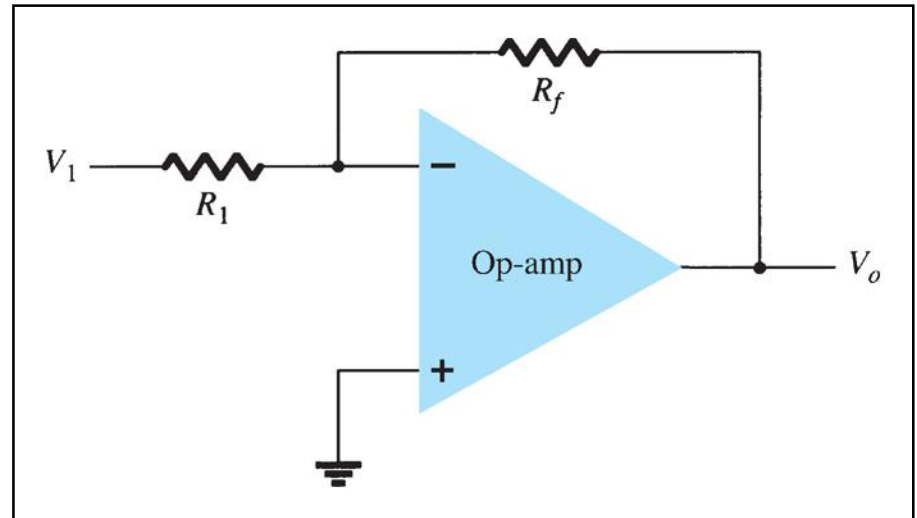The **feedback resistor** ( $R_f$ ) is connected from the output to the negative (inverting) input; providing *negative feedback*.





# Inverting Op-Amp Gain


Gain is set using external resistors:  $R_f$  and  $R_1$

$$A_v = \frac{V_o}{V_i} = -\frac{R_f}{R_1}$$

Gain can be set to any value by manipulating the values of  $R_f$  and  $R_1$ .

Unity gain ( $A_v = 1$ ):
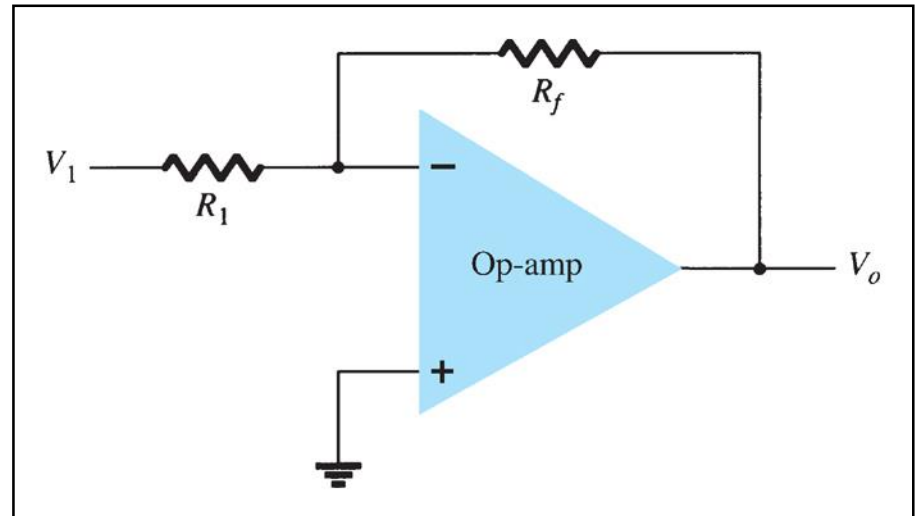
$$R_f = R_1$$
$$A_v = \frac{-R_f}{R_1} = -1$$





The negative sign denotes a  $180^\circ$  phase shift between input and output.
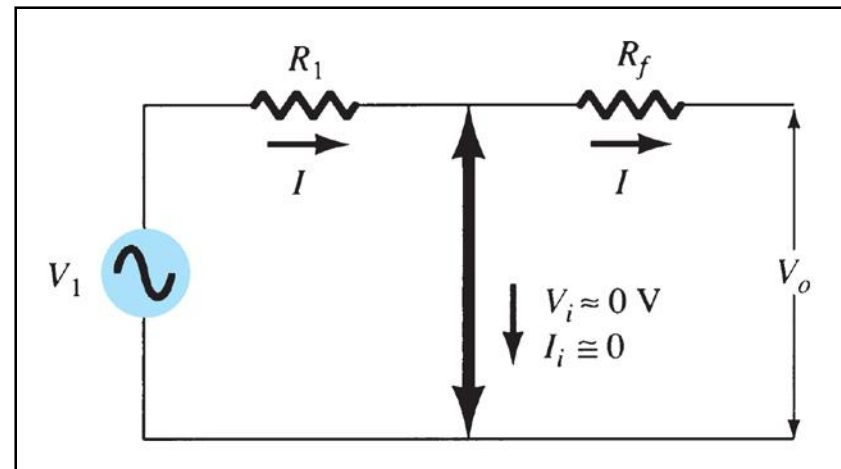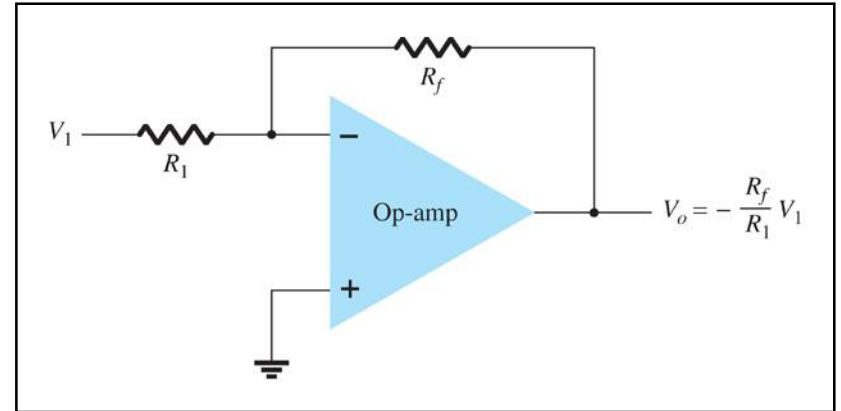
# Virtual Ground

**Virtual ground:** A term used to describe the condition where  $V_i \cong 0 \text{ V}$  (at the inverting input) when the noninverting input is grounded.

The op-amp has such high input impedance that even with a high gain there is no current through the inverting input pin, therefore all of the input current passes through  $R_f$ .



# Common Op-Amp Circuits

**Inverting amplifier**

**Noninverting amplifier**

**Unity follower**

**Summing amplifier**


**Integrator**

**Differentiator**

# Inverting/Noninverting Amplifiers


## Inverting Amplifier

$$V_o = -\frac{R_f}{R_1} V_1$$


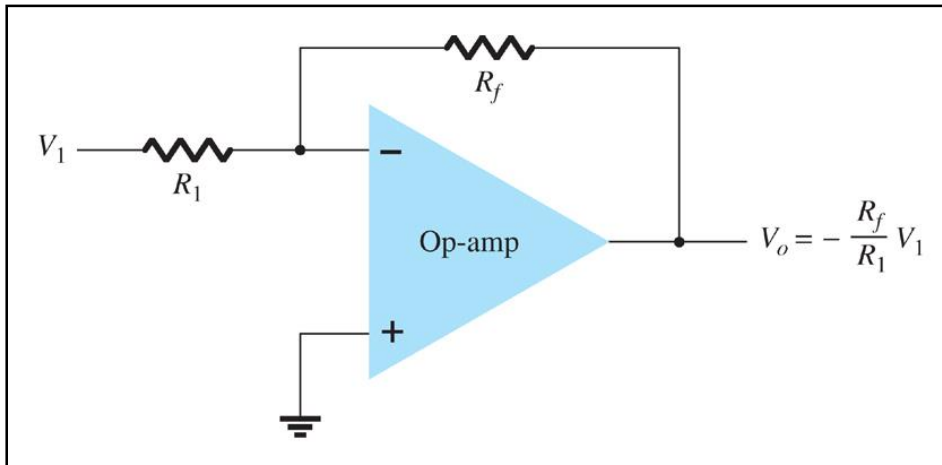


## Noninverting Amplifier

$$V_o = ?$$

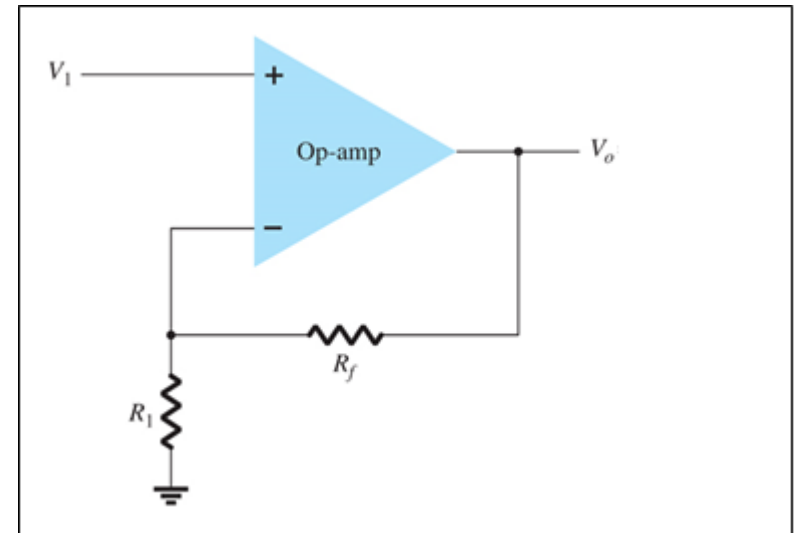

# Noninverting Amplifiers

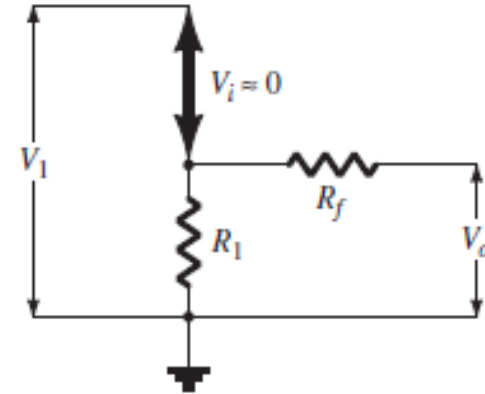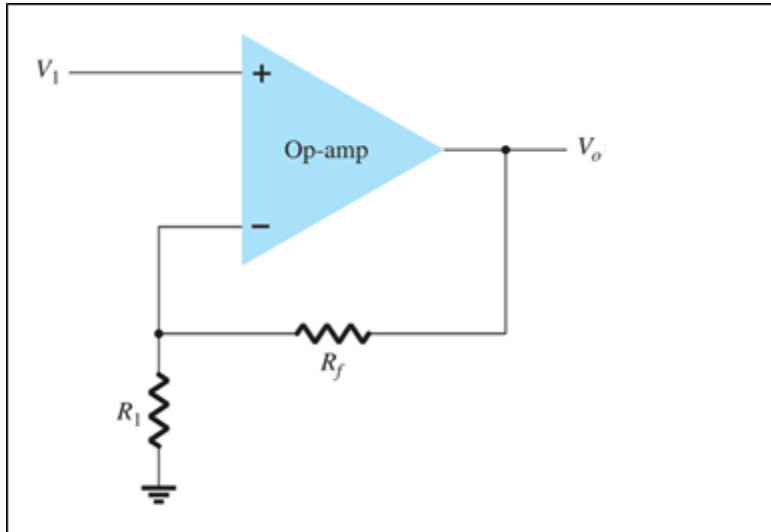


$$V_1 = \frac{R_1}{R_1 + R_f} V_o$$

$$\frac{V_o}{V_1} = \frac{R_1 + R_f}{R_1} = 1 + \frac{R_f}{R_1}$$

# Noninverting Amplifiers


## Inverting Amplifier

$$V_o = -\frac{R_f}{R_1} V_1$$

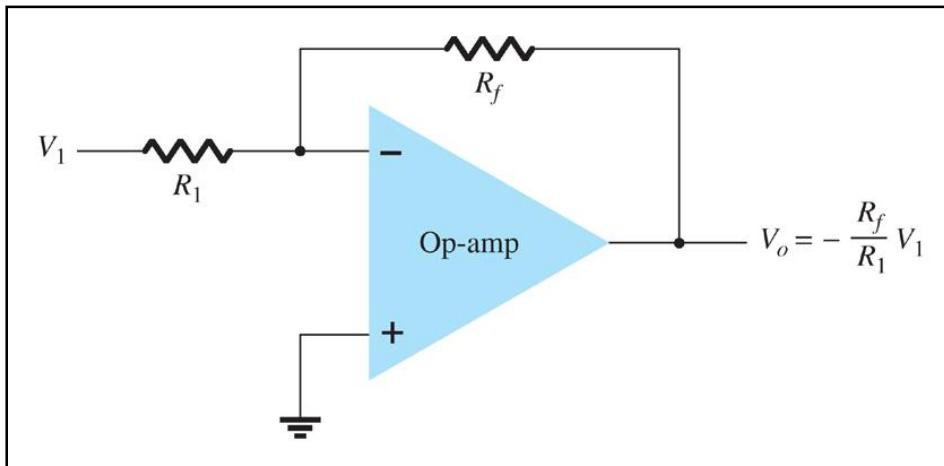

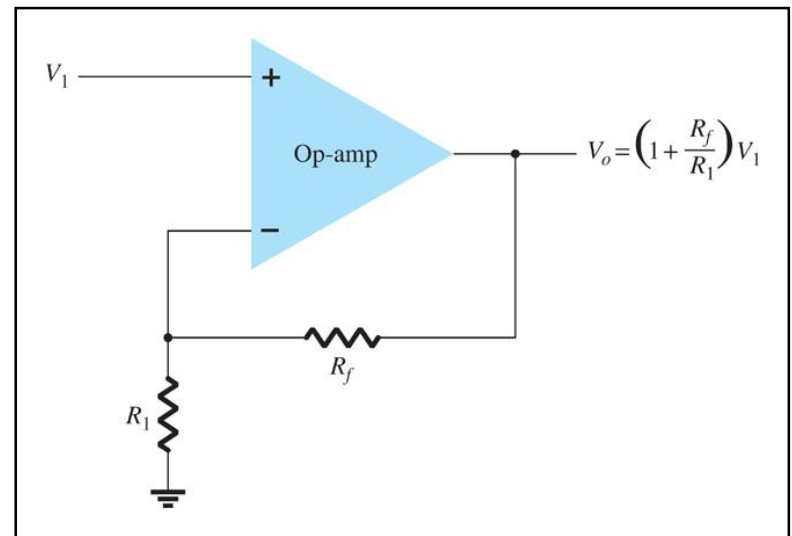
## Noninverting Amplifier



$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_1$$



# Unity Follower


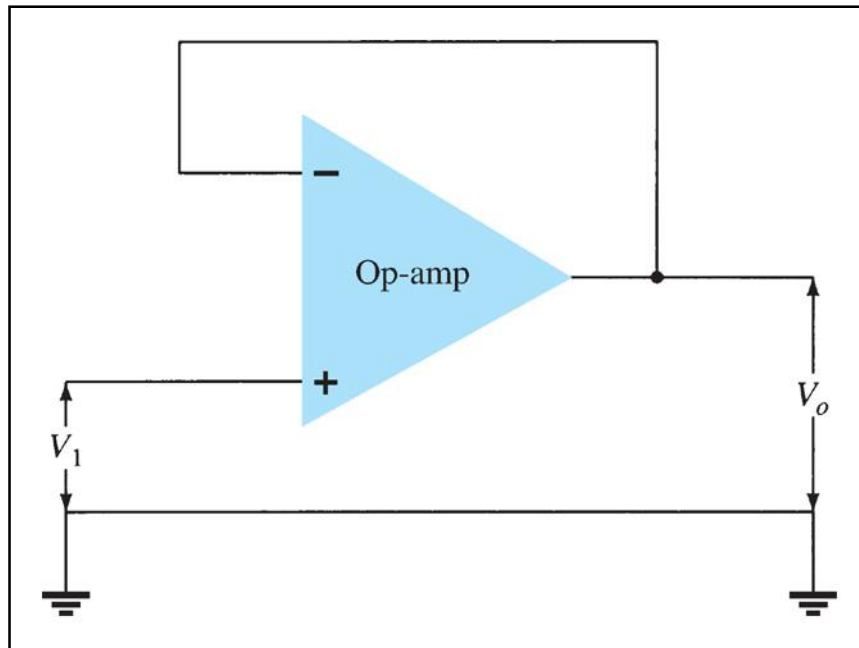


# Unity Follower

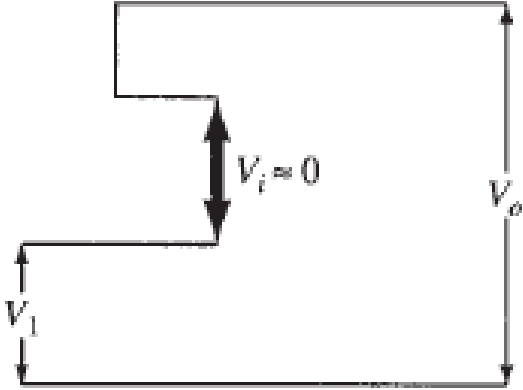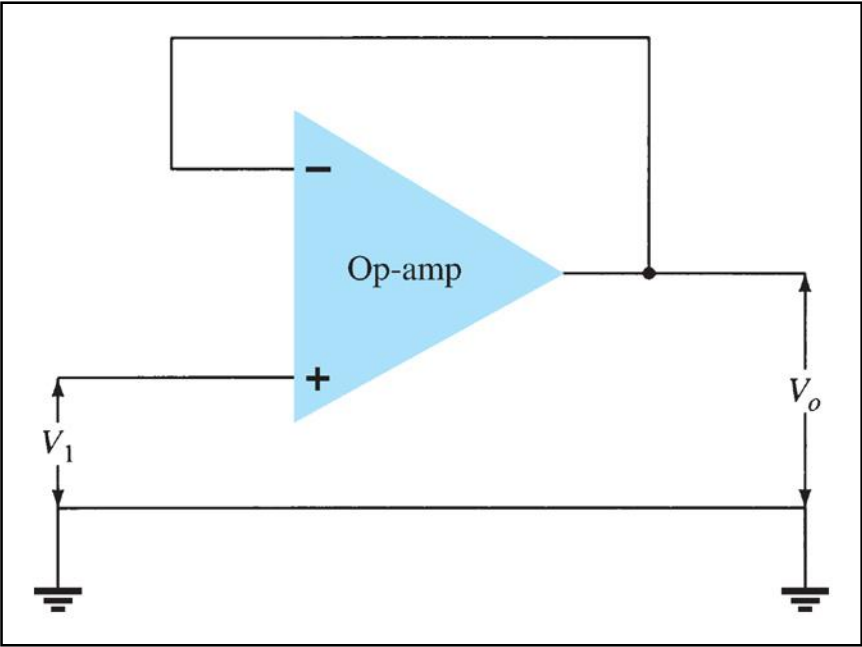





# Unity Follower



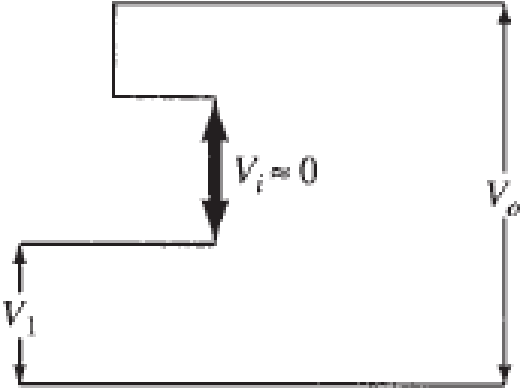
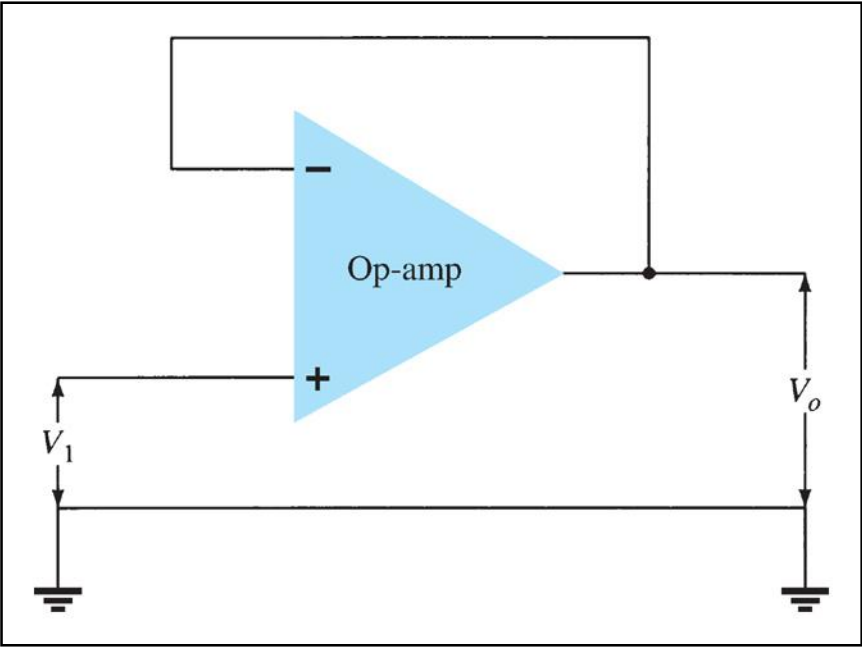


$$V_o = V_1$$


# Unity Follower

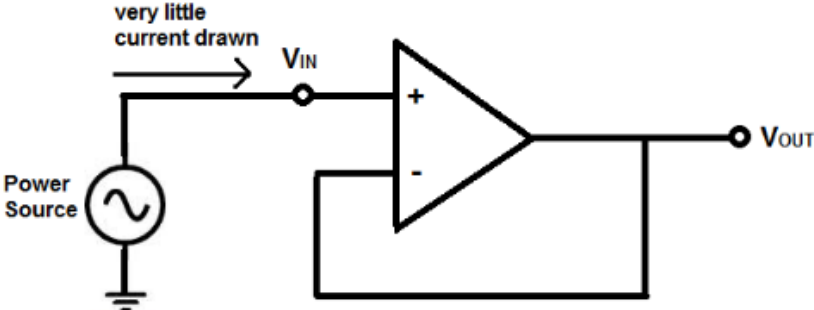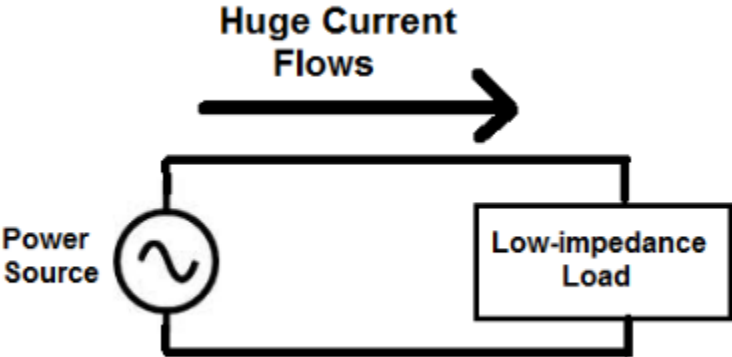



# Unity Follower

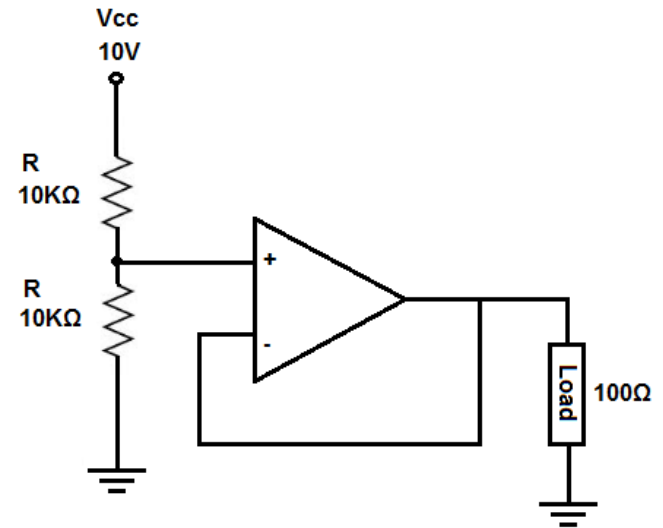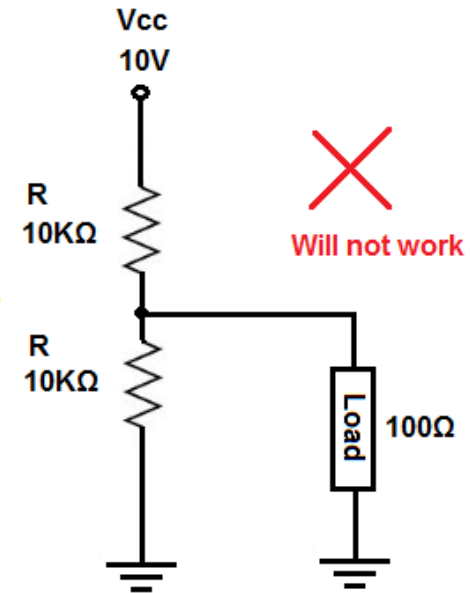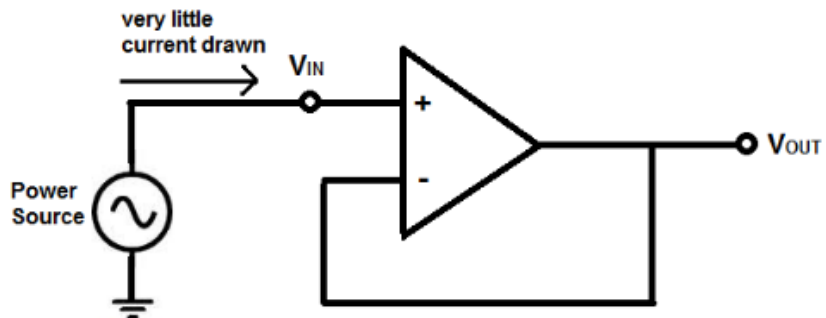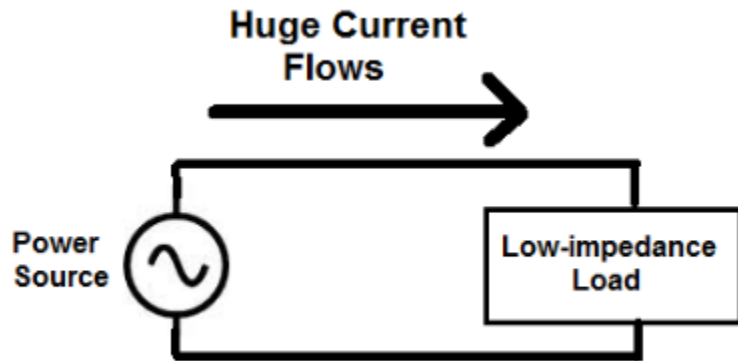



# Summing Amplifier

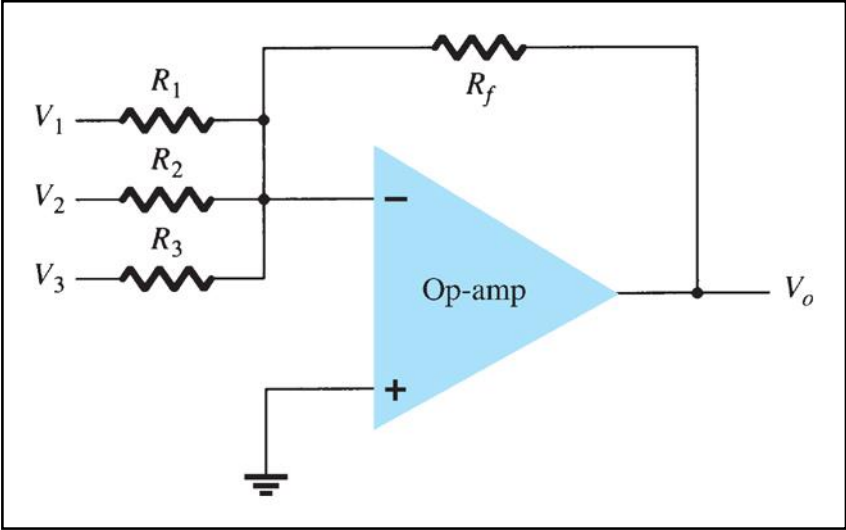

# Summing Amplifier

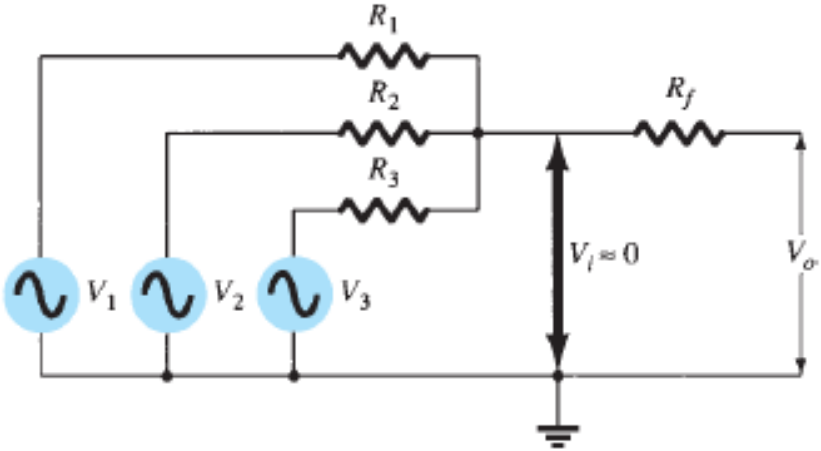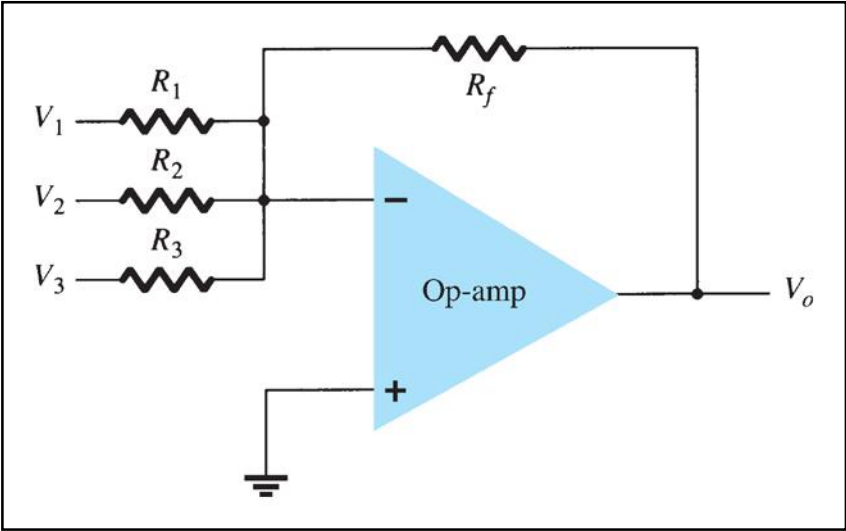



# Summing Amplifier

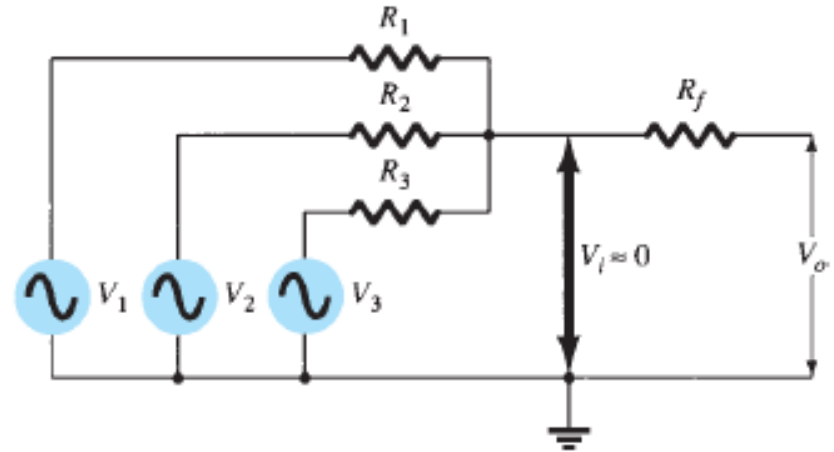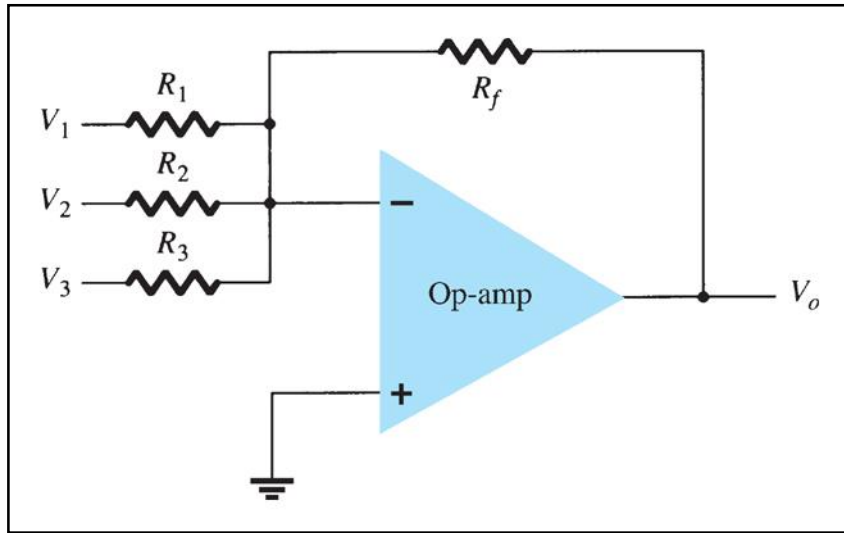

Because the op-amp has a high input impedance, the multiple inputs are treated as separate inputs.

$$V_o = - \left( \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$


# Integrator

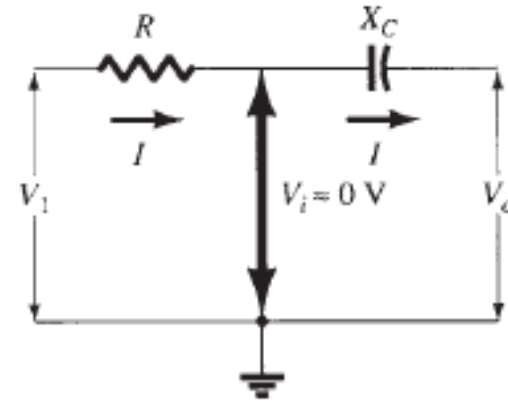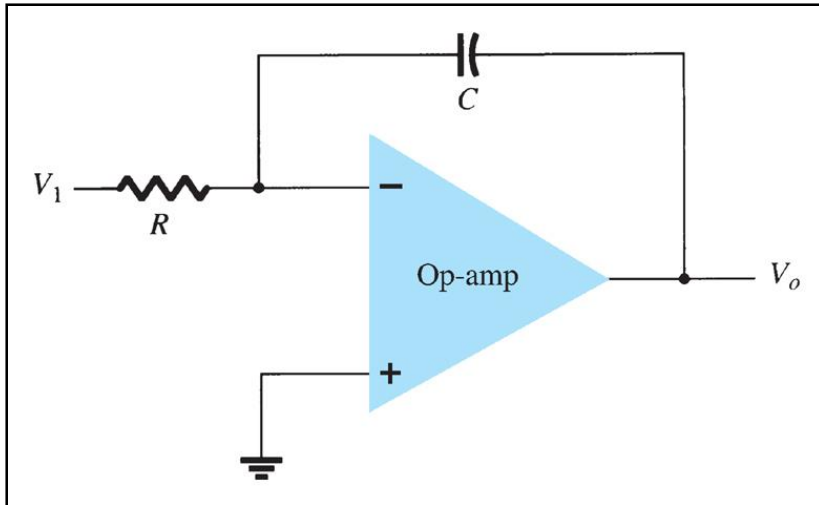

$$v_o(t) = -\frac{1}{RC} \int v_1(t) dt$$

The output is the integral of the input; i.e., proportional to the area under the input waveform. This circuit is useful in low-pass filter circuits and sensor conditioning circuits.

# Differentiator

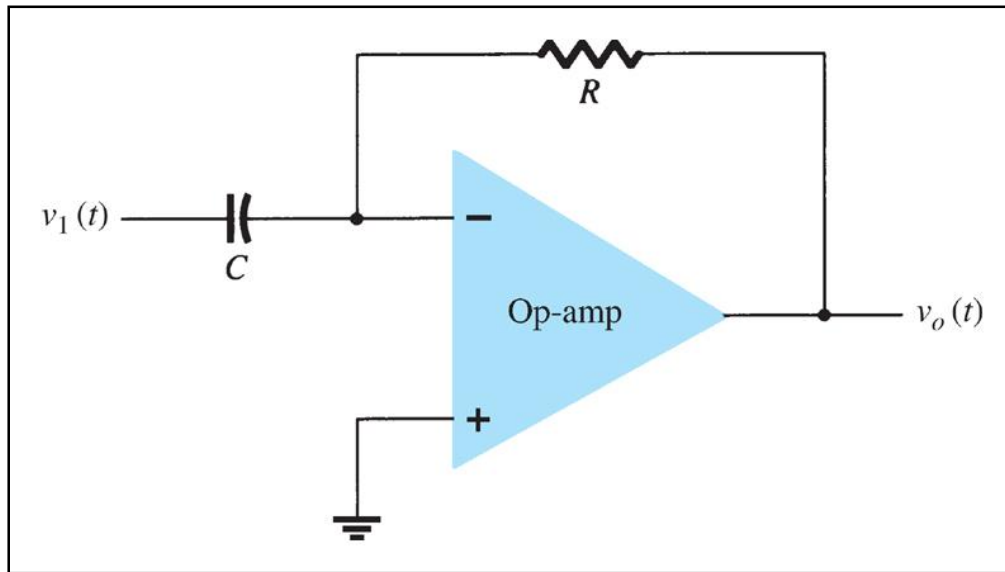

$$v_o(t) = -RC \frac{dv_1(t)}{dt}$$

The differentiator takes the derivative of the input. This circuit is useful in high-pass filter circuits.