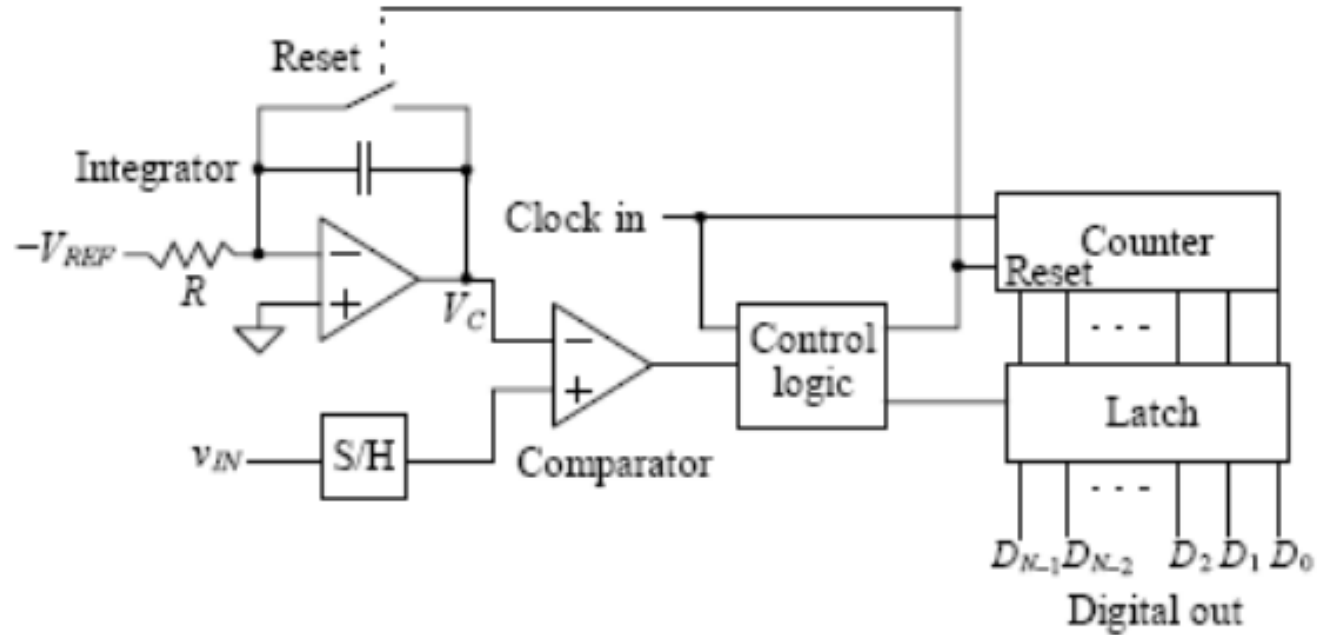



# Linear Integrated Circuits

# Single Slope ADC



- Comparator checks input voltage with integrated reference voltage,  $V_{REF}$
- At the same time the number of clock cycles is being counted.
- When the integrator output equals  $V_{IN}$ , the comparator outputs a logic '0', triggering the counter and integrator to reset and the latch to hold the digital output.

# Single Slope ADC

 


$$t_c = \frac{v_{in}}{\Delta V} T_{CLK}$$
$$= \frac{v_{in}}{V_{REF}} 2^N T_{CLK}$$

- $\Delta V$  the smallest change in analog signal that will result in a change in the digital output, also called «Resolution»

$$\Delta V = \frac{V_{REF}}{2^N - 1} \approx \frac{V_{REF}}{2^N} \quad \text{for large } N$$


# Single Slope ADC

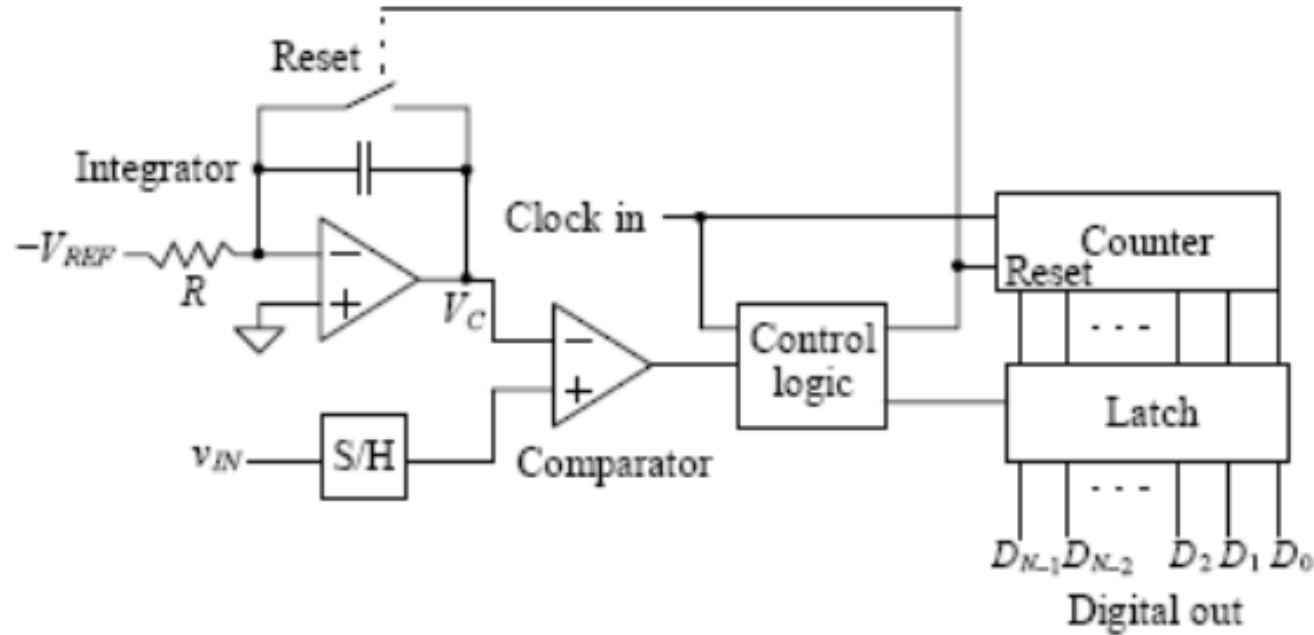

$$t_c = \frac{v_{in}}{\Delta V} T_{CLK}$$
$$= \frac{v_{in}}{V_{REF}} 2^N T_{CLK}$$

- Accuracy depends on tolerance of R and C.
- It would be better to develop an ADC whose accuracy does NOT depend on circuit element tolerances


# Dual Slope ADC

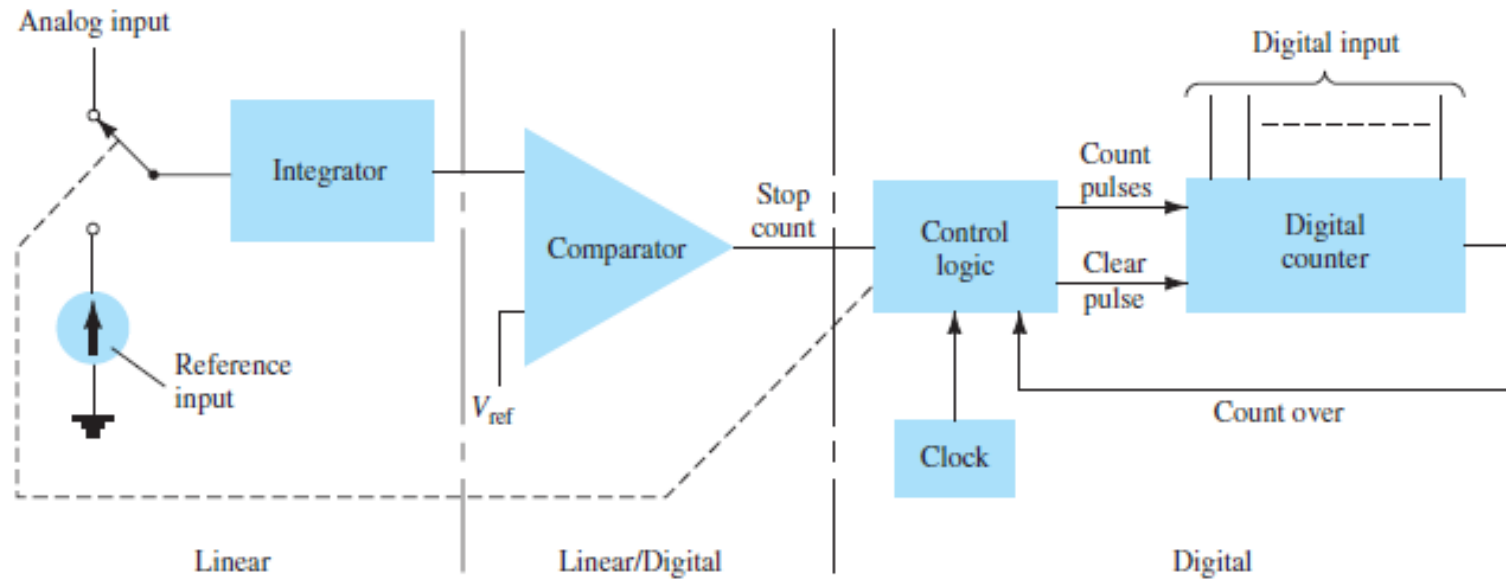



- For a **fixed time interval**, analog voltage connected to the integrator raises the voltage at the comparator input to some positive level
- At the end of this interval, count is set to zero and the electronic switch connects the integrator to a reference or fixed input voltage
- Then, counter advances whereas the integrator's output decreases at a **fixed rate** until it drops below the comparator reference voltage
- Then, control logic receives a signal (the comparator output) to stop the count
- Digital value stored in the counter is the digital output of the converter
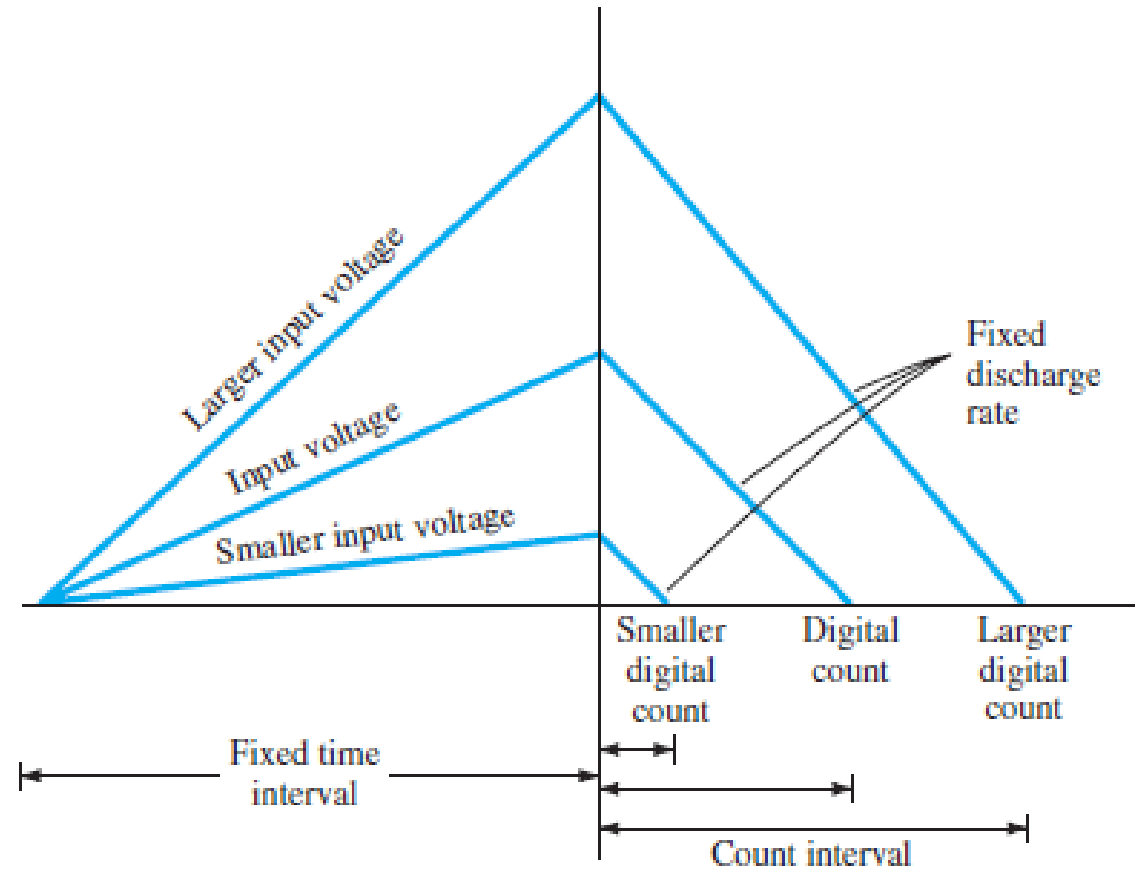
# Dual Slope ADC

- For a **fixed time interval**, analog voltage connected to the integrator raises the voltage at the comparator input to some positive level
- At the end of this interval, the voltage from the integrator is greater for the larger input voltage
- Count is set to zero and the electronic switch connects the integrator to a reference or fixed input voltage
- Counter advances whereas the integrator's output decreases at a **fixed rate** until it drops below the comparator reference voltage




# Ladder Network Conversion

 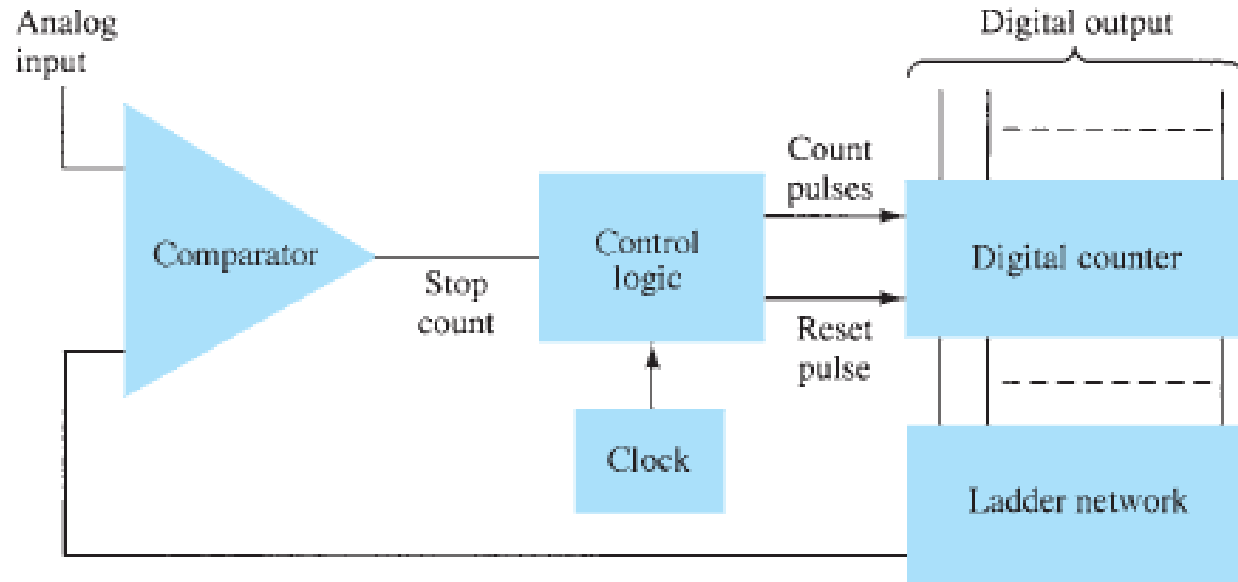

- A digital counter advances from a zero count while a ladder network driven by the counter outputs a staircase voltage, as shown in right Fig., which increases one voltage increment for each count step
- A comparator circuit, receiving both staircase voltage and analog input voltage, provides a signal to stop the count when the staircase voltage rises above the input voltage
- The counter value at that time is the digital output

# Ladder Network Conversion

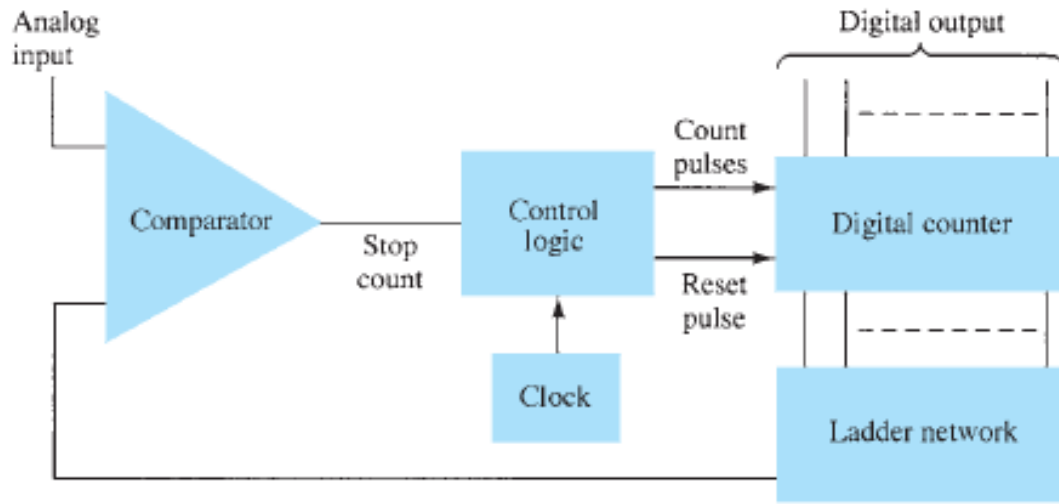

- The amount of voltage change stepped by the staircase signal depends on the number of count bits used
- A 12-stage counter operating a 12-stage ladder network using a reference voltage of 10 V steps each count by a voltage of

$$\Delta V = \frac{V_{ref}}{2^{12} - 1} \approx \frac{10 V}{4096} = 2.4 mV$$

- The minimum number of conversions that could be carried out each second is then


$$\#conversions = \frac{1}{4.1} ms \approx 244 conversions/second$$

- Since a clock rate of 1 MHz operating a 12-stage counter needs a maximum conversion time of  $4096 \times 1\mu s = 4096\mu s \approx 4.1ms$
- Since on the average, with some conversions requiring little count time and others near maximum count time, a conversion time of  $\frac{4.1ms}{2} = 2.05 ms$  is needed,
- And the average number of conversions is  $2 \times 244 = 488$  conversions/second
- A slower clock rate would result in fewer conversions per second
- A converter using fewer count stages (and less conversion resolution) would carry out more conversions per sec.
- The conversion accuracy depends on the accuracy of the comparator



 
# Analog to Digital Conversion Example

- A non-periodic analog signal
- Convert to a digital signal by using a 4-bit ADC
- What should be the sampling rate?
  - At least twice the highest frequency of the signal
  - But signal is NOT periodic
  - Cannot define a period or frequency of the signal
  - Instead we should take the bandwidth of the signal
  - Sampling rate at least twice the bandwidth
  - i.e.  $f_s = \frac{1}{T_s} \geq 2 BW$  (Nyquist criterion)



 
# Analog to Digital Conversion Example

- Sampling
  - Let's take  $T_s = 1 \text{ ms}$  (Assuming it satisfies Nyquist criterion  $f_s = \frac{1}{T_s} \geq 2 \text{ BW}$ )
  - We take samples at each  $T_s$
- Quantization
  - The sampled value of the analog signal is kept constant via a sample and hold circuit.
  - These values will be represented by the combinations that can be obtained by using 4-bits ( $N=4$ )


 
# Analog to Digital Conversion Example

- $$\Delta V = \frac{V_{\max} - V_{\min}}{2^N - 1} = \frac{4 - (-4)}{2^4 - 1} = \frac{8}{15} = 0.53 \text{ V}$$




Analog      Digital  
Signal      Word  
Level

$-3.99 \text{ V} \rightarrow 1111$   
 $+3.46 \text{ V} \rightarrow 1110$   
 $+2.92 \text{ V} \rightarrow 1101$   
 $+2.38 \text{ V} \rightarrow 1100$   
 $+1.85 \text{ V} \rightarrow 1011$   
 $+1.32 \text{ V} \rightarrow 1010$   
 $+0.79 \text{ V} \rightarrow 1001$   
 $+0.26 \text{ V} \rightarrow 1000$   
 $-0.28 \text{ V} \rightarrow 0111$   
 $-0.81 \text{ V} \rightarrow 0110$   
 $-1.34 \text{ V} \rightarrow 0101$   
 $-1.88 \text{ V} \rightarrow 0100$   
 $-2.41 \text{ V} \rightarrow 0011$   
 $-2.94 \text{ V} \rightarrow 0010$   
 $-3.47 \text{ V} \rightarrow 0001$   
 $-4.00 \text{ V} \rightarrow 0000$

| Sample # | Signal value | Quant. value | Digital word |
|----------|--------------|--------------|--------------|
| S1       | +1 V         | +0.79        | 1001         |
| S2       | +2.5 V       | +2.38        | 1100         |
| S3       | +3 V         | +2.92        | 1101         |
| S4       | 0 V          | -0.28        | 0111         |
| S5       | -3.2 V       | -3.47        | 0001         |
| S6       | -1.98 V      | -2.41        | 0011         |
| S7       | +2.6 V       | +2.38        | 1100         |
| S8       | +3.8 V       | +3.46        | 1110         |
| ...      | ...          | ...          | ...          |
 
# Analog to Digital Conversion Example

$$\bullet \Delta V = \frac{V_{\max} - V_{\min}}{2^N - 1} = \frac{4 - (-4)}{2^4 - 1} = \frac{8}{15} = 0.53 \text{ V}$$




| <u>Analog</u><br><u>Signal</u><br><u>Level</u> | <u>Digital</u><br><u>Word</u> |
|------------------------------------------------|-------------------------------|
|------------------------------------------------|-------------------------------|

|         |        |
|---------|--------|
| -3.99 V | → 1111 |
| +3.46 V | → 1110 |
| +2.92 V | → 1101 |
| +2.38 V | → 1100 |
| +1.85 V | → 1011 |
| +1.32 V | → 1010 |
| +0.79 V | → 1001 |
| +0.26 V | → 1000 |
| -0.28 V | → 0111 |
| -0.81 V | → 0110 |
| -1.34 V | → 0101 |
| -1.88 V | → 0100 |
| -2.41 V | → 0011 |
| -2.94 V | → 0010 |
| -3.47 V | → 0001 |
| -4.00 V | → 0000 |

- S1 = 1V does NOT exist among analog signal levels that can be represented by a 4-bit word.
- We have to choose among available values
- 1V is between two quantized values: +0.79 and +1.32
- We choose the lowest one as a rule here.


# Analog to Digital Conversion Example

 

- If one bit is generated in 1 clock cycle of the ADC,
- To represent each signal sample, we need 4 clock cycles
- We can fasten conversion of each analog signal by increasing the clock frequency.

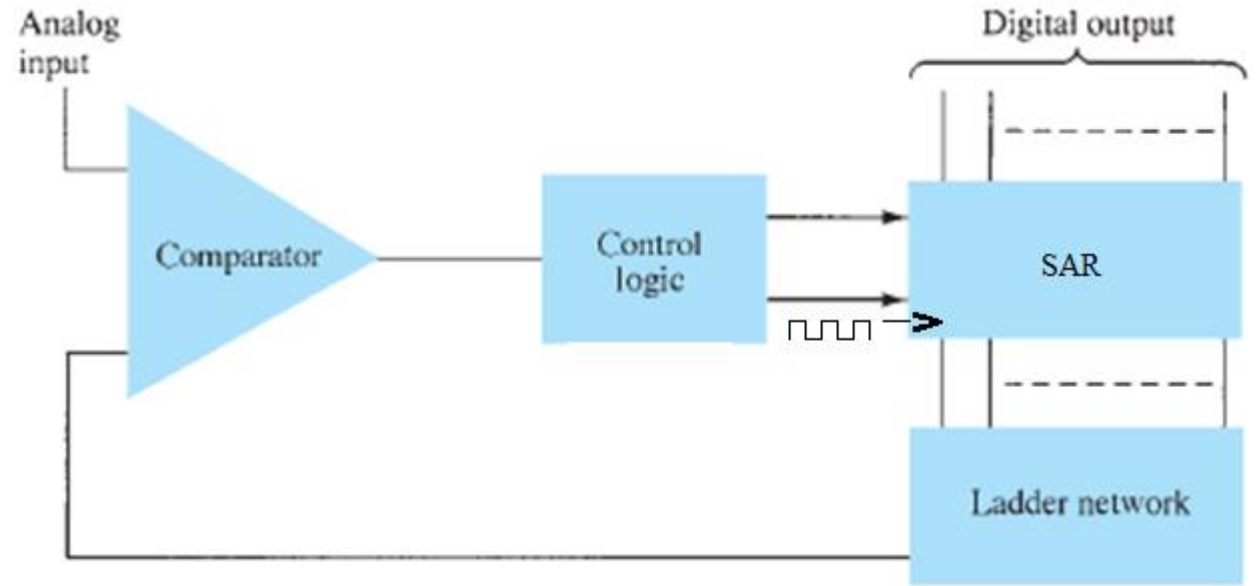
# Successive Approximation ADC

- Initially, the successive approximation register (SAR) is set to a value where only the most significant bit (MSB) is equal to 1, all other bits zero.
- This code is fed into the ladder network,
- The ladder network provides the analog equivalent of this digital code ( $V_{ref}/2$ )
- Comparator checks it with the sampled input voltage level
- If this analog voltage exceeds  $V_{in}$ , the comparator causes the SAR to reset this bit
- Otherwise, the bit is left as 1 and next bit is set to 1 and the same test is done
- This goes on until every bit in the SAR has been tested
- The resulting code is the digital approximation of the sampled input



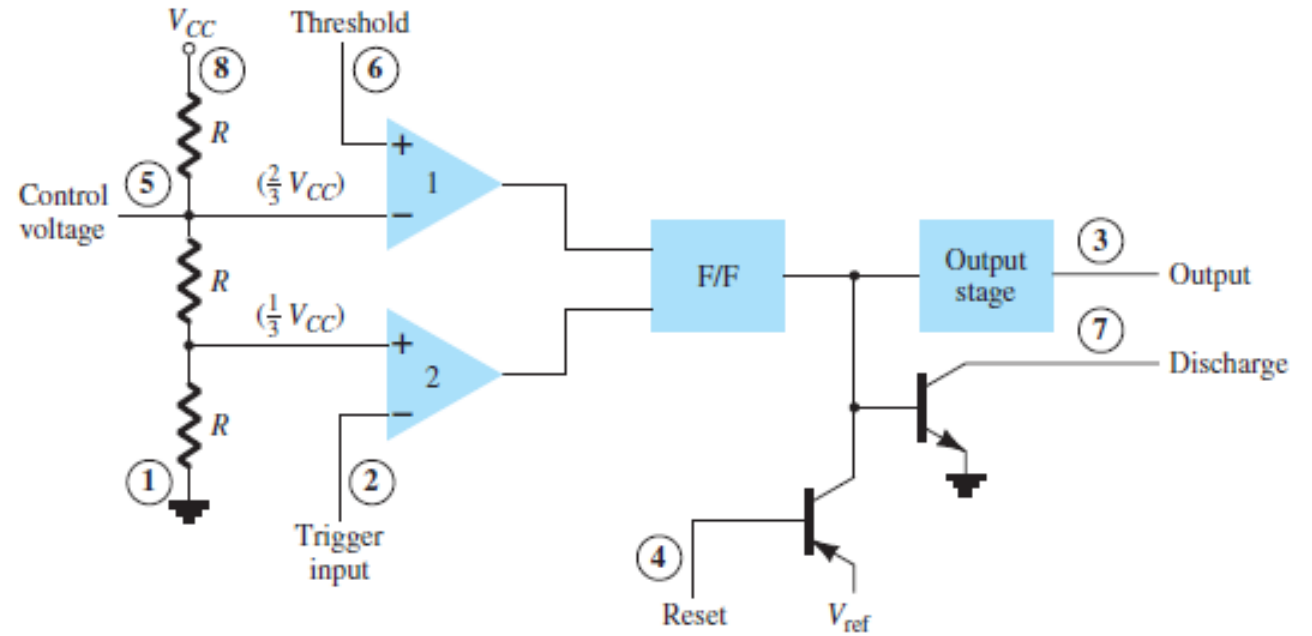
# Timer IC Unit Operation

- Capacitor C charges toward  $V_{CC}$  through external resistors  $R_A$  and  $R_B$
- Capacitor voltage rises until it goes above  $2V_{CC}/3$
- This is the threshold voltage at pin 6, which drives comparator 1 to trigger the flip-flop so that the output at pin 3 goes low
- In addition, the discharge transistor is driven on, causing the output at pin 7 to discharge the capacitor through resistor  $R_B$
- The capacitor voltage then decreases until it drops below the trigger level ( $V_{CC}/3$ )
- The flip-flop is triggered so that the output goes back high and the discharge transistor is turned off, so that the capacitor can again charge through resistors  $R_A$  and  $R_B$  toward  $V_{CC}$ .



# Timer IC Unit Operation


 


$$T_{\text{high}} \approx 0.7(R_A + R_B)C$$

$$T_{\text{low}} \approx 0.7R_B C$$


$$T = \text{period} = T_{\text{high}} + T_{\text{low}}$$
 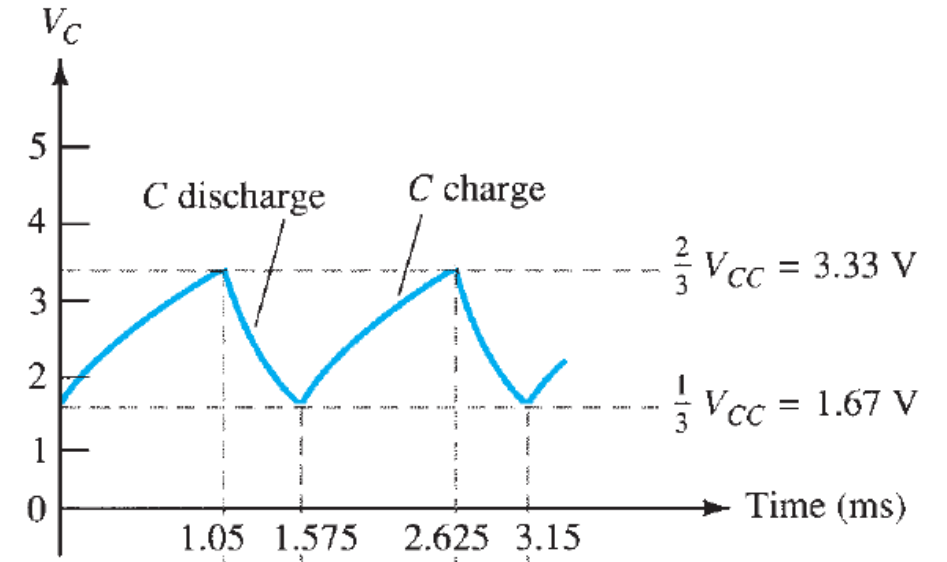
$$f = \frac{1}{T} \approx \frac{1.44}{(R_A + 2R_B)C}$$





# Timer IC Unit Operation


 


$$T_{\text{high}} \approx 0.7(R_A + R_B)C$$


$$T_{\text{low}} \approx 0.7R_B C$$

$$T = \text{period} = T_{\text{high}} + T_{\text{low}}$$
 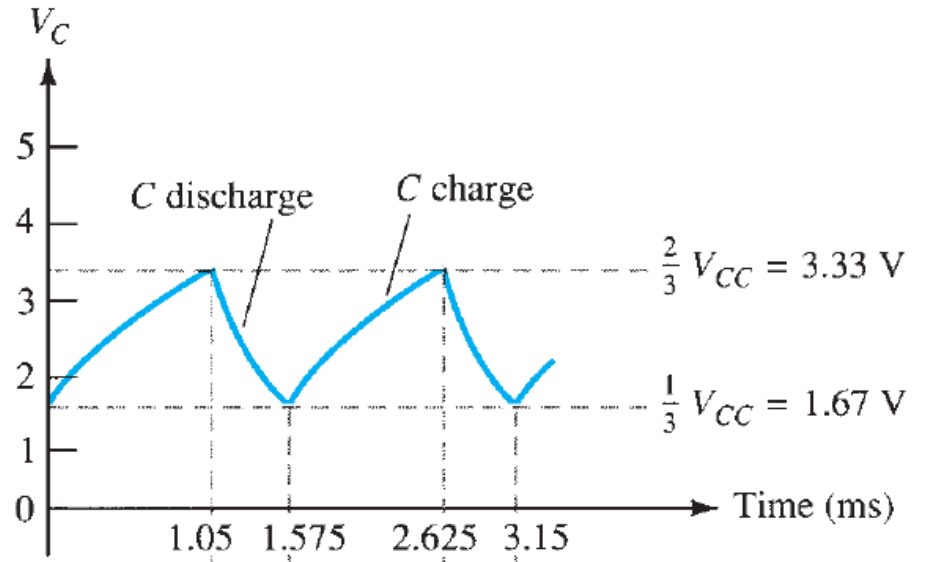
$$f = \frac{1}{T} \approx \frac{1.44}{(R_A + 2R_B)C}$$



# Timer IC Unit Operation

 

$$T_{\text{high}} \approx 0.7(R_A + R_B)C$$

$$T_{\text{low}} \approx 0.7R_B C$$

$$T = \text{period} = T_{\text{high}} + T_{\text{low}}$$



$$f = \frac{1}{T} \approx \frac{1.44}{(R_A + 2R_B)C}$$

$$T_{\text{high}} = 0.7(R_A + R_B)C = 0.7(7.5 \times 10^3 + 7.5 \times 10^3)(0.1 \times 10^{-6}) = 1.05 \text{ ms}$$


$$T_{\text{low}} = 0.7R_B C = 0.7(7.5 \times 10^3)(0.1 \times 10^{-6}) = 0.525 \text{ ms}$$

$$T = T_{\text{high}} + T_{\text{low}} = 1.05 \text{ ms} + 0.525 \text{ ms} = 1.575 \text{ ms}$$
  
$$f = \frac{1}{T} = \frac{1}{1.575 \times 10^{-3}} \approx \mathbf{635 \text{ Hz}}$$



# Timer IC Unit Operation

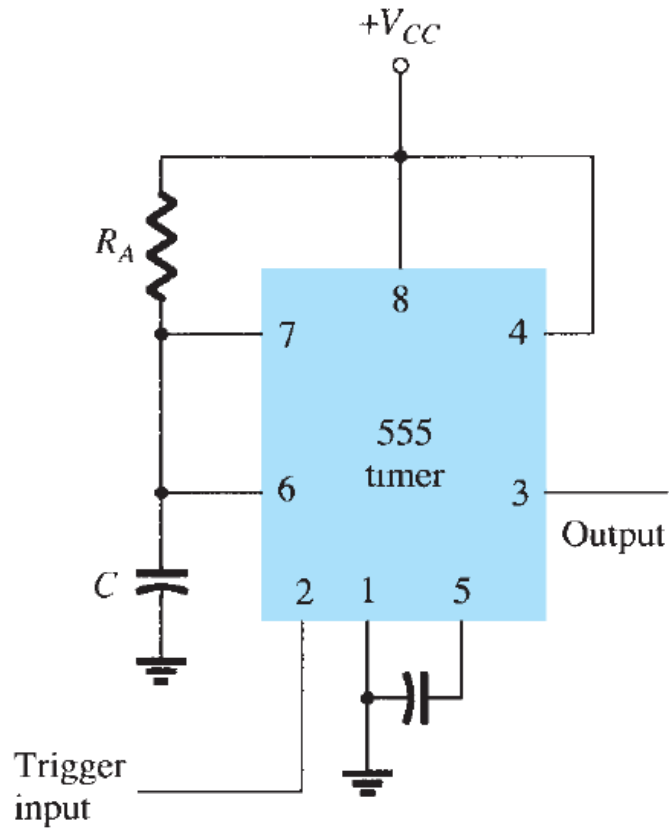

- When trigger input signal goes negative, it triggers the one-shot, with output at pin 3 then going high for a time period given by
$$T_{high} = 1.1R_A C$$
- Negative edge of the trigger input causes comparator 2 to trigger the flip-flop, with the output at pin 3 going high
- Capacitor C charges toward  $V_{CC}$  through resistor  $R_A$
- When the voltage across the capacitor reaches the threshold level of  $2V_{CC}/3$ , comparator 1 triggers the flip-flop, with output going low
- The discharge transistor also goes low, causing the capacitor to remain near 0V until triggered again

