
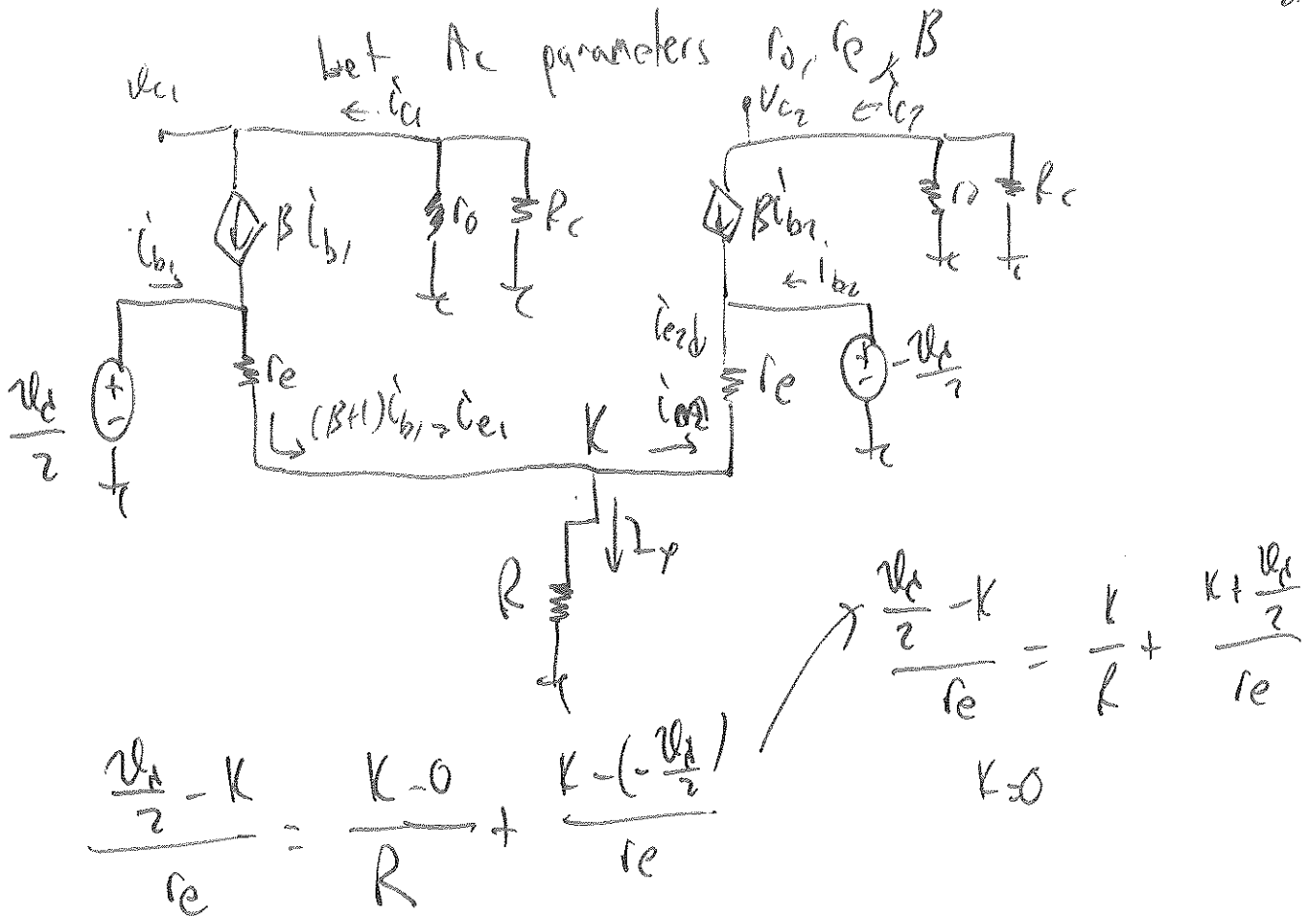


Equivalence of the diff amplifier to a common-emitter amplifier

DC circuit

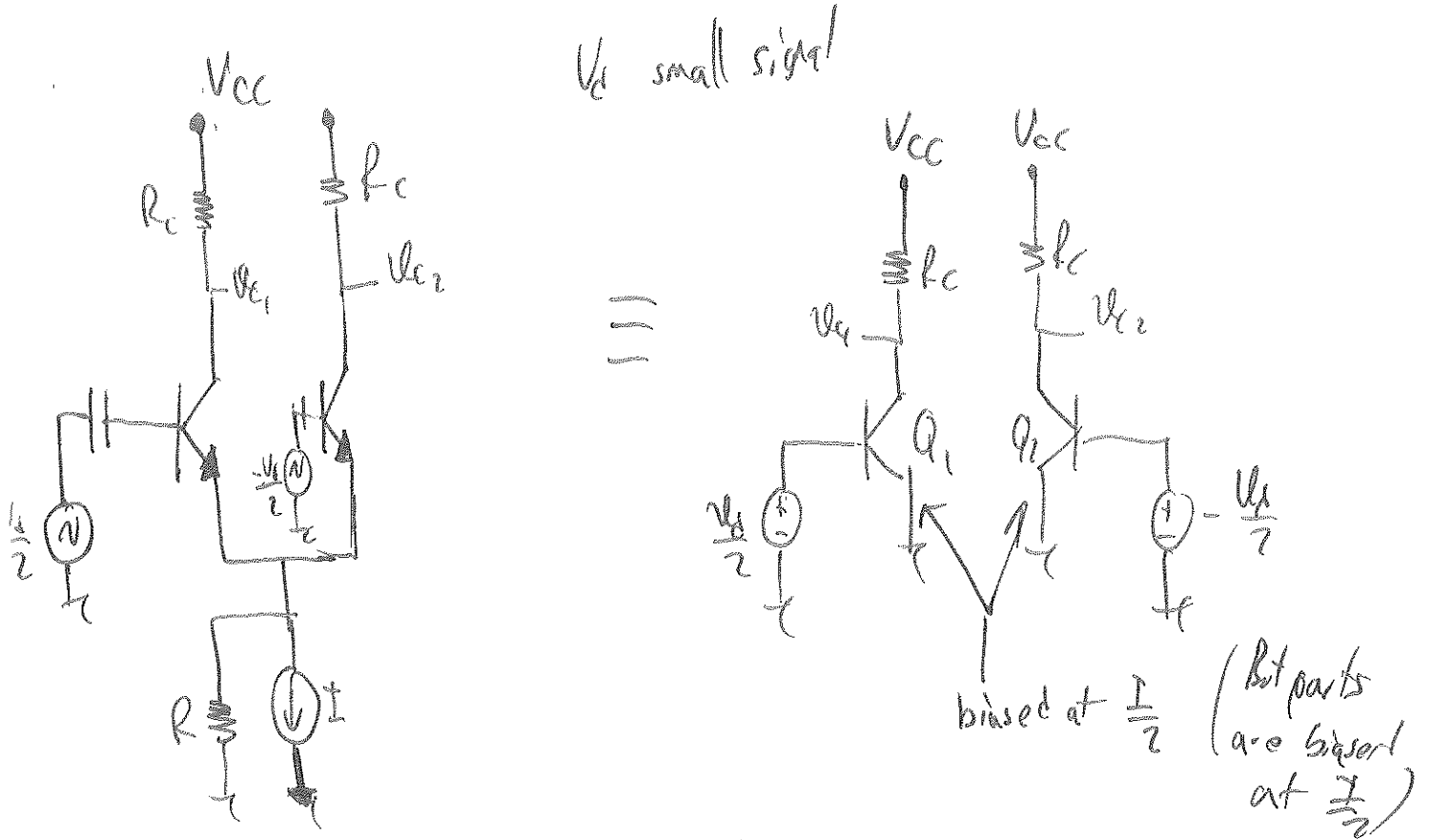

$$i_{c1} = (\beta+1) i_{b1} = \frac{\frac{v_d}{2} - v_c}{r_e} = \frac{v_d}{2r_e} \quad i_{c2} = \frac{0 - (-\frac{v_d}{2})}{r_e} = +\frac{v_d}{2r_e}$$

$$i_{b1} = \frac{v_d}{2r_e(\beta+1)}$$

$$i_{c1} = \beta i_{b1}$$

$$v_{c1} = -[r_o || R_c] i_{c1} = -[r_o || R_c] \beta i_{b1} = -[r_o || R_c] \beta \frac{v_d}{2r_e(\beta+1)}$$

$$v_{c2} = -[r_o || R_c] i_{c2} = -[r_o || R_c] \left(-\frac{v_d}{2r_e(\beta+1)} \right)$$


$$v_{diff}: v_{c1} - v_{c2} = -[r_o || R_c] \frac{v_d \beta}{2r_e(\beta+1)} \times 2 =$$

$$\frac{v_{diff}}{v_d} = \frac{-[r_o || R_c] \beta}{r_e(\beta+1)} \approx \frac{-(R_c || r_o)}{r_e}$$


$$\approx -g_m (R_c || r_o)$$

Common mode gain

AC circuit

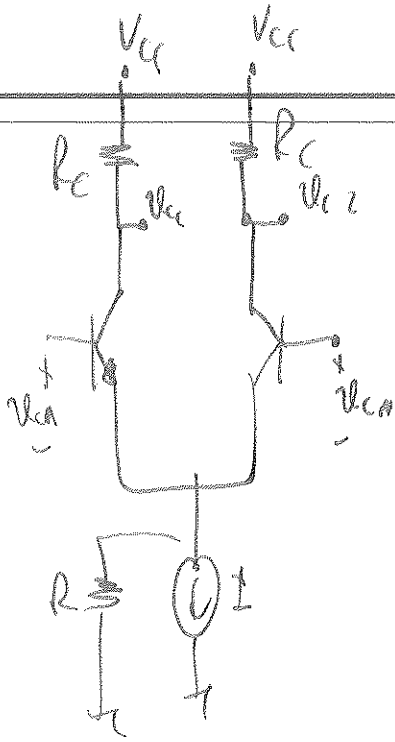

DC circuit

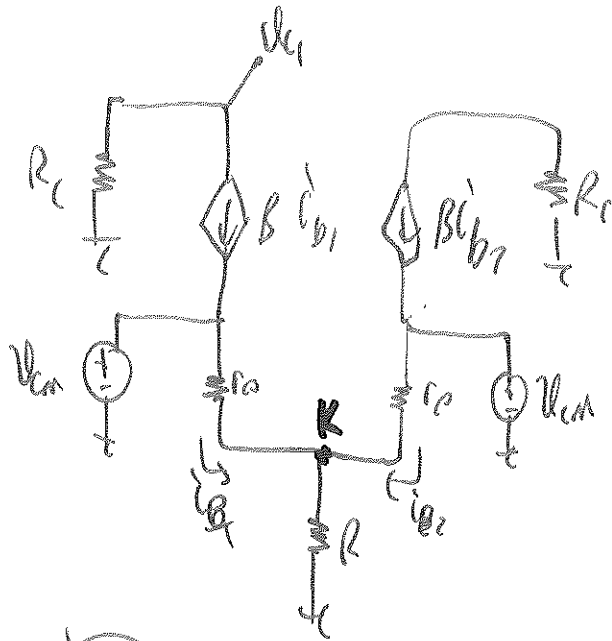

$$v_{c2} = \beta i_{b1} R_C$$

$$\frac{v_{cm} - K}{r_e} + \frac{v_{cm} - K}{r_e} = \frac{K}{R}$$

$$\frac{2v_{cm}}{r_e} = K \left[\frac{1}{r_o} + \frac{1}{r_e} + \frac{1}{R} \right]$$

$$\frac{1}{2} \frac{v_{cm}}{r_e} = K \left[\frac{2r_o + R}{r_o R} \right]$$

~~$$K = \frac{2v_{cm} r_o R}{r_o (2r_o + R)}$$~~

$$K = \frac{2v_{cm} R}{r_o + 2R} = \frac{2v_{cm} R}{r_o + 2R}$$

$$v_{c1} = -\beta i_{b1} R_C$$

$$i_{b1} = \frac{v_{cm} - K}{r_e (\beta + 1)} = \frac{v_{cm} - \frac{2v_{cm} R}{r_o + 2R}}{r_e (\beta + 1)}$$

$$i_{b1} = \frac{v_{cm} r_o}{r_e (r_o + 2R) (\beta + 1)} = \frac{v_{cm}}{(r_o + 2R) (\beta + 1)} \implies v_{c1} = -\frac{v_{cm} (\beta) R_C}{(r_o + 2R) (\beta + 1)}$$