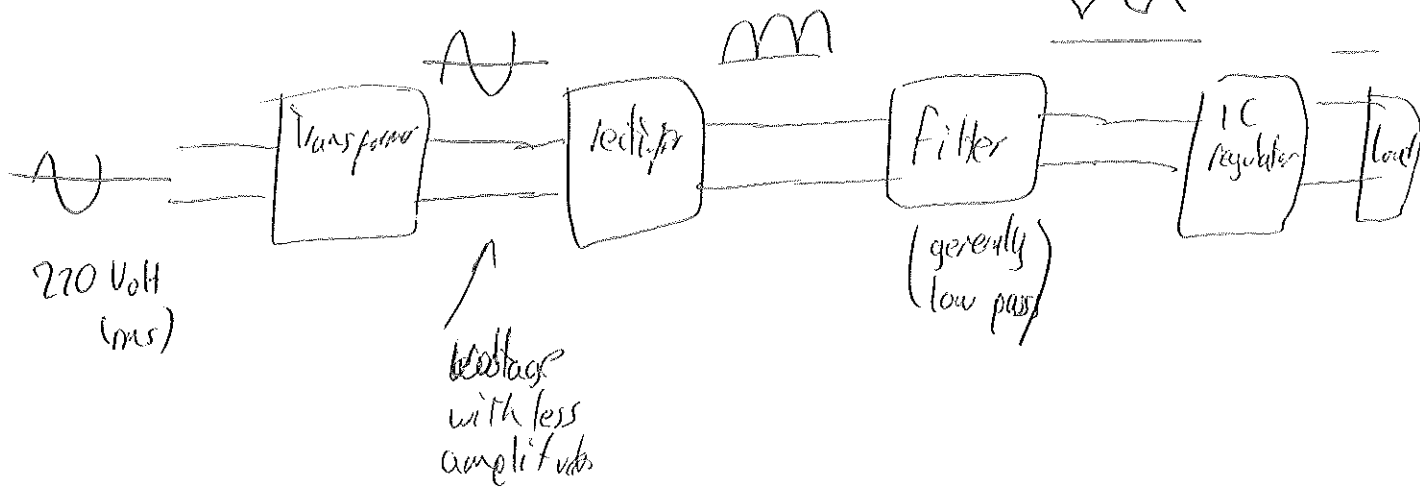


(1)

Power Supplies (Voltage regulators)




The process of obtaining DC from AC voltage

General filter considerations

- A rectifier circuit is necessary to convert a zero average voltage (ex: 220 Volt (ms) electricity from the network) to a non-zero average voltage (DC, 24 Volt, 12 Volt, 6.8 Volt)
- Output of the process is a pulsating DC voltage
- This DC can be used to charge a battery, as a DC voltage is large enough to perform charging of a battery
- Filter is important for pure DC to accomplish jobs related with computers, radio and stereo systems, this will clear the pulsating DC forms

(2) Filter Voltage Regulation and Ripple Voltage

v

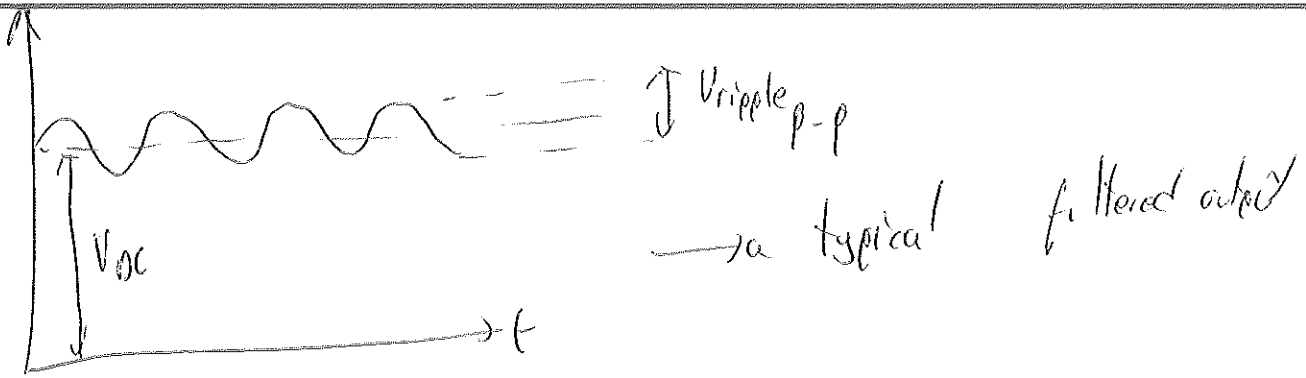

$V_{DC} \rightarrow$ DC value

$V_{ripple\ p-p} \rightarrow$ AC variation at DC (ripple-voltage)

This is obtained from some AC source after rectification so it has ripple but generally battery voltage doesn't contain ripple voltage

- As ripple is smaller the quality of DC increases


$$r = \frac{\text{ripple voltage (rms)}}{\text{DC voltage}} = \frac{V_{p(rms)}}{V_{DC}} \times 100$$

Voltage regulation: Amount of the DC ~~voltage~~ output voltage changes over a range of circuit operation.




$$\text{Voltage regulation} = \frac{\text{no-load voltage} - \text{full-load voltage}}{\text{full-load voltage}} \times 100$$

Voltage regulation is best when no-load voltage = full-load voltage

(3) Capacitor filter

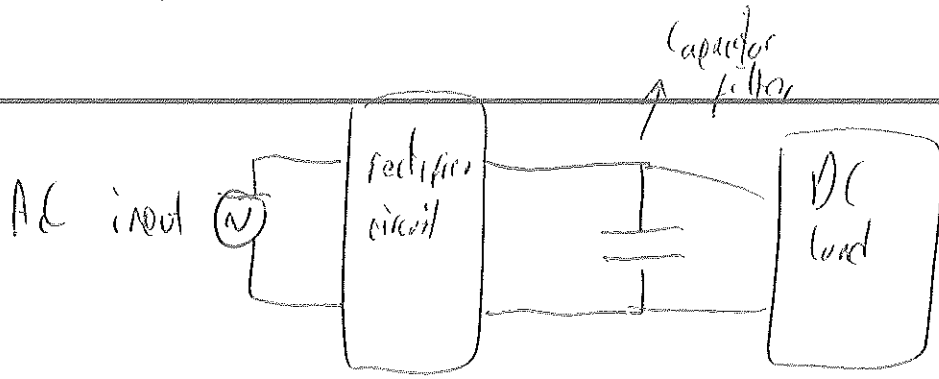

Ex:

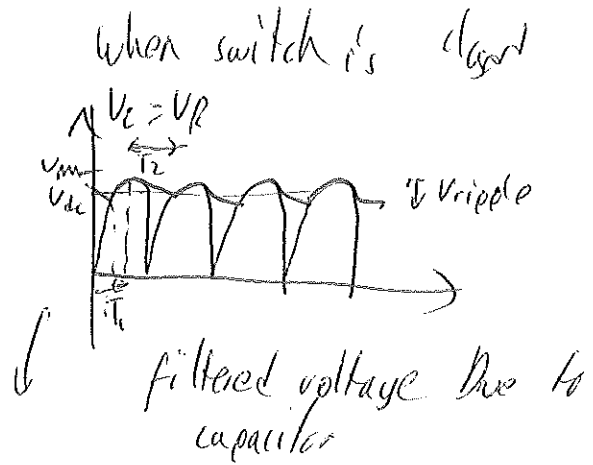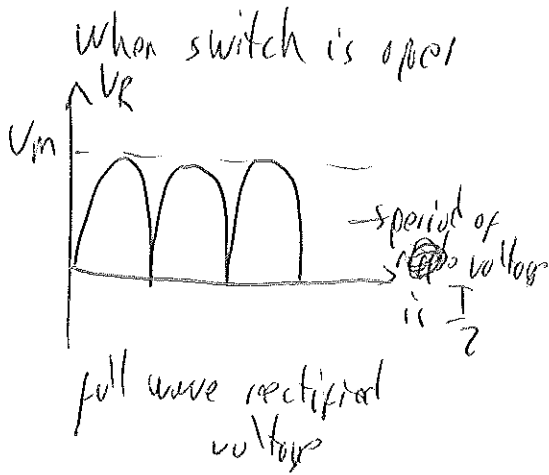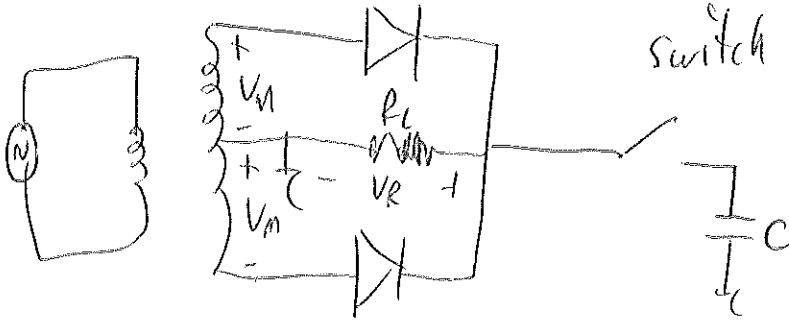

ripple voltage $\leftarrow V_r = \frac{I_{dc}}{4fC} = \frac{V_{dc}}{R_L 4fC}$

$f \rightarrow$ frequency

~~$V_{dc} = V_m$~~
 $V_{dc} = V_m - \frac{V_{dc}}{R_L 4fC}$

$$V_{dc} \left(1 + \frac{1}{4RfC} \right) = V_m$$


$$V_{dc} = \frac{V_m}{1 + \frac{1}{4RfC}}$$

filter capacitor ripple

$$r = \frac{V_r (\text{rms})}{V_{DC} \times 4\sqrt{3}} \times 100 = \frac{V_{DC}}{C R_L V_{DC}} \times 100 \times \frac{1}{4\sqrt{3}}$$

Diode conduction period

Diode conducts only in T_1

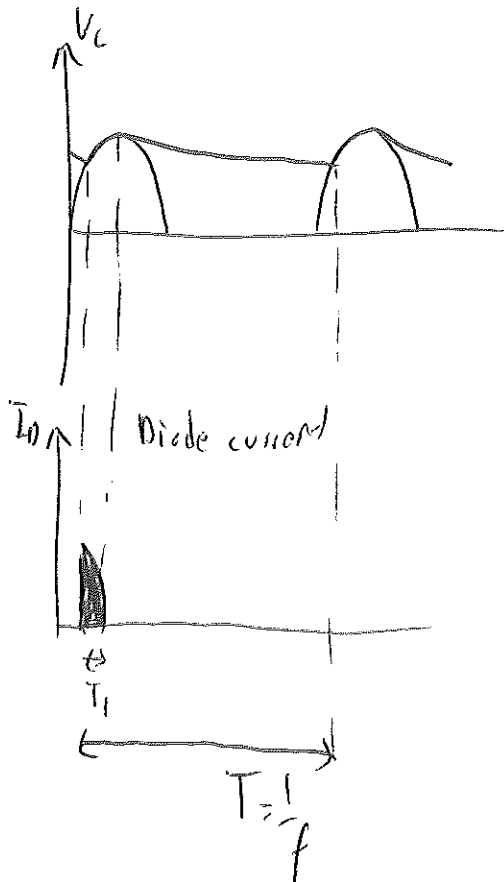


$T_1 =$ diode conduction time

$T = \frac{1}{f}$ period


$I_{DC} =$ Average current drawn from filter. $\frac{V_{DC}}{R_L}$

$I_{peak} =$ peak current through the conducting diodes

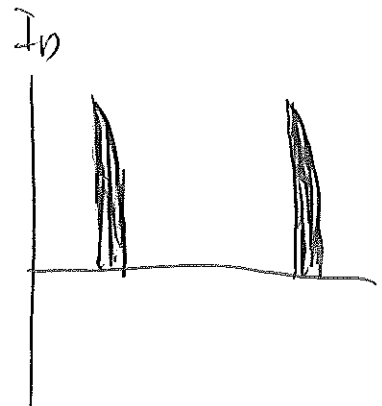if $C \uparrow$ I_D increases \rightarrow




5) RC filter


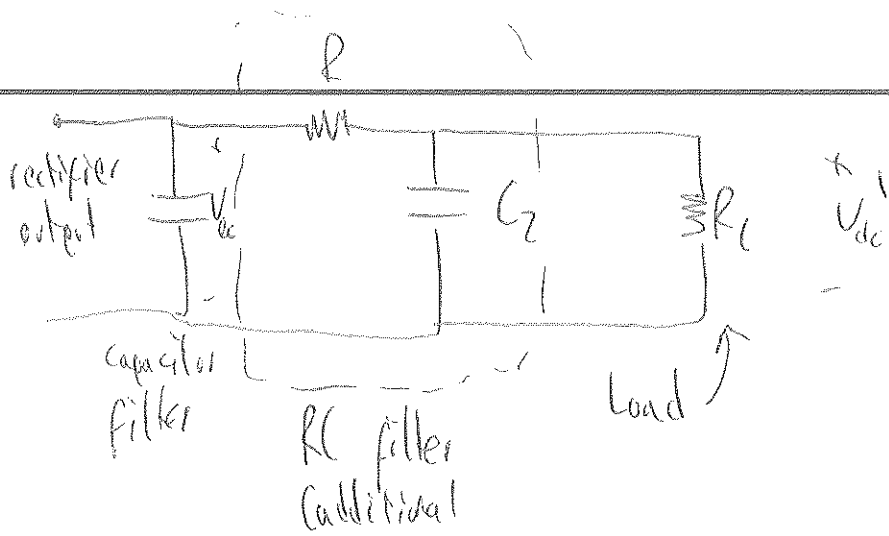


DC operation

$$V_{dc}' = \frac{R_L}{R + R_L} V_{dc}$$

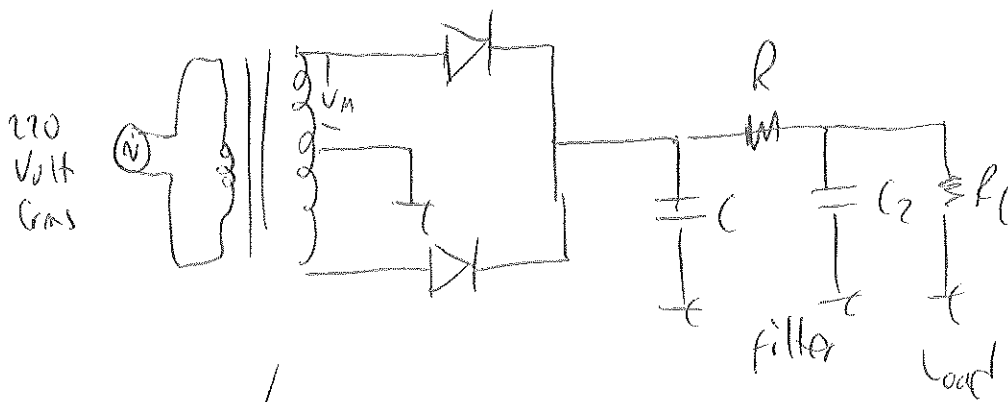

DC equivalent

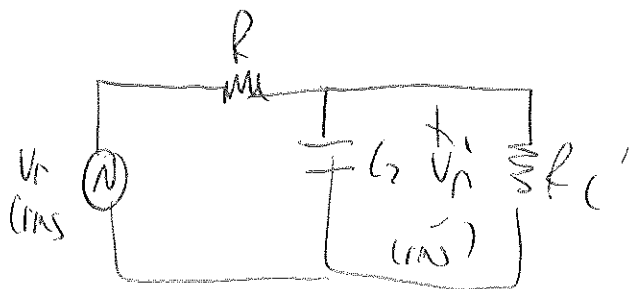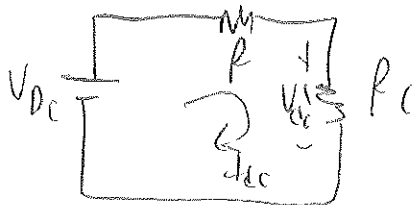

putting R_{C2} filter

$V_r \xrightarrow{\text{drops}} V_r'$
 $V_{DC} \xrightarrow{\text{drops}} V_{DC}'$

(both ripple and DC voltage decreases)

(6)

$$V_1'(rms) = V_1 \times \frac{X_{C2} \parallel X_{R1}}{R_T}$$

$$\frac{X_{C2} X_{R1}}{X_{C2} + X_{R1}}$$

$$R_T \frac{X_{C2} X_{R1}}{X_{C2} + X_{R1}}$$

$$X_{R1} = R_1$$

$$X_{C2} = \frac{1}{sC}$$

$$s = j\omega$$

$$\omega = 2\pi f$$

$$X_{C2} = \frac{1}{j2\pi fC}$$

$$|X_{C2}| = \frac{1}{2\pi fC}$$

generally $(X_{C2} \ll X_{R1})$

hence

$$V_1'(rms) \approx \frac{X_{C2}}{R} V_1(rms)$$