

# Battery Charging Regulator

- $D_1, D_2$  produce full wave rectifier signal across  $SCR_1$
- 12 Volt battery will be charged
- At low battery voltages  $SCR_2$  is at Off state (so  $SCR_2$  is open)
- If  $SCR_2$  is open,  $SCR_1$  acts as series static switch control (discussed in early examples)
- If full wave rectified input is high enough to produce the required turn-on gate current (controlled by  $R_1$ )  $SCR_1$  will turn on and it will charge the battery
- At the beginning as battery is starting being charged the voltage  $V_f$  will be low, due to voltage divider resistor ratios ( $R_4$  and  $R_5$ )
- As  $V_f$  is low the gate voltage of  $SCR_2$ ,  $V_{G_{SCR_2}} = V_{R2} + V_Z$  and  $V_Z$  will be very small (below 11 volt) for conduction and firing  $SCR_2$ , (Zener is open in this case)
- $C_1$  regulates the voltage at  $V_{G_{SCR_2}}$  and prevents any transients to turn on  $SCR_2$  on. (It acts as a DC holder circuit)

- As charge increase  $V_R$  will increase


(2)

~~$V_{SCR}$~~   $V_{SCR_2} = V_R + V_Z \rightarrow V_R + 11$  (it will go for on mode)

at  $V_Z \approx 11$  volt it will fire  $SCR_2$

- As  $SCR_2$  fired  $SCR_1$  Anode-Cathode will be short circuit  $V_Z$  will drop to a lower value and  $SCR_1$  will be at off state (that means charging is finished)

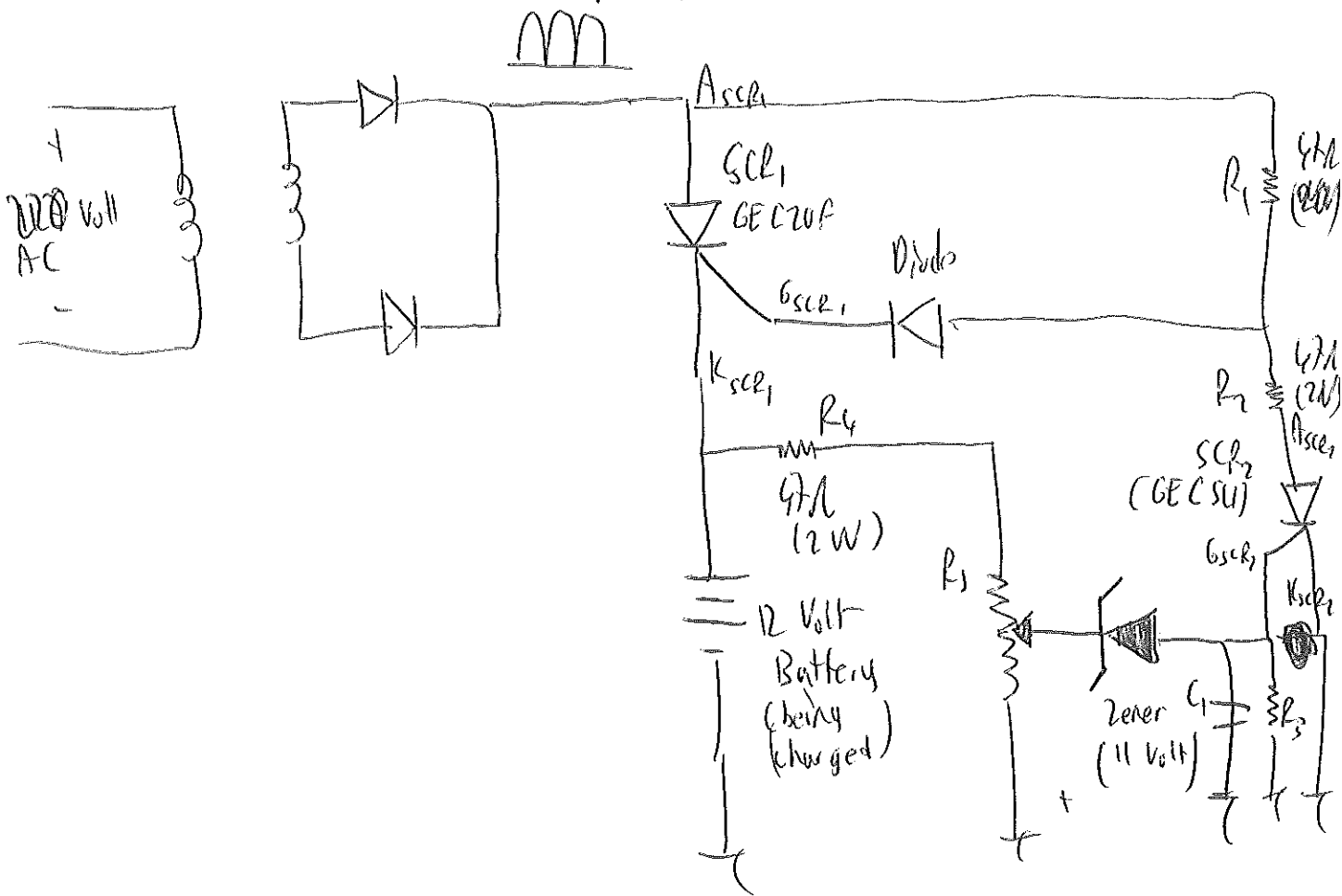Circuit for battery charging  
rectified signal




# Temperature Controller

(3)

100 - Watt heater load

GE C58  
or  
C126B

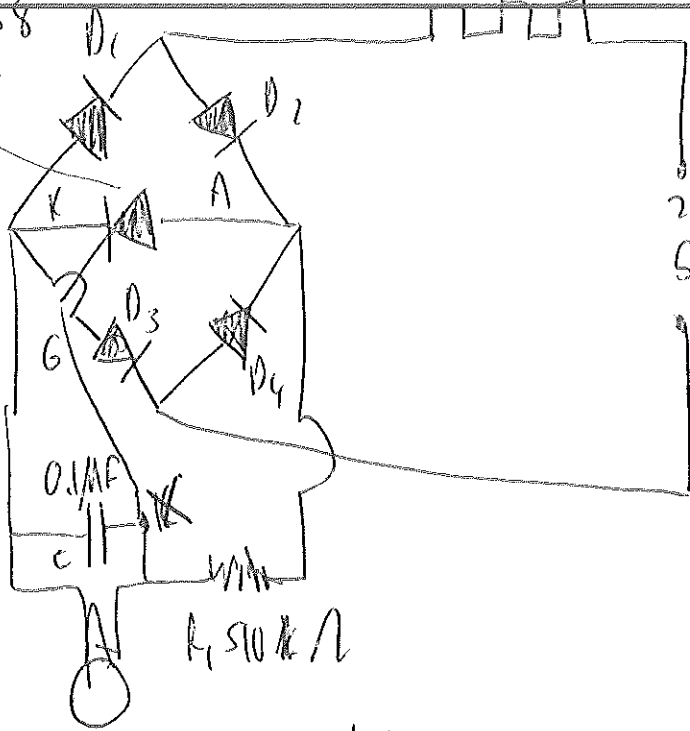


D<sub>1</sub> - D<sub>4</sub>  
GE A14B

Mercury ← Hg in glass thermostat  
(such as vap. air div. 206-44 series  
prints #1141 or equivalent)



- In this circuit SCR acts as current amplifier
- It is not an amplifier in the sense that it magnifies the current level of the thermostat, rather, it is a device whose higher current level is controlled by the behavior of thermostat
- We observe full-wave rectified voltage over SCR
- When thermostat is open the capacitor voltage will be charged over  $f_i$  and  $C$ , and time constant will be  $\tau = CR_1$  as the charging happens  $V_c$  voltage will reach to a value to fire  $G-X_1$ .
- This will trigger the SCR during each half-cycle of the input signal, permitting a flow of charge (current) through heater

- As the temperature rises, the conductive thermostat will be short circuit (as a result capacitor will be shorted) and that will ~~be~~ eliminate the possibility of the capacitor charging to the firing potential and triggering the SCR.
- In this case  $R_1$  will have very low current value

### Silicon Controlled Switch

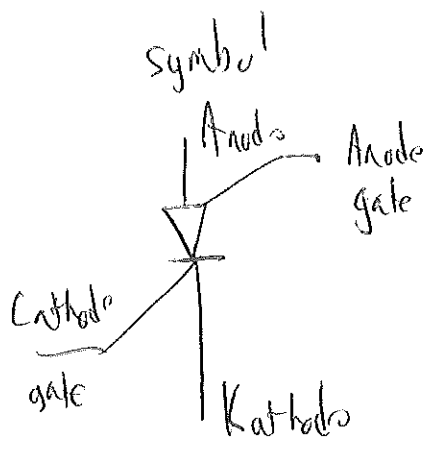

model

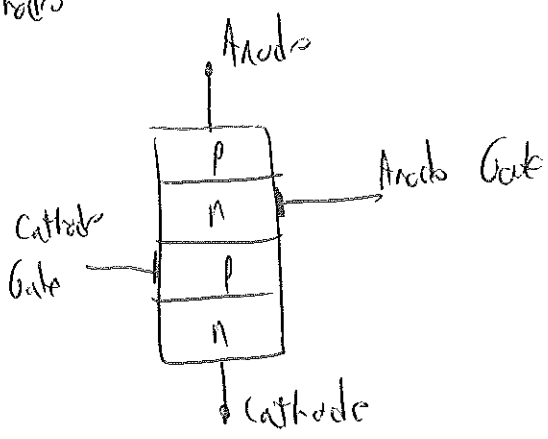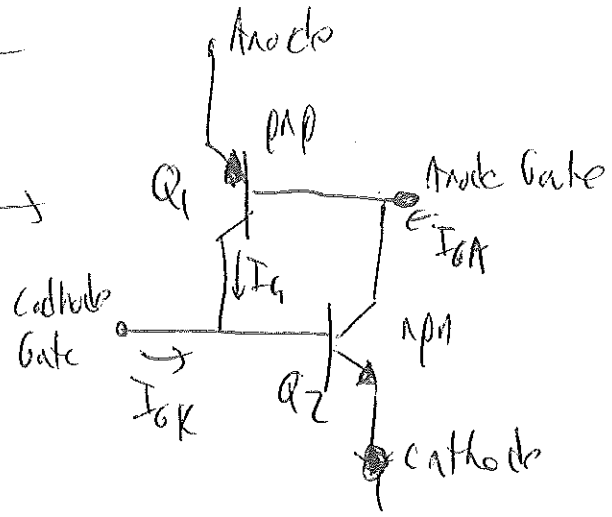

## Turn on techniques


(5)

- Anode gate connector can be used to turn the device ON or OFF
- To turn OFF a negative pulse is necessary and to turn ON a positive pulse is necessary.
- A negative pulse at the anode gate will forward bias base-to-emitter junction  $V_{BE_{Q1}} > 0$  so  $Q_1$  will be ON and  $I_{C1}$  will be produced and  $I_{C1}$  will turn ON  $Q_2$  resulting in a regenerative action and the ON state for SCS (Silicon Controlled Switch) will be observed
- Reverse A positive pulse will turn base-to-emitter junction to reverse bias  $V_{BE_{Q1}} < 0$  so  $Q_1$  will be OFF and SCS will be OFF state,


Generally (turn-on) anode gate current  $I_{GA}$  is 1.5mA whereas the required cathode gate current  $I_{GC}$  is 1mA.

# Turn-off circuits


(6)

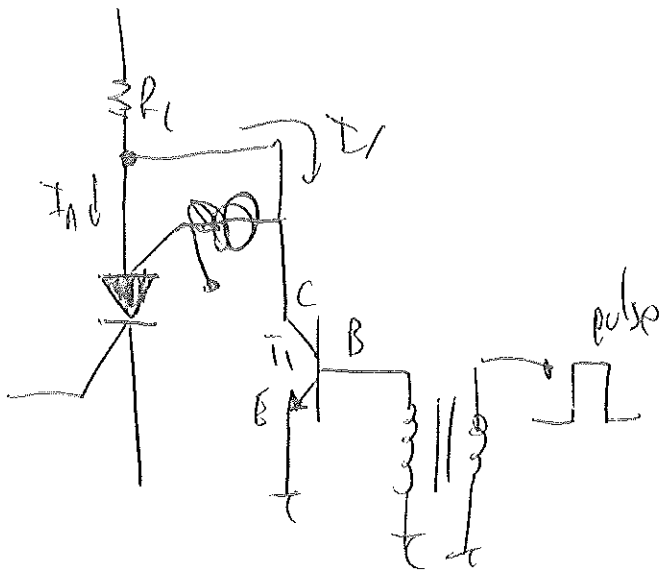

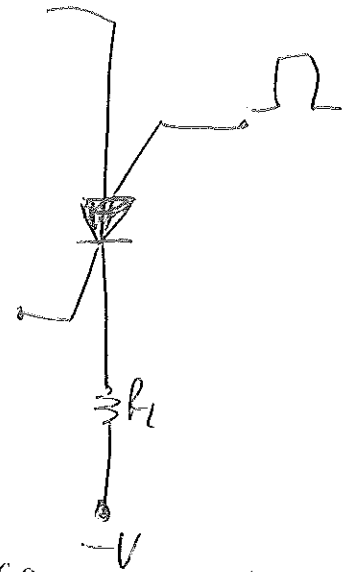(a) Apply pulse, the transistor will conduct heavily, resulting in low impedance (short-circuit) over C and E of  $T_1$ , so  $I_f$  will be pulled by  $T_1$  and  $I_x$  will increase  $I_A$  will decrease



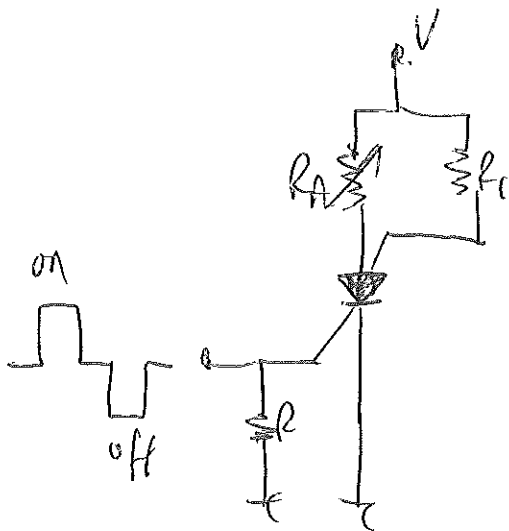(b) Positive pulse at the anode gate will open circuit SCS




→ (c) apply a suitable pulse ~~on~~ on or off? at the cathode gate with proper magnitude  
-  $R_A$  should be selected suitably

- SCS has reduced turn-on time w.r.t. SCR
- SCS has increased triggering and control sensitivity
- Applications of SCS (Voltage sensor, alarm circuit)

# DIAC



symbols

(7)

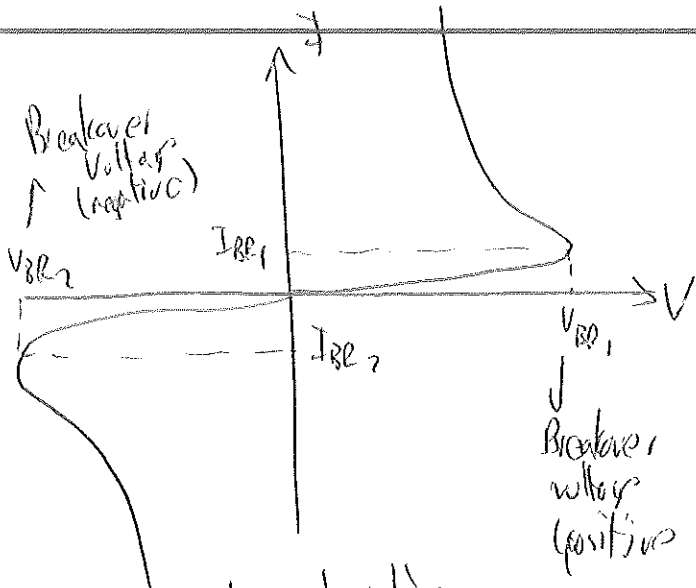

characteristic

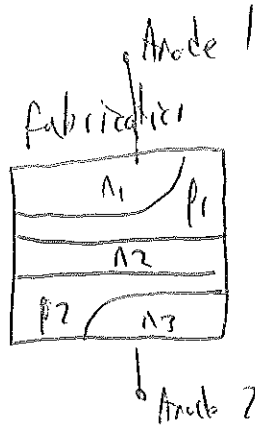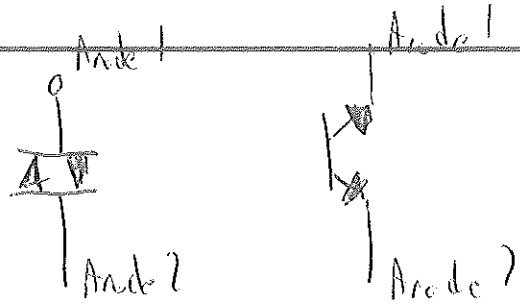$I_{BR1}$ ,  $I_{BR2}$  → breakover currents





- Permit triggering in both directions
- ON operation is possible in both directions

Generally  $V_{BR1} = V_{BR2} \pm 0.1 V_{BR2}$

$$28 < V_{BR1}, V_{BR2} < 42$$

$$I_{BR1}, I_{BR2} \approx 0.2 \text{ mA}$$

## Proximity detector

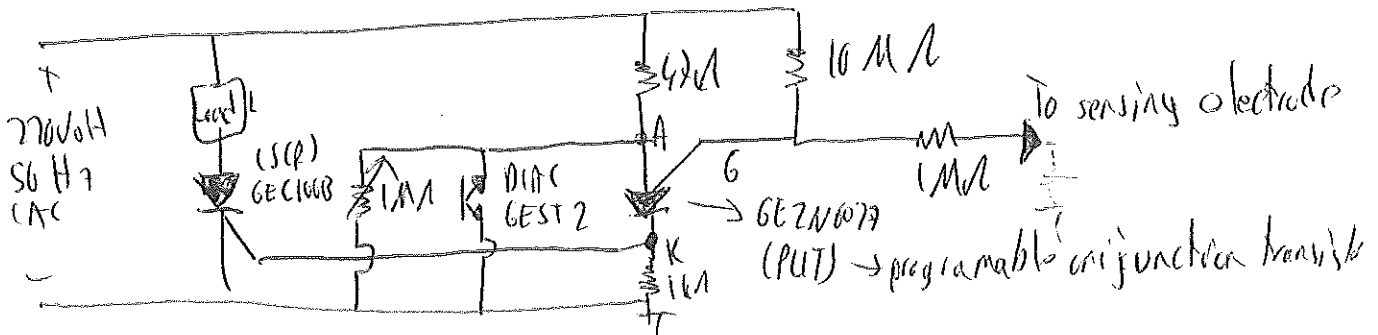
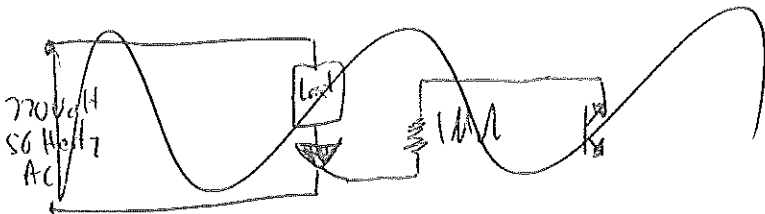


- As human body approaches to the sensing electrode the capacitance b/w electrode and ground increases. The UST


(8)

(PUT programmable unijunction transistor) is a device that will fire (enter short circuit) when  $A \geq 6 + 0.7$  (for silicon)

Before UST turn on (at off mode)

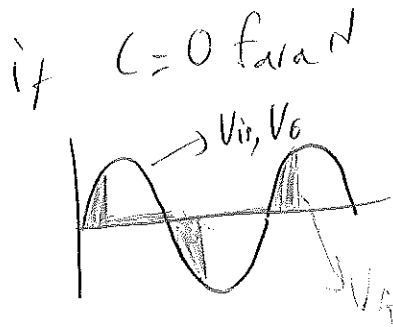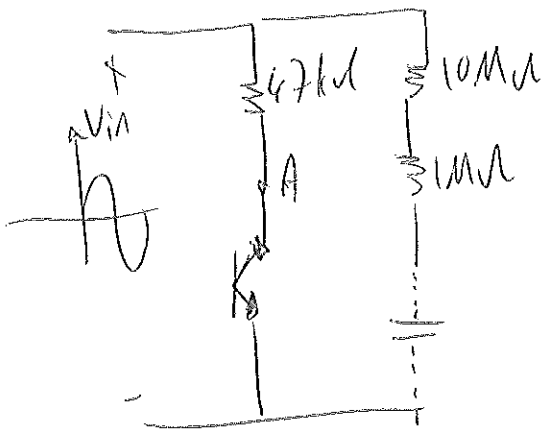

if  $C \neq 0$  farad

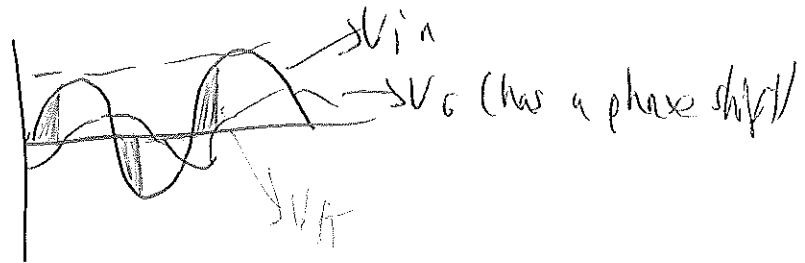

- As input voltage rises, the diac voltage  $V_G$  will follow until firing potential is reached

- It will then turn on and the diac voltage will drop substantially (diac is in essentially open-circuit state until it fires)

-  $A$  can never be greater than  $B$  by 0.7

- As capacitive element is introduced  $B$  can lag and  $A$  can be greater than  $B$  by 0.7 and the PUT will be fired





- PUT will establish heavy current in this case and  $V_G$  voltage will rise an SCR will be turned on and heavy current will be observed



over load (meaning a person is approaching)

(9)

TRIAC

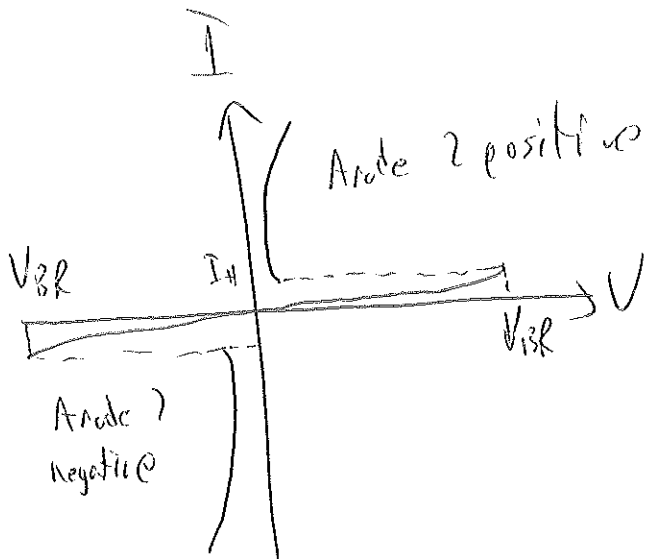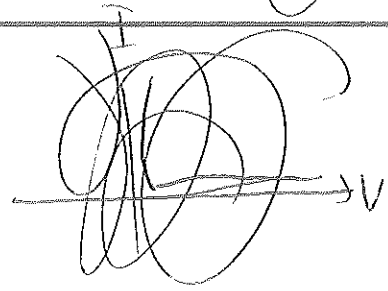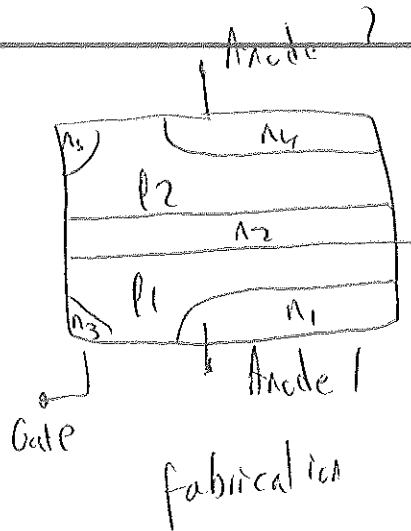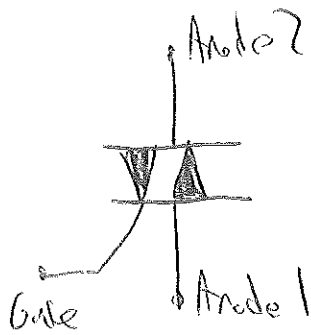

Phase (Power) Control

