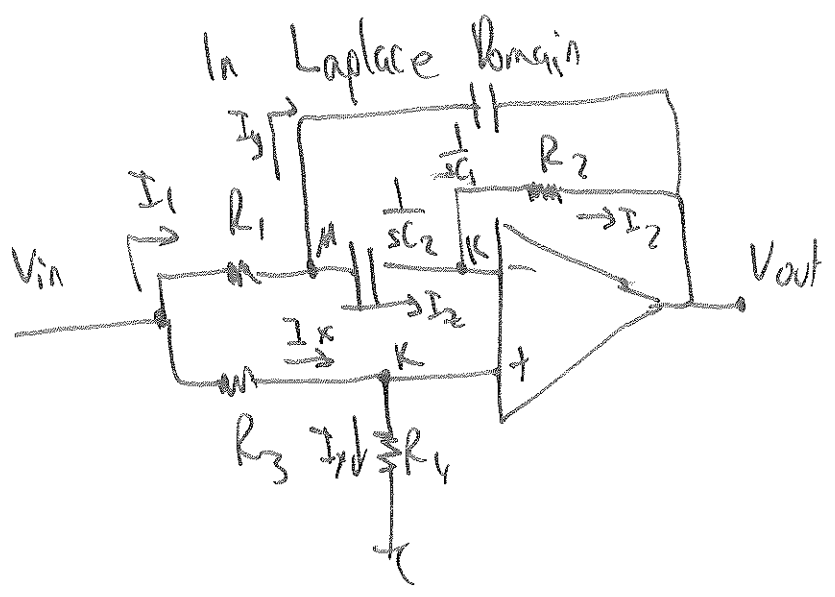



Band-stop filter
(multiple feedback)

MECE 397
Week 8 extra notes
Band-stop filter



$$\frac{V_{in} - K}{R_3} = \frac{K}{R_4} \quad \text{Let } R_3 = R_4$$

$$K = V_{in} \frac{R_4}{R_3 + R_4}$$

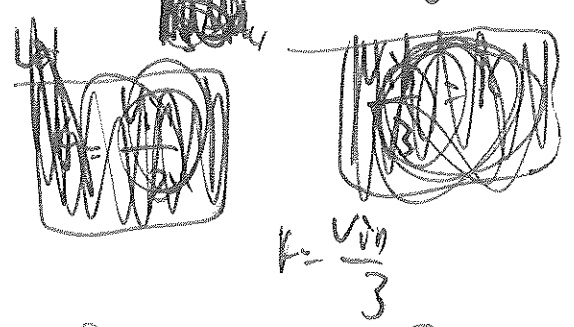

$$\frac{V_{in} - M}{R_1} = \frac{M - K}{\frac{1}{sC_2}} + \frac{M - V_{out}}{\frac{1}{sC_1}}$$

$$\frac{V_{in}}{R_1} = M \left[\frac{1}{R_1} + sC_1 + sC_2 \right] - K sC_2 - V_{out} sC_1 \quad \left[\text{Let } C_1 = C_2 = C \right]$$

$$\frac{V_{in}}{R_1} = M \left[\frac{1}{R_1} + 2sC \right] - K sC - V_{out} sC$$

$$\frac{M - K}{\frac{1}{sC_2}} = \frac{K - V_{out}}{R_2}$$

$$M sC = K \left[\frac{1}{R_2} + sC \right] - \frac{V_{out} sC}{R_2}$$

$$V_{in} = M[1 + 2sCR_1] - KsCR_1 - V_{out}sCR_1$$

$$MsCR_2 = K[1 + sCR_2] - V_{out}$$

$$K = \frac{V_{in}}{3}$$

$$M = \frac{V_{in}}{1 + 2sCR_1} + \frac{KsCR_1}{1 + 2sCR_1} + \frac{V_{out}sCR_1}{1 + 2sCR_1} = \frac{K[1 + sCR_2]}{sCR_2} - \frac{V_{out}}{sCR_2}$$

$$V_{in}sCR_2 + Ks^2C^2R_1R_2 + V_{out}s^2C^2R_1R_2 = K[1 + sCR_2][1 + 2sCR_1] - V_{out}(1 + 2sCR_1)$$

Let $R_1 = R_2 = R$

$$V_{in}sCR + Ks^2C^2R^2 + V_{out}s^2C^2R^2 = K[1 + sCR][1 + 2sCR] - V_{out}(1 + 2sCR)$$

$$V_{in}sCR + V_{out}[\cancel{1 + 2sCR} + s^2C^2R^2] = K[1 + 2s^2C^2R^2 - s^2C^2R^2 + 3sCR]$$

$$V_{in}sCR + V_{out}[\cancel{1 + 2sCR} + s^2C^2R^2] = K[1 + s^2C^2R^2 + 3sCR]$$

$$V_{in}sCR + V_{out}[\cancel{1 + 2sCR} + s^2C^2R^2] = \frac{V_{in}}{3}[1 + s^2C^2R^2 + 3sCR]$$

$$V_{in}sCR + V_{out}[\cancel{1 + 2sCR} + s^2C^2R^2] = V_{in}\left[\frac{1}{3} + \frac{1}{3}s^2C^2R^2 + sCR\right]$$

$$V_{out}[\cancel{1 + 2sCR} + s^2C^2R^2] = \frac{1}{3}V_{in}[1 + s^2C^2R^2]$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{3} \frac{1 + s^2C^2R^2}{1 + 2sCR + s^2C^2R^2}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{3} \frac{1s^2C^2R^2}{1+2sCR+s^2C^2R^2} = \frac{1}{3} \frac{s^2 \cdot \frac{1}{C^2R^2}}{s^2 + s \frac{2}{CR} + \frac{1}{C^2R^2}}$$


$$H(j\omega) \rightarrow \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{1}{3} \frac{\left[-\omega^2 + \frac{1}{C^2R^2}\right]}{\left[-\omega^2 + \frac{1}{C^2R^2}\right] + j\omega \frac{2}{CR}}$$

if $\omega = 0$ $|H(j\omega)| = \frac{1}{3} //$

if $\omega \rightarrow \infty$ $|H(j\omega)| = \frac{1}{3}$


if $\omega = \frac{1}{CR}$ $|H(j\omega)| = 0$

$$|H(j\omega)| = \frac{\left|\frac{1}{C^2R^2} - \omega^2\right|}{\sqrt{\left(\frac{1}{C^2R^2} - \omega^2\right)^2 + \left(\frac{2\omega}{CR}\right)^2}}$$

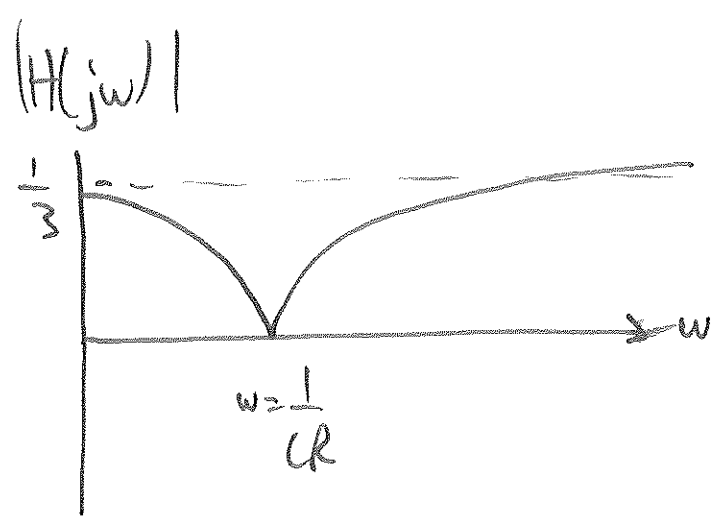

State variable filter

In Laplace domain

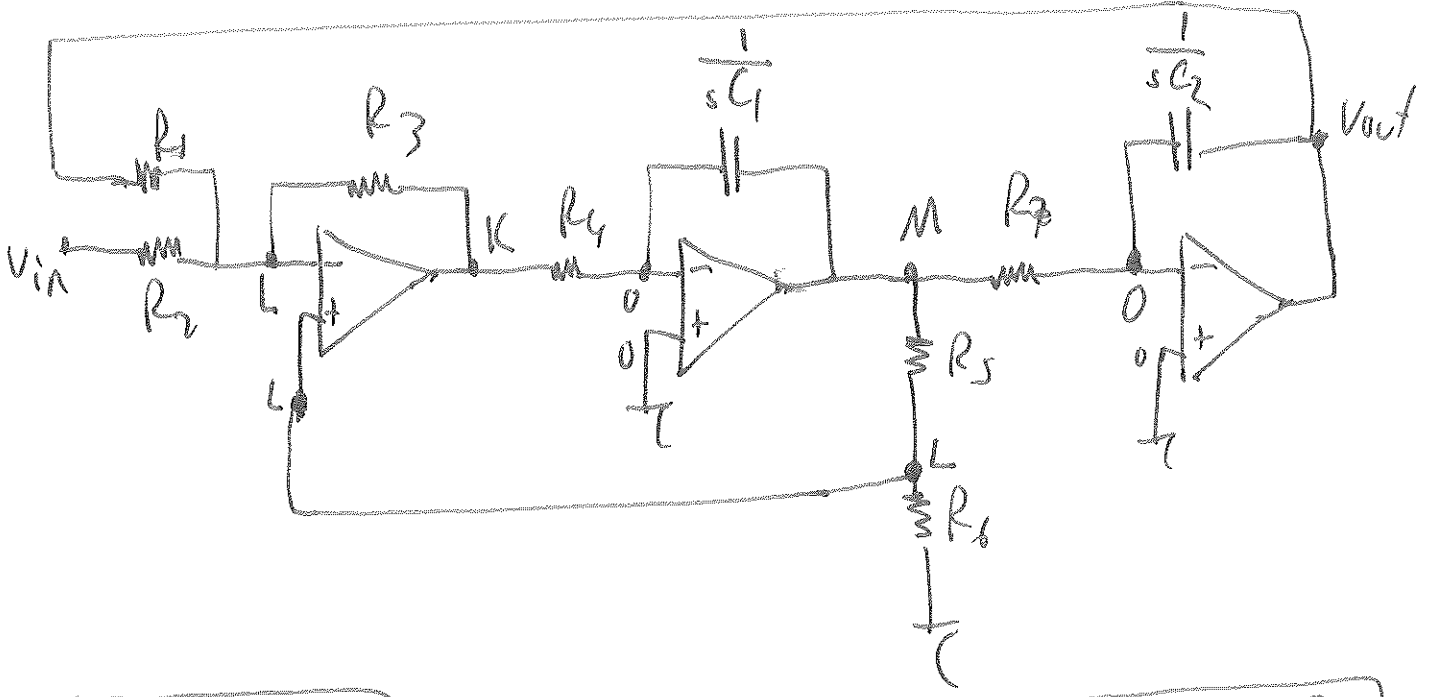

$$L = M \frac{R_6}{R_5 R_6}$$

$$\frac{K - 0}{R_4} = \frac{0 - M}{\frac{1}{sC_1}}$$

$$K = -M [R_4 s C_1]$$

$$K = -M s C_1 R_4$$

$$M = -V_{out} s C_2 R_7$$

$$\frac{M - 0}{R_7} = \frac{0 - V_{out}}{\frac{1}{sC_2}}$$

$$\frac{V_{in} - L}{R_2} + \frac{V_{out} - L}{R_1} = \frac{L - K}{R_3}$$

$$\frac{V_{in}}{R_2} + \frac{V_{out}}{R_1} = L \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] - \frac{K}{R_3}$$

$$\frac{V_{in}}{R_2} + \frac{V_{out}}{R_1} = M \frac{R_6}{R_5 R_6} \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] + \frac{M s C_1 R_4}{R_3}$$

$R_1 = R_2 = R_3 = R_4 = R_7$ $C_1 = C_2$ let $\frac{R_6}{R_5 R_0} = X$

$\frac{V_{in}}{R} + \frac{V_{out}}{R} = M \left[\frac{3}{R} \right] + MsC$, $M = -V_{out} sCR$

$\frac{V_{in}}{R} + \frac{V_{out}}{R} = M \left[\frac{3X}{R} + sC \right]$

$K = -MsCR$

$\frac{V_{in}}{R} + \frac{V_{out}}{R} = -V_{out} sCR \left[\frac{3X}{R} + sC \right]$

$\frac{V_{in}}{R} = -V_{out} \left[\frac{1}{R} + 3sCR + s^2 C^2 R \right]$

$\frac{V_{in}}{R} = -V_{out} \left[\frac{1 + 3sCRX + s^2 C^2 R^2}{R} \right]$

$\frac{V_{out}}{V_{in}} = - \frac{1}{s^2 C^2 R^2 + 3sCRX + 1}$

Low pass filter

put. $V_{out} = - \frac{M}{sCR}$

~~Vout~~

$\frac{- \frac{M}{sCR}}{V_{in}} = - \frac{1}{s^2 C^2 R^2 + 3sCRX + 1}$

$\frac{M}{V_{in}} = \frac{sCR}{s^2 C^2 R^2 + 3sCRX + 1}$ → Band-pass filter

$$M_z = \frac{-K}{sCR}$$


Page 6

$$\frac{\frac{-K}{sCR}}{V_{in}} = \frac{sCR}{s^2 C^2 R^2 + 3sCRX + 1}$$

$$\frac{K}{V_{in}} = \frac{-s^2 C^2 R^2}{s^2 C^2 R^2 + 3sCRX + 1} \rightarrow \text{High pass filter}$$

Band stop filter (using state variable filter)

Page 7

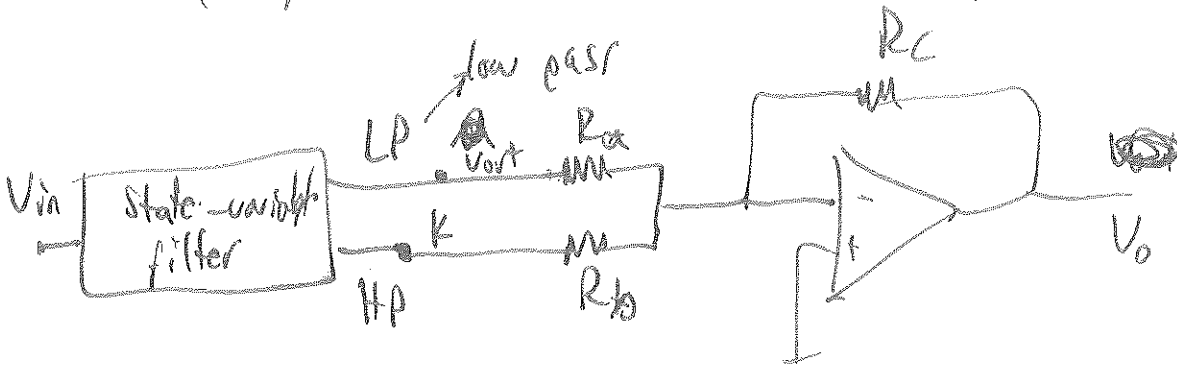

V_{out}

$$\frac{0 - V_{out}}{R_a} + \frac{V_{out} - 0}{R_b} = \frac{0 - V_o}{R_c}$$

$$V_o = -\frac{R_c}{R_a} V_{out} - \frac{R_c}{R_b} V_{out}$$

$$V_o = -\frac{R_c}{R_a} V_{out} - \frac{R_c}{R_b} k V_{out}$$

$$V_o = -\frac{R_c}{R_a} \left[\frac{V_{in}}{s^2 C^2 R^2 + 3sCRX + 1} \right] - \frac{R_c}{R_b} \left[\frac{-s^2 C^2 R^2}{s^2 C^2 R^2 + 3sCRX + 1} \right]$$

$$V_o = \frac{R_c}{R_a} \frac{V_{in}}{s^2 C^2 R^2 + 3sCRX + 1} + \frac{R_c}{R_b} \left[\frac{s^2 C^2 R^2 V_{in}}{s^2 C^2 R^2 + 3sCRX + 1} \right]$$

$$V_o = \frac{R_c R_b + R_c R_a s^2 C^2 R^2}{(R_a R_b) [s^2 C^2 R^2 + 3sCRX + 1]} V_{in}$$

$$V_o = \frac{R_c R_a C^2 R^2 \left[s^2 + \frac{R_c R_b}{R_c R_a C^2 R^2} \right]}{\left(\frac{R_a R_b}{C R} \right) \left[s^2 + \frac{3sX}{CR} + \frac{1}{C^2 R^2} \right]} V_{in}$$

$$V_o = \frac{R_c R_a}{R_b} \left[\frac{s^2 + \frac{R_b}{R_a C^2 R^2}}{s^2 + \frac{3sX}{CR} + \frac{1}{C^2 R^2}} \right] V_{in}$$

$$H(s) = \frac{V_o}{V_{in}} = \frac{R_c}{R_b} \left[\frac{s^2 + \frac{R_b}{R_a C^2 R^2}}{s^2 + \frac{3sX}{CR} + \frac{1}{C^2 R^2}} \right]$$


$$H(j\omega) = \frac{R_c}{R_b} \frac{\left[\frac{R_b}{R_a C^2 R^2} - \omega^2 \right]}{\left[\frac{1 - \omega^2}{C^2 R^2} \right] + \frac{3X j\omega}{CR}}$$

$$|H(j\omega)| = \frac{R_c}{R_b} \frac{\left| \frac{R_b}{R_a C^2 R^2} - \omega^2 \right|}{\sqrt{\left(\frac{1}{C^2 R^2} - \omega^2 \right)^2 + \left(\frac{3X\omega}{CR} \right)^2}}$$


$$|H(j\omega)| \Big|_{\omega=0} = \frac{R_c}{R_b} \frac{\overbrace{R_b}^{R_b}}{R_a C^2 R^2} = \frac{R_c}{R_a}$$

$$\lim_{\omega \rightarrow \infty} |H(j\omega)| = \frac{R_c}{R_b} //$$

$$\text{if } \omega = \sqrt{\frac{R_b}{R_a C^2 R^2}} \Rightarrow |H(j\omega)| = 0$$

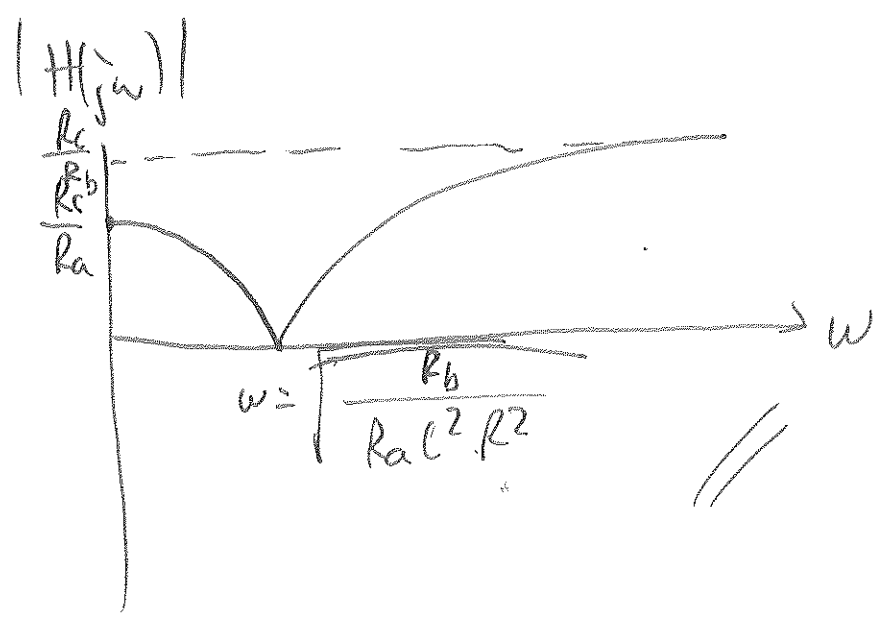

$$\text{if } R_a = R_b$$

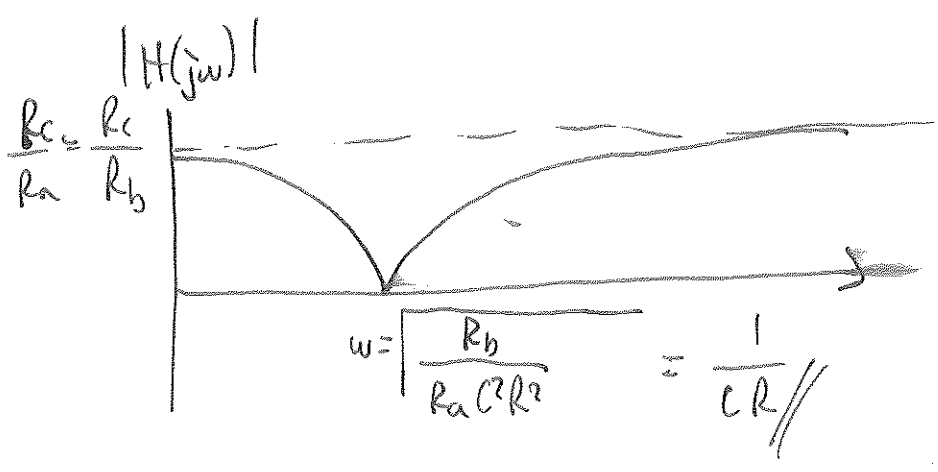

Band pass filter

$$\frac{M}{V_{in}} = \frac{sCR}{s^2 C^2 R^2 + 3sCR + 1}$$

$$\frac{\frac{s}{CR}}{s^2 + \frac{3sX}{CR} + \frac{1}{C^2 R^2}} = \frac{\omega_0^2}{s^2 + 2\zeta\omega_0 s + \omega_0^2}$$

$$\omega_0 = \frac{1}{CR} \quad \omega_0^2 = \frac{1}{C^2 R^2}$$

$$2\zeta\omega_0 = \frac{3X}{CR} \quad 2\zeta\omega_0 = 3X\omega_0$$

$$\zeta = \frac{3X}{2} \quad \zeta = \frac{3}{2} \left[\frac{R_6}{R_1 + R_6} \right] \rightarrow \text{damping ratio}$$

$$\omega_0 = \frac{1}{CR} \quad \omega_{c_1, c_2} = \frac{2\zeta\omega_0 \pm \sqrt{4\zeta^2\omega_0^2 - 4\omega_0^2}}{2}$$

$$\omega_{c_1, c_2} = \frac{3\omega_0 \pm \omega_0 \sqrt{3^2 - 1}}{2}$$

$$\omega_{c_1, c_2} = \frac{\frac{3X}{2}\omega_0 \pm \omega_0 \sqrt{\frac{9X^2}{4} - 1}}{2}$$

$$|\omega_{c_1} - \omega_{c_2}| \Rightarrow BW = \text{bandwidth} = \frac{3X}{2}\omega_0 + \omega_0 \sqrt{\frac{9X^2}{4} - 1}$$

$$BW = \frac{\frac{3X}{2}\omega_0 + \omega_0 \sqrt{\frac{9X^2}{4} - 1}}{2} - \frac{\frac{3X}{2}\omega_0 - \omega_0 \sqrt{\frac{9X^2}{4} - 1}}{2}$$

$$BW = \omega_0 \sqrt{\frac{9X^2}{4} - 1} \quad Q = \frac{\omega_0}{BW} = \frac{\omega_0}{\omega_0 \sqrt{\frac{9X^2}{4} - 1}} = \frac{2}{2.3X} = \frac{1}{3} \left[\frac{R_1}{R_1 + R_6} \right]$$

$$R = \frac{1}{3} \frac{R_5 + R_6}{R_6} = \frac{1}{3} \left[\frac{R_5}{R_6} + 1 \right] = \frac{1}{3} \left[\frac{R_5}{R_6} + 1 \right]$$