

Name _____
Date _____
Instructor _____

EXPERIMENT
28

Linear Op-Amp Circuits

OBJECTIVE

To measure DC and AC voltages in linear op-amp circuits.

EQUIPMENT REQUIRED

Instruments

Oscilloscope
DMM
Function generator
DC power supply

Components

Resistors

(1) 20-k Ω
(3) 100-k Ω

ICs

(1) 741 Op-amp

EQUIPMENT ISSUED

Item	Laboratory serial no.
DC power supply	
Function generator	
Oscilloscope	
DMM	

RÉSUMÉ OF THEORY

The op-amp is a very high gain amplifier with inverting and noninverting inputs. It can be used to provide a much smaller but exact gain set by external resistors or to sum more than one input, each input having a desired voltage gain.

As an inverting amplifier the resistors are connected to the inverting input as shown in Fig. 28.1 with output voltage

$$V_o = -\frac{R_o}{R_i} V_i \tag{28.1}$$

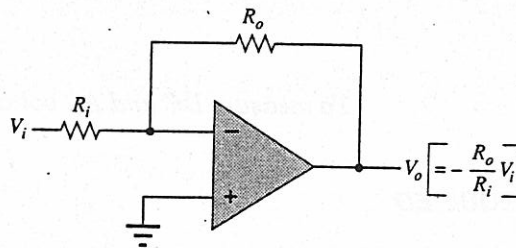


Figure 28-1

A noninverting amplifier is provided by the circuit of Fig. 28.2 with output voltage given by

$$V_o = \left(1 + \frac{R_o}{R_i}\right) V_i \tag{28.2}$$

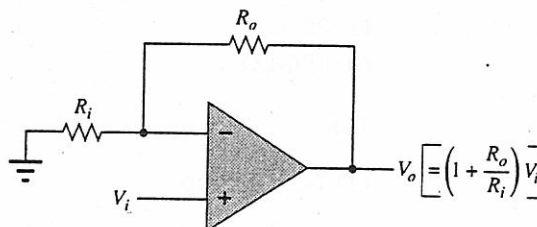


Figure 28-2

Connecting the output back to the inverting input as in Fig. 28.3 provides a gain of exactly unity:

$$V_o = V_i \tag{28.3}$$

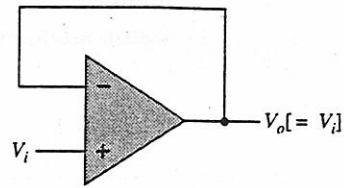


Figure 28-3

More than one input can be connected through separate resistors as shown in Fig. 28.4, with the output voltage then

$$V_o = -\left(\frac{R_o}{R_1} V_1 + \frac{R_o}{R_2} V_2\right) \quad (28.4)$$

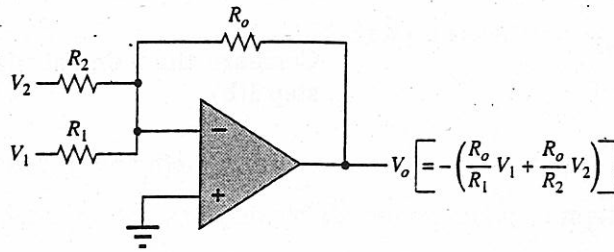


Figure 28-4

PROCEDURE

Part 1. Inverting Amplifier

- a. Calculate the voltage gain for the amplifier circuit of Fig. 28.5.

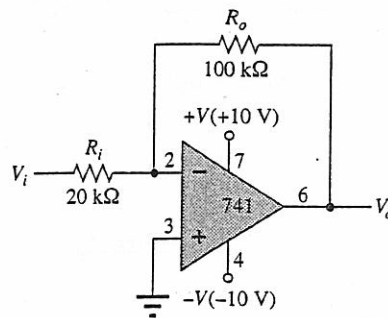


Figure 28-5

V_o/V_i (calculated) = _____

- b. Construct the circuit of Fig. 28.5. (Measure and record resistor values in Fig. 28.5.) Apply an input of $V_i = 1$ V, rms ($f = 10$ kHz). Using a DMM measure and record the output voltage.

Calculated voltage gain using measured values: V_o (measured) = 5

Compare the gain calculated in step 1(a) with that measured in step 1(b). $A_v =$ 5


- c. Replace R_1 with a 100-k Ω resistor. Calculate V_o/V_i .

For input of $V_i = 1$ V, rms measure and record V_o . V_o/V_i (calculated) = _____

Calculate A_v . V_o (measured) = _____

Compare the calculated and measured values of the voltage gain. $A_v =$ _____

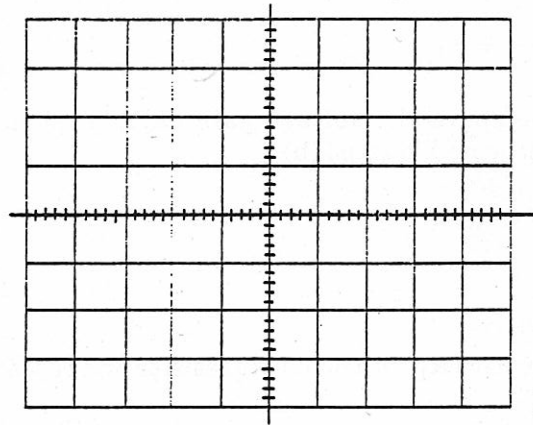- d. Using the oscilloscope, observe and sketch the input and output waveforms in Fig. 28.6.



Vertical sensitivity = _____
 Horizontal sensitivity = _____

Figure 28-6

Part 2. Noninverting Amplifier

- a. Calculate the voltage gain of the noninverting amplifier in Fig. 28.7.

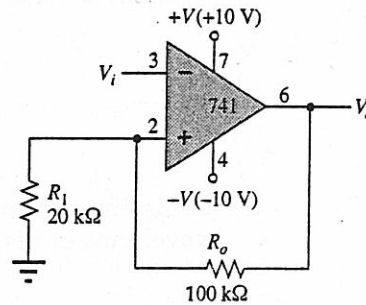


Figure 28-7

A_v (calculated) = _____

- b. Construct the circuit of Fig. 28.7. Apply an input of $V_i = 1$ V, rms ($f = 10$ kHz). Using a DMM, measure and record the output voltage.

V_o (measured) = _____

Calculate the voltage gain of the circuit using measured voltages.

$$V_o/V_i = \underline{\hspace{2cm}}$$

Compare the voltage gain calculated in step 2(a) with that measured in step 2(b).

- c. Replace R_1 with a 100-k Ω resistor and repeat steps 2(a) and 2(b).

$$A_v \text{ (calculated)} = \underline{\hspace{2cm}}$$

$$V_o \text{ (measured)} = \underline{\hspace{2cm}}$$

$$V_o/V_i = \underline{\hspace{2cm}}$$

Compare the calculated voltage gain with that measured.

- d. Using the oscilloscope, observe and sketch the input and output waveforms in Fig. 28.8.

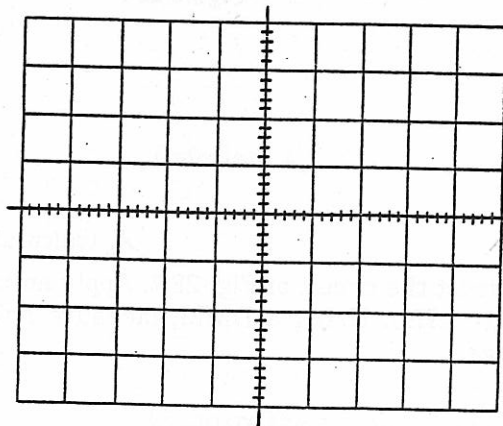


Figure 28-8

$$\text{Vertical sensitivity} = \underline{\hspace{2cm}}$$

$$\text{Horizontal sensitivity} = \underline{\hspace{2cm}}$$

Part 3. Unity-Gain Follower

- a. Construct the circuit of Fig. 28.9. Apply an input signal of $V_i = 2\text{ V}$, rms ($f = 10\text{ kHz}$). Using a DMM, measure and record the input and output voltages.

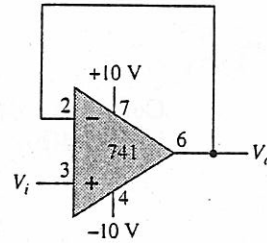


Figure 28-9

V_i (measured) = _____
 V_o (measured) = _____

Compare the circuit voltage gain, V_o/V_i with the theoretical unity gain.

Part 4. Summing Amplifier

- a. Calculate the output voltage for the circuit of Fig. 28.10 (see Fig. 28.4) with inputs of $V_1 = V_2 = 1\text{ V}$, rms.

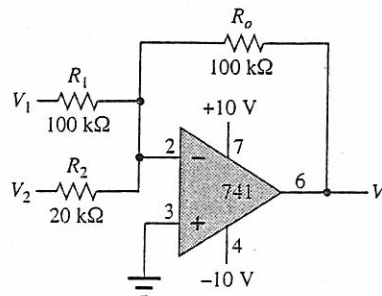


Figure 28-10

V_o (calculated) = _____

- b. Construct the circuit of Fig. 28.10. Apply inputs of $V_1 = V_2 = 1\text{ V}$, rms ($f = 10\text{ kHz}$). Measure and record the output voltage.

$$V_o \text{ (measured)} = \underline{\hspace{2cm}}$$

Compare output voltage calculated in step 4(a) and that measured in step 4(b).

- c. Change R_2 to $100\text{ k}\Omega$. Repeat steps 4(a) and 4(b).

$$\begin{aligned} V_o \text{ (calculated)} &= \underline{\hspace{2cm}} \\ V_o \text{ (measured)} &= \underline{\hspace{2cm}} \end{aligned}$$

Compare the calculated output voltage with that measured.