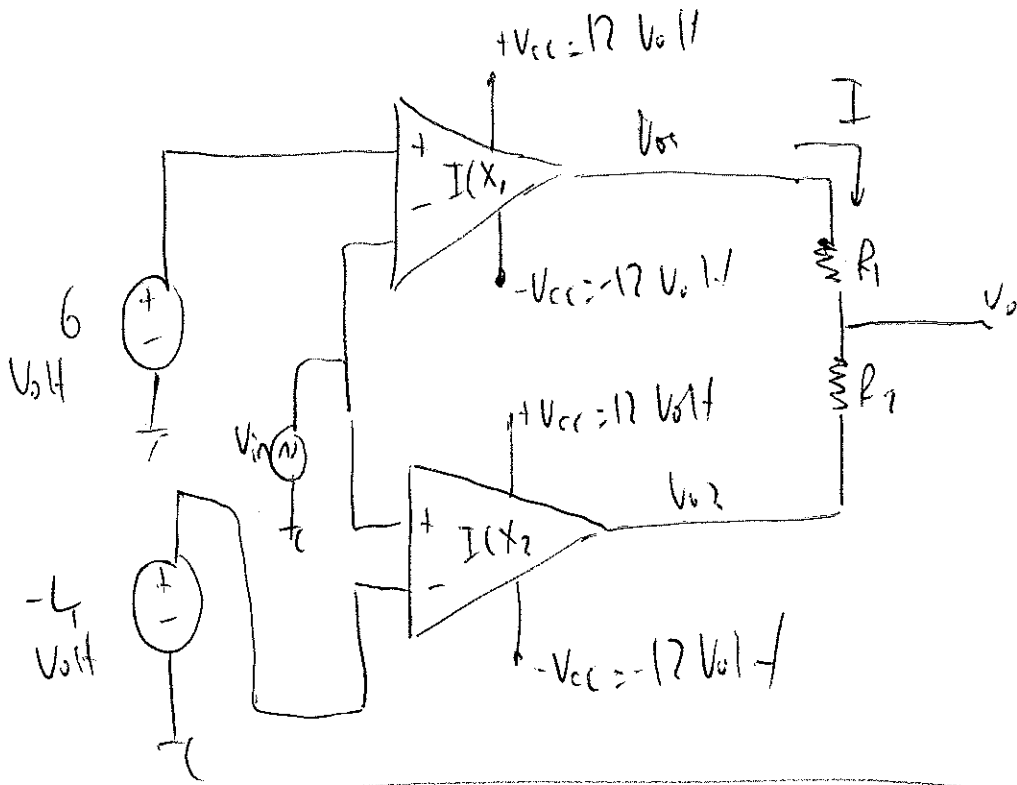


Q1



For $I(X_1)$ if $6 \geq V_{in} \Rightarrow V_{o1} = 2(V_{in} - 6)$
 if $6 < V_{in} \Rightarrow V_{o1} = 3(6 - V_{in})$
 V_{o1} saturates at $+12$ and -12 volt

1 point

For $I(X_2)$ if $V_{in} \geq -4 \Rightarrow V_{o2} = 2(-4 - V_{in})$
 if $V_{in} < -4 \Rightarrow V_{o2} = 3(V_{in} - (-4)) = 3(V_{in} + 4)$
 V_{o2} saturates at $+12$ and -12 volt

1 point

if $V_{in} = 0$ $V_{o1} = -12$ volt (saturates)
 if $V_{in} = 10$ $V_{o1} = -12$ volt
~~if $V_{in} = 0$ $V_{o2} = 12$ volt (saturates)~~

if $V_{in} = -8$ $V_{o2} = -12$ volt (saturates)
 if $V_{in} = 2$ volt $V_{o2} = -12$ volt (saturates)

important points $10, 6, 2, 0, -4, -8$

3 point

$$V_{o1} = 3(6 - V_{in})$$

if $V_{in} > 10$ $V_{o1} = -12 \text{ Volt}$ $V_{o2} = -12 \text{ Volt}$

$$I = \frac{V_{o1} - V_{o2}}{R_1 + R_2} = \frac{-12 - (-12)}{1000 + 2000} = 0 \text{ Ampere}$$

(L plug)

$$V_o = V_{o1} - I R_1 = -12 - 0 \times 1000 = -12 \text{ Volt}$$

if $6 < V_{in} < 10$ $V_{o1} = 3(6 - V_{in})$ $V_{o2} = -12 \text{ Volt}$

$$I = \frac{3(6 - V_{in}) - (-12)}{3000} = \frac{30 - 3V_{in}}{3000} \text{ Ampere}$$

(2 plug)

$$V_o = V_{o1} - I R_1 = 3(6 - V_{in}) - \frac{30 - 3V_{in}}{3000} \times 1000 = 18 - 3V_{in} - 10 + V_{in} = 8 - 2V_{in}$$

if $2 < V_{in} \leq 6$

$$V_{o1} = 2(V_{in} - 6)$$

$$V_{o2} = -12 \text{ Volt}$$

(2 plug)

$$I = \frac{2(V_{in} - 6) - (-12)}{3000} = \frac{2V_{in}}{3000} \text{ Ampere}$$

$$V_o = V_{o1} - I R_1 = 2(V_{in} - 6) - \frac{2V_{in}}{3000} \times 1000$$

$$= 2V_{in} - 12 - \frac{2V_{in}}{3} = \frac{4V_{in}}{3} - 12 = \frac{4V_{in} - 36}{3} \text{ Volt}$$

$0 < V_{in} < 2$ $V_{o1} = 2(V_{in} - 6)$ $V_{o2} = 2(-4 - V_{in})$

(2 plug)

$$I = \frac{V_{o1} - V_{o2}}{3000} = \frac{2V_{in} - 12 - (-8 - 2V_{in})}{3000} = \frac{-4 + 4V_{in}}{3000} \text{ Ampere}$$

$$V_o = V_{o1} - I R_1 = 2V_{in} - 12 - \left(\frac{-4 + 4V_{in}}{3000}\right) \times 1000 \rightarrow V_o = 2V_{in} - 12 + \frac{4}{3} - \frac{4V_{in}}{3} = \frac{2V_{in} - 32}{3}$$

$-4 < V_{in} < 0$ $V_{o1} = -12$ $V_{o2} = 2(-4 - V_{in})$

(2 plug)

$$I = \frac{V_{o1} - V_{o2}}{3000} = \frac{-12 - (8 + 2V_{in})}{3000} = \frac{-4 - 2V_{in}}{3000}$$

$$V_o = V_{o1} - I R_1 = -12 - \left(\frac{-4 - 2V_{in}}{3000}\right) \times 1000 = -12 + \frac{4}{3} + \frac{2V_{in}}{3} = \frac{-32 - 2V_{in}}{3}$$

$$-8 < V_{in} < -4 \quad V_{o1} = -12 \quad V_{o2} = 3(V_{in}/4)$$

$$I = \frac{V_{o1} - V_{o2}}{3000} = \frac{-12 - 3V_{in}/4 - 12}{3000} = \frac{-24 - 3V_{in}}{3000} \text{ Ampere}$$

$$V_o = V_{o1} - I R_1 = -12 - \left(\frac{-24 - 3V_{in}}{3000} \right) 1000 = -12 + \frac{24}{3} + \frac{3V_{in}}{3}$$

$$= -4 + V_{in} \text{ Volt}$$

(2 points)


$$V_{in} < -8$$

$$V_{o1} = -12 \quad V_{o2} = -12$$


$$I = \frac{V_{o1} - V_{o2}}{3000} = \frac{-12 - (-12)}{3000} = 0 \text{ Ampere}$$

(2 points)
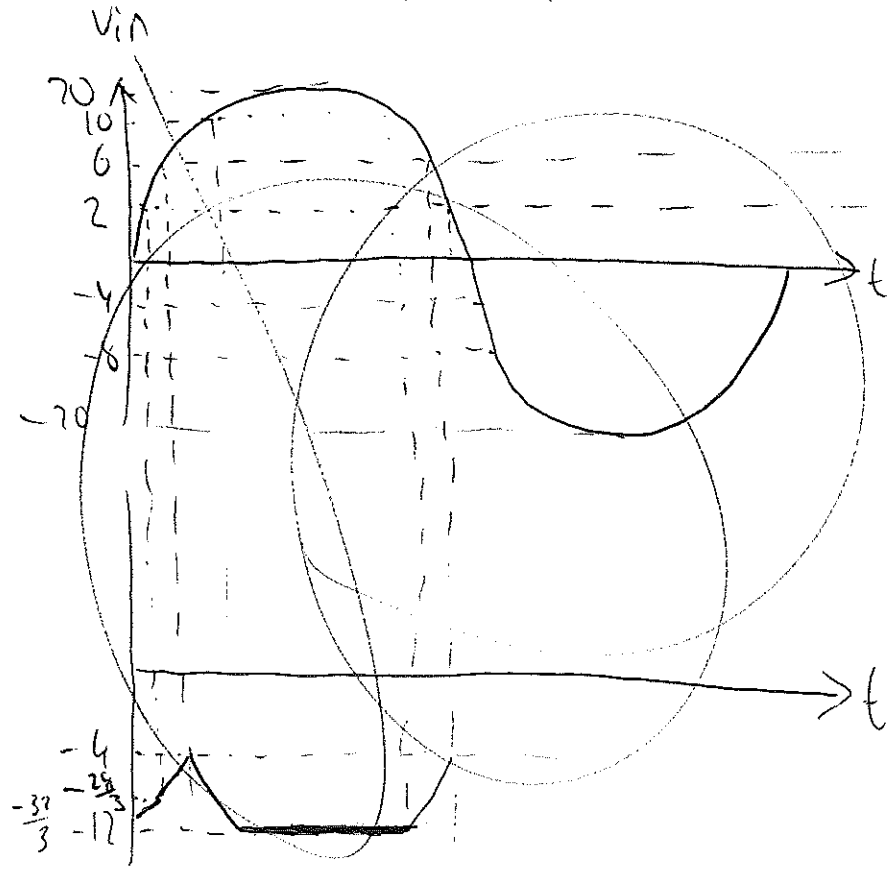
$$V_o = V_{o1} - I R_1 = -12 - 0 \times 1000 = -12 \text{ Volt}$$



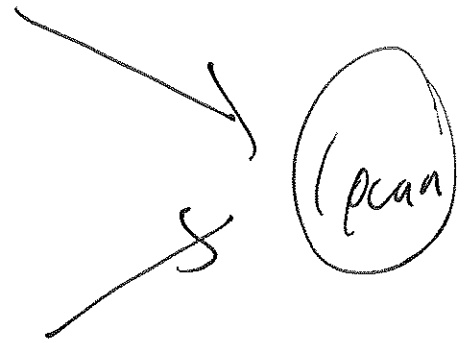
$$V_o = \begin{cases} -12, & v_{in} > 10 \\ 8 - 2v_{in}, & 6 < v_{in} < 10 \\ \frac{4v_{in} - 36}{3}, & 2 < v_{in} < 6 \\ \frac{2v_{in} - 32}{3}, & 0 < v_{in} < 2 \\ \frac{-32 - 2v_{in}}{3}, & -4 < v_{in} < 0 \\ -4v_{in}, & -8 < v_{in} < -4 \\ -12, & v_{in} < -8 \end{cases} \text{ in Volt}$$



$$I = \begin{cases} 0, & v_{in} > 10 \\ \frac{36 - 3v_{in}}{3000}, & 6 < v_{in} < 10 \\ \frac{2v_{in} - 36}{3000}, & 2 < v_{in} < 6 \\ \frac{-4v_{in} - 32}{3000}, & 0 < v_{in} < 2 \\ \frac{-4 + 2v_{in}}{3000}, & -4 < v_{in} < 0 \\ \frac{-24 - 3v_{in}}{3000}, & -8 < v_{in} < -4 \\ 0, & v_{in} < -8 \end{cases} \text{ in Ampere}$$


(b)

25
PUN

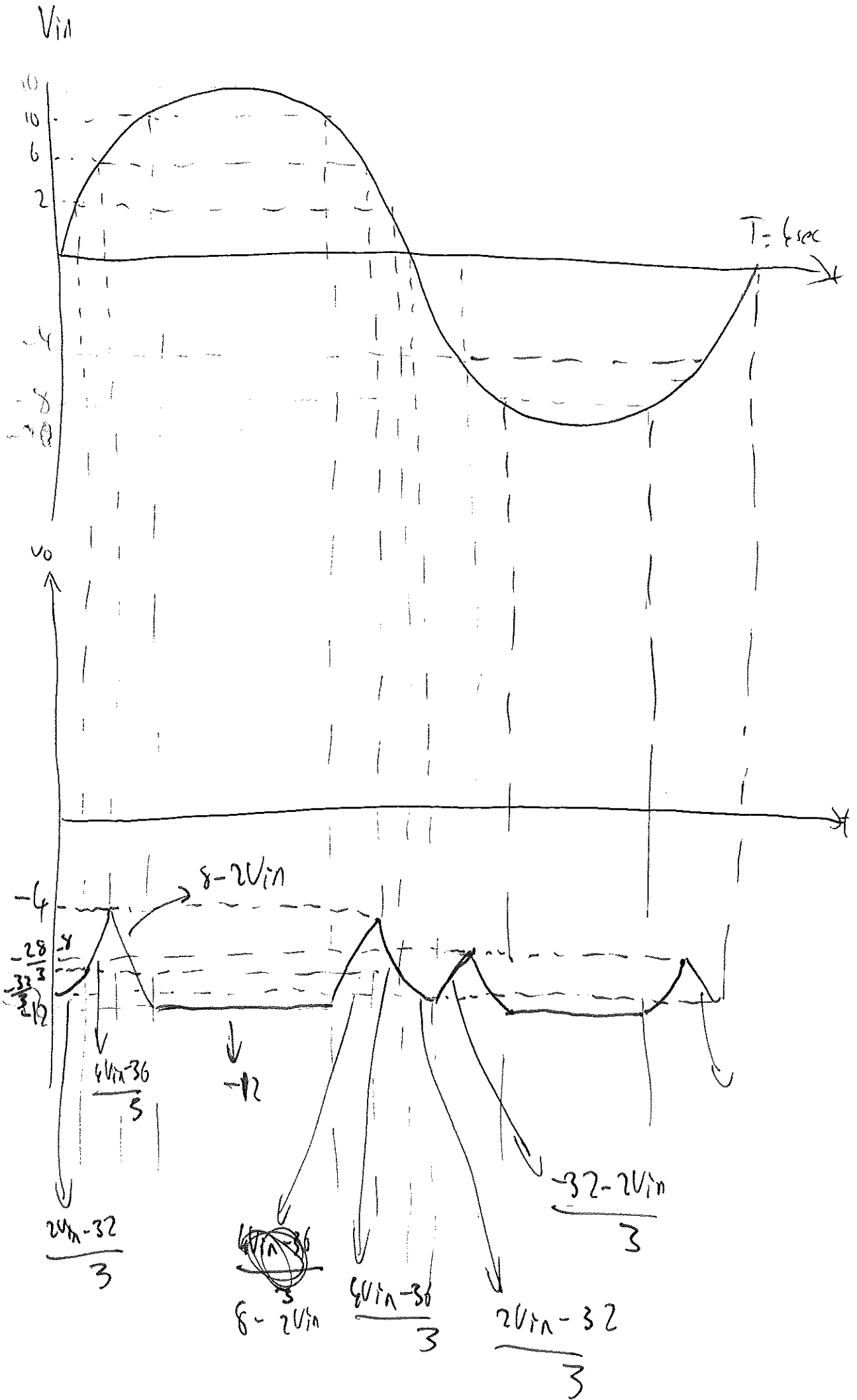


6

25 puan

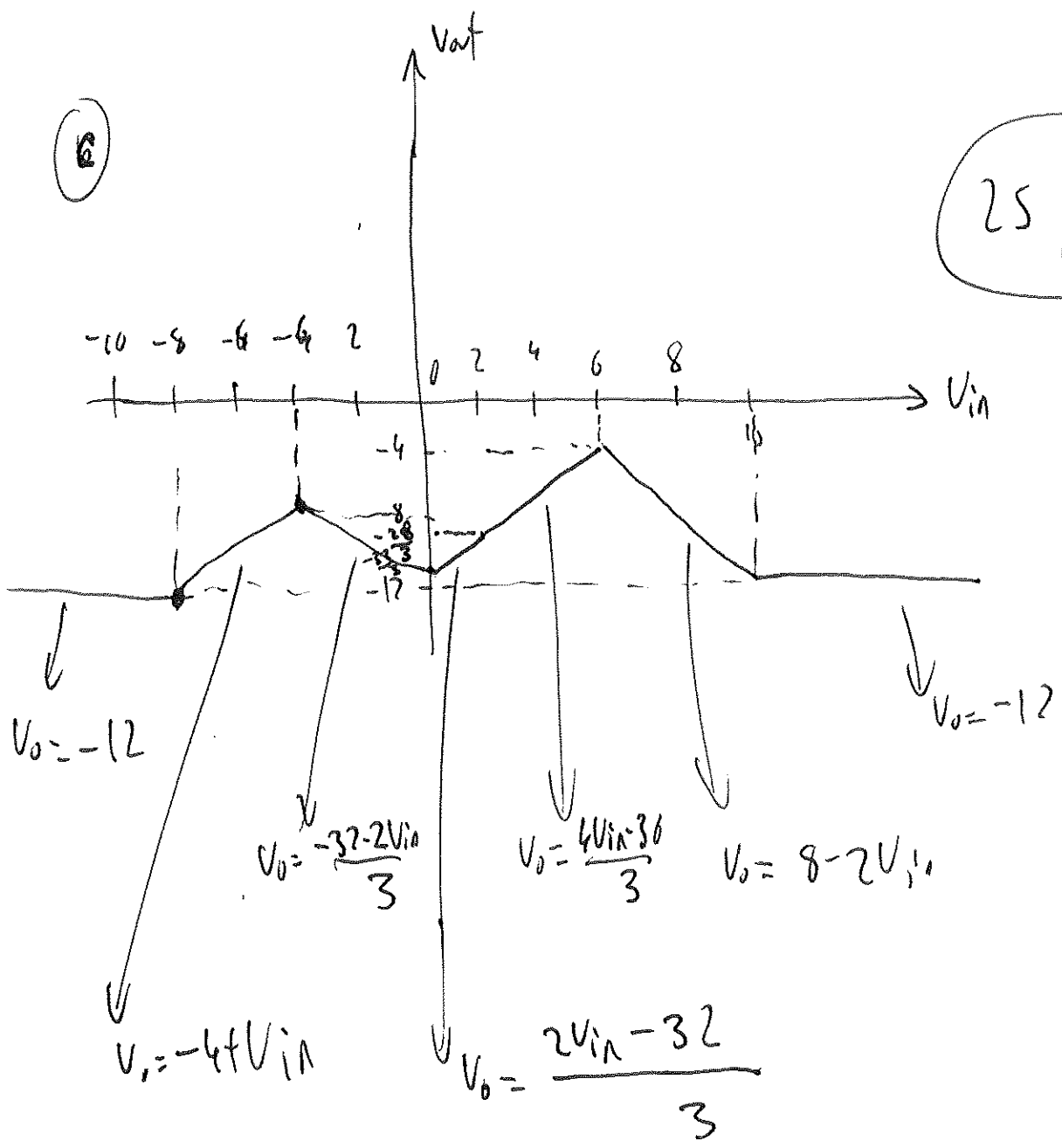

Q2

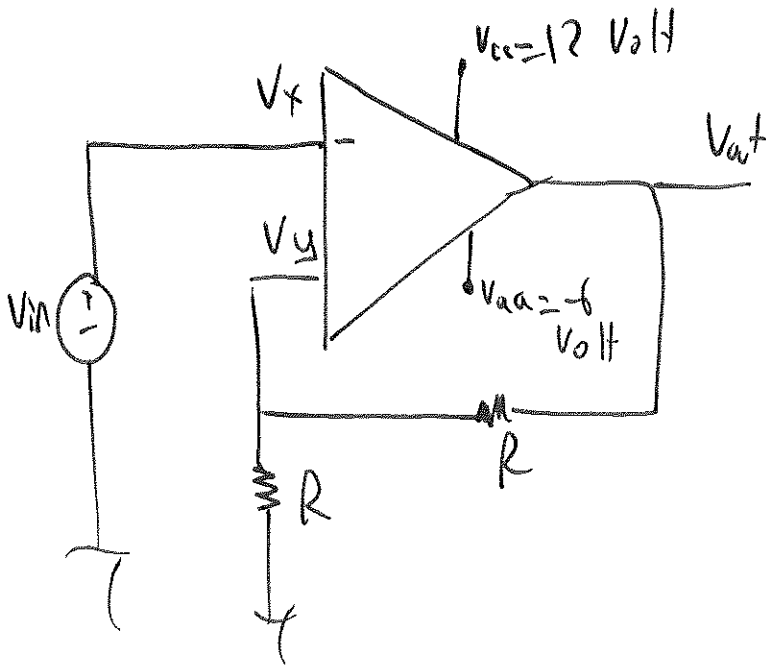

$$V_{yf} = \frac{V_{out}}{2R} \times R$$

puan $V_y = \frac{V_{out}}{2}$

$$V_{out} = 2V_y$$

Let $V_x = V_{in} > V_y \Rightarrow V_{out} = \frac{1}{2} [V_{aa} + (V_y - V_{in})]$

$$V_{out} = \frac{1}{2} \left[-6 + \frac{V_{out}}{2} - V_{in} \right]$$

$$V_{out} = -3 + \frac{V_{out}}{4} - \frac{V_{in}}{2}$$

$$\frac{3V_{out}}{4} = -3 - \frac{V_{in}}{2}$$

puan

$$V_{out} = -4 - \frac{2V_{in}}{3} *$$

Let $V_x = V_{in} < V_y$ $V_{out} = \frac{1}{2} [V_{cc} + (V_y - V_{in})]$


$$V_{out} = \frac{1}{2} \left[12 + \frac{V_{out}}{2} - V_{in} \right]$$

$$V_{out} = 6 + \frac{V_{out}}{4} - \frac{V_{in}}{2} *$$

puan

$$\frac{3V_{out}}{4} = 6 - \frac{V_{in}}{2} \Rightarrow V_{out} = 8 - \frac{2V_{in}}{3}$$

Draw * and **

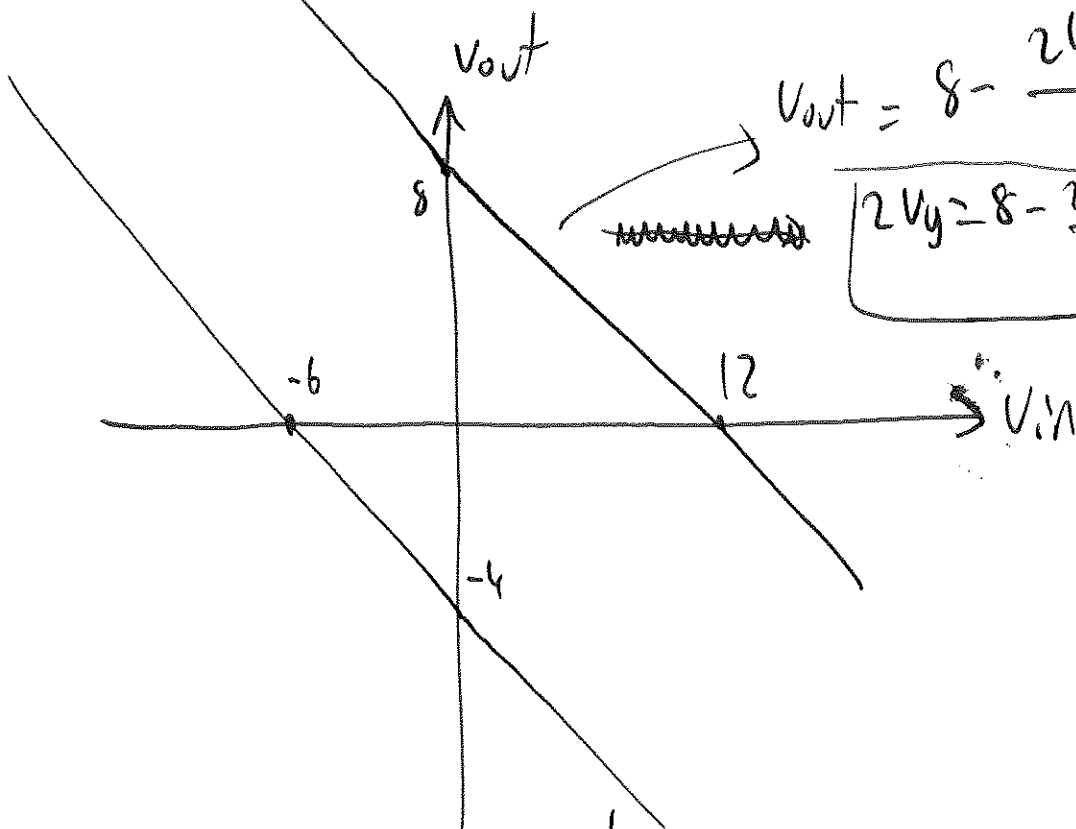

$$v_{out} = 8 - \frac{2v_{in}}{3}$$

$$2v_y = 8 - \frac{2v_{in}}{3}$$

$$v_y = \frac{v_{out}}{2}$$

$$v_{out} = -4 - \frac{2v_{in}}{3} \Rightarrow 2v_y = -4 - \frac{2v_{in}}{3}$$

Find the points on these lines where $v_{in} = v_x = v_y = \frac{v_{out}}{2}$

$$2v_y = 8 - \frac{2v_{in}}{3} \quad v_y = v_{in} \rightarrow 2v_{in} = 8 - \frac{2v_{in}}{3} \quad \frac{8v_{in}}{3} = 8 \quad v_{in} = 3$$

if $v_{in} = 3$ $v_y = 3$ $v_{out} = 6$ critical point

3 point

$$2v_y = -4 - \frac{2v_{in}}{3} \quad v_y = v_{in} \rightarrow 2v_{in} = -4 - \frac{2v_{in}}{3} \quad \frac{8v_{in}}{3} = -4 \quad v_{in} = -1.5 \text{ Volt}$$

if $v_{in} = -1.5$ $v_y = -1.5$ $v_{out} = -3$

3 point

Let $V_{in} = -12$ and increase V_{in} until $V_{in} = 3$

if $-12 < V_{in} < 3$ and $V_{in} \uparrow$ $V_{out} = 8 - \frac{2V_{in}}{3}$

(Ques) when $V_{in} = 3$ $V_{out} = 6 \Rightarrow V_y = 3$
after this point $V_{in} > V_y$ then V_{out} jumps to
 $V_{out} = -4 - \frac{2 \times 3}{3} = -6$ Volt

Let $V_{in} = 3$ and increase V_{in} until $V_{in} = 12$

(Ques) if $3 < V_{in} < 12$ and $V_{in} \uparrow$ $V_{out} = -4 - \frac{2V_{in}}{3}$

when $V_{in} = 3$ $V_{out} = -6 \Rightarrow V_y = -3$

$V_{in} > V_y$ then V_{out} is

$$V_{out} = -4 - \frac{2V_{in}}{3}$$

Let $V_{in} = 12$ and decrease V_{in} until $V_{in} = -1.5$

(Ques) if $4.5 < V_{in} < 12$ and $V_{in} \downarrow$ $V_{out} = -4 - \frac{2V_{in}}{3}$

when $V_{in} = -1.5$ $V_{out} = -3$ $V_y = -1.5$

after this point $V_{in} < V_y$ then V_{out} jumps to

$$V_{out} = 8 - \frac{2 \times (-1.5)}{3} = 9 \text{ Volt}$$

Let $V_{in} = -1.5$ and decrease V_{in} until $V_{in} = -12$

(Ques) if $-12 < V_{in} < -1.5$ and $V_{in} \downarrow$ $V_{out} = 8 - \frac{2V_{in}}{3}$

when $V_{in} = -1.5$ $V_{out} = 9$ $V_y = 4.5$

$V_{in} < V_y$ then V_{out} is
 $V_{out} = 8 - \frac{2V_{in}}{3}$

