
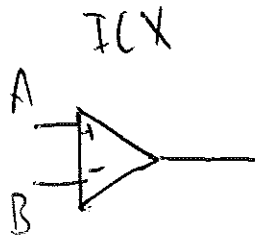


Q1

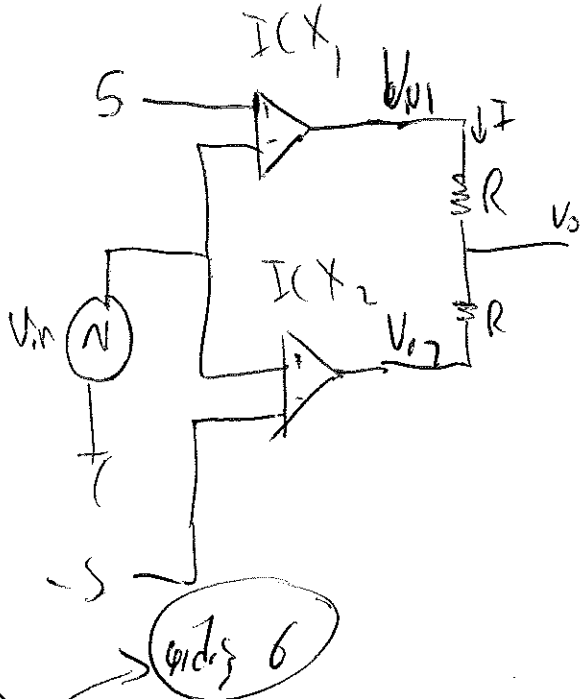

$A > B \quad (A - B)$

$B > A \quad (B - A)$



$V_{in} = 10 \sin(2\pi f t)$

$f = \text{0.25 Hertz}$

$R = 1000 \Omega$

~~order 6~~

a) for ICX₁ if $V_{in} > 5$ $V_{01} = V_{in} - 5$
 ICX₂ if $V_{in} > 5$ $V_{02} = V_{in} - (-5) = V_{in} + 5$
 $I = \frac{V_{01} - (+V_{02})}{2 \times 1000} = \frac{V_{01} - V_{02}}{2R} = \frac{(V_{in} - 5) - (V_{in} + 5)}{2 \times 1000} = \frac{-10}{2} = -5 \text{ Amper}$

$V_0 = V_{01} - RI = V_{in} - 5 - 1 \times (-5) = V_{in}$

for ICX₁ if $-5 < V_{in} < 5$ $V_{01} = 5 - V_{in}$
 ICX₂ if $-5 < V_{in} < 5$ $V_{02} = V_{in} - (-5) = V_{in} + 5$
 $I = \frac{V_{01} - (V_{02})}{2R} = \frac{5 - V_{in} - (V_{in} + 5)}{2 \times 1000} = \frac{-2V_{in}}{2 \times 1000} = -\frac{V_{in}}{1000} \text{ Amper}$
 $V_0 = V_{01} - RI = 5 - V_{in} - 1 \cdot (-\frac{V_{in}}{1000}) = 5 - V_{in} + \frac{V_{in}}{1000}$


for ICX₁ if $V_{in} < 0$ $V_{o1} = V_{in} - V_{in}$
 ICX₂ if $V_{in} > 0$ $V_{o2} = (-V_{in} - V_{in})$


$I = \frac{V_{o1} - V_{o2}}{2R} = \frac{V_{in} - V_{in} - (-V_{in} - V_{in})}{2 \times 1} = \frac{S - V_{in} + S + V_{in}}{2} = \frac{10}{2} = 5A$

$V_o = V_{o1} - R I = S - V_{in} - 1 \times 5 = -V_{in}$

$V_o(s) = \begin{cases} V_{in}, & V_{in} > 0 \\ S, & -S < V_{in} < S \\ -V_{in}, & V_{in} < -S \end{cases}$
$I(s) = \begin{cases} -S, & V_{in} > S \\ -V_{in}, & -S < V_{in} < S \\ S, & V_{in} < -S \end{cases}$

(b)

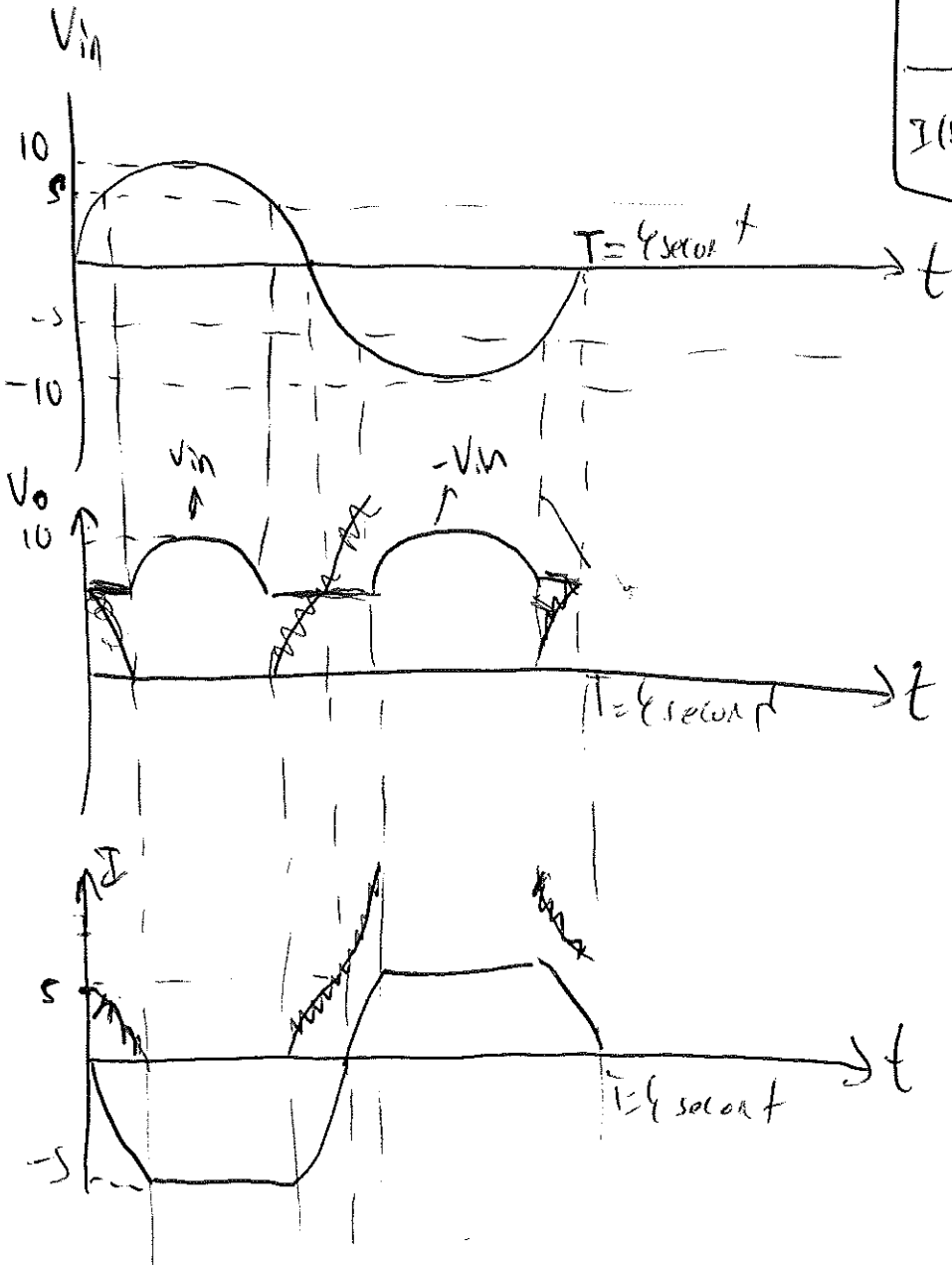


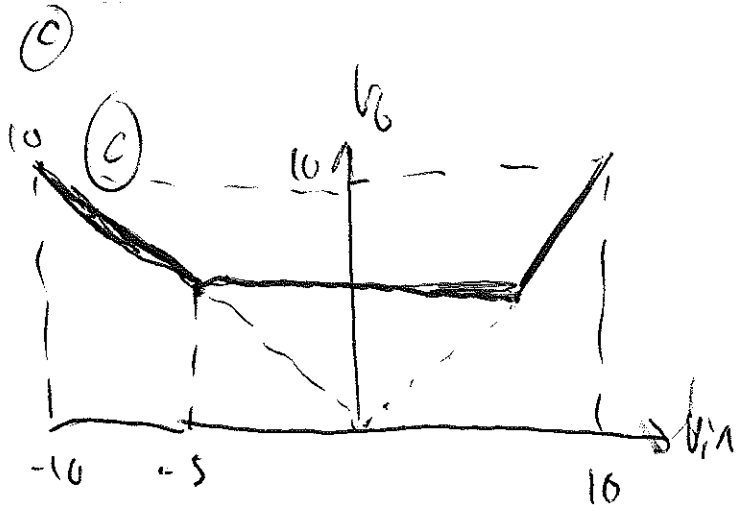


Q2

(a, b) → Gids 8 puan


Grafiçiler
 (a) → 4 puan
 b → 4 puan

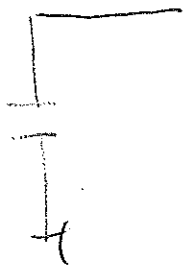

$V_{cc} = 12 \text{ Volt}$

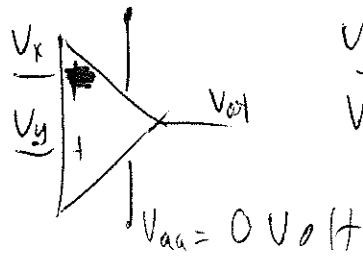

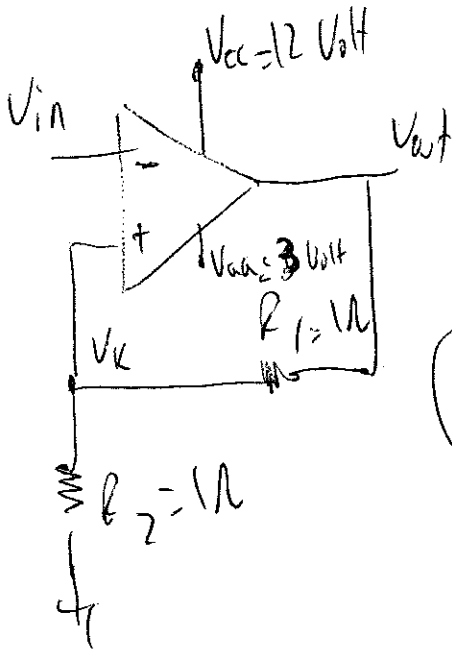$V_y > V_x \Rightarrow V_{out} = V_{sat}$
 $V_x > V_y \Rightarrow V_{out} = -V_{sat}$



$V_{in} = 10 \sin(2\pi ft)$ $f = \frac{1}{4} \text{ Herz}$



region (1) Let $0 < V_{in} < 6$ and $V_{out} = 12 \text{ Volt}$ $V_c = 6 \text{ Volt}$
 $V_c > V_{in} \Rightarrow V_{out} = 12$ remains unchange



region (2) = 2 Let $V_{in} \geq 6$ and $V_{out} = 12 \text{ Volt} \Rightarrow V_c = \frac{V_{out}}{R_1 R_2} R_2 = \frac{12}{2} \times 1 = 6 \text{ Volt}$
 $V_{in} > V_c$


then $V_{out} = 3 \text{ Volt}$ change P $\Rightarrow V_c = \frac{V_{out}}{R_1 R_2} R_2 = \frac{3}{2} \times 1 = 1.5 \text{ Volt}$ change

region (3) = 3 Let $1.5 \leq V_{in} < 6$ and $V_{out} = 3 \text{ Volt} \Rightarrow V_c = 1.5 \text{ Volt}$ $V_{in} > V_c$
 then $V_{out} = 3 \text{ Volt}$ unchange

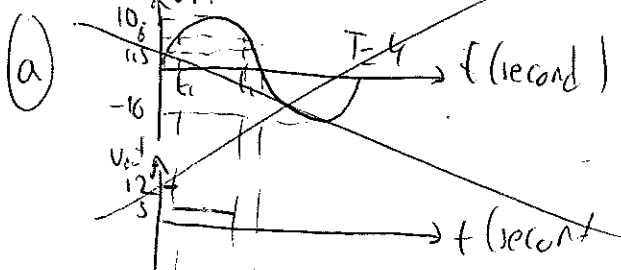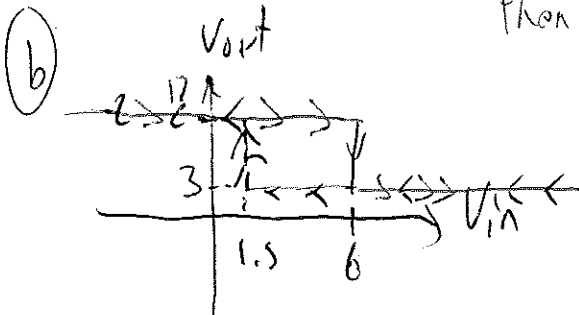(4) Let $1.5 < V_{in}$ and $V_{out} = 3 \Rightarrow V_c = 1.5 \text{ Volt}$ $V_{in} < V_c$
 then $V_{out} = 12 \text{ Volt} \Rightarrow V_c = 6 \text{ Volt}$



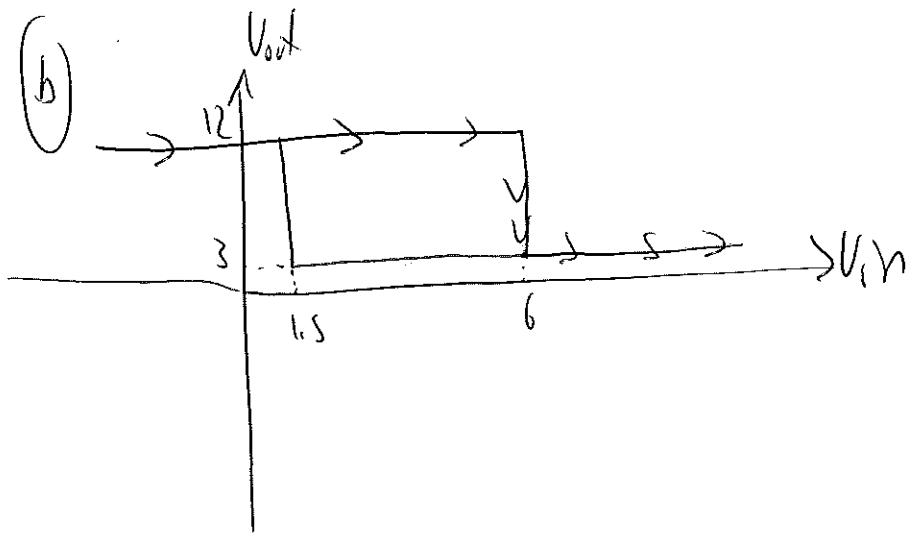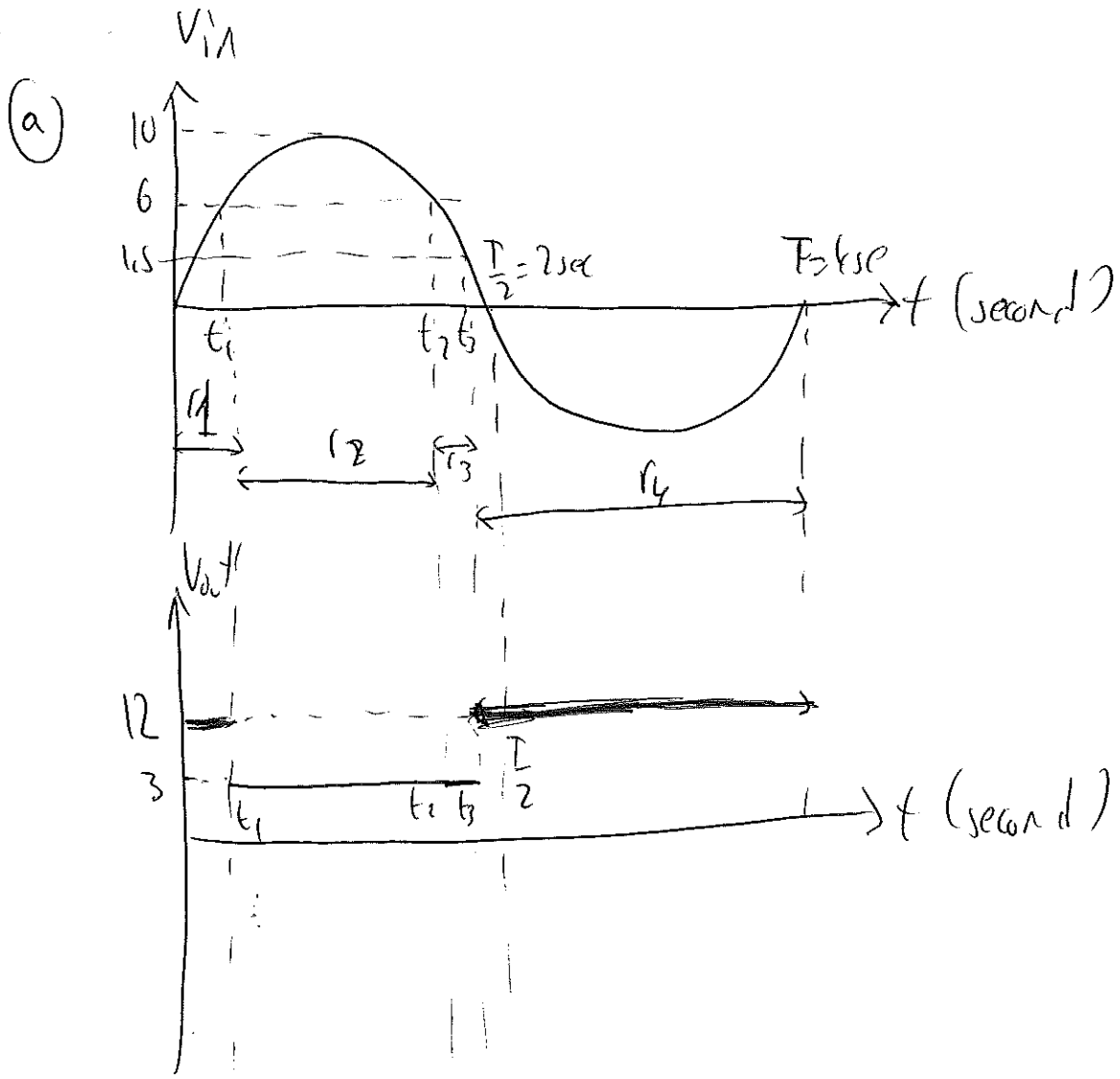

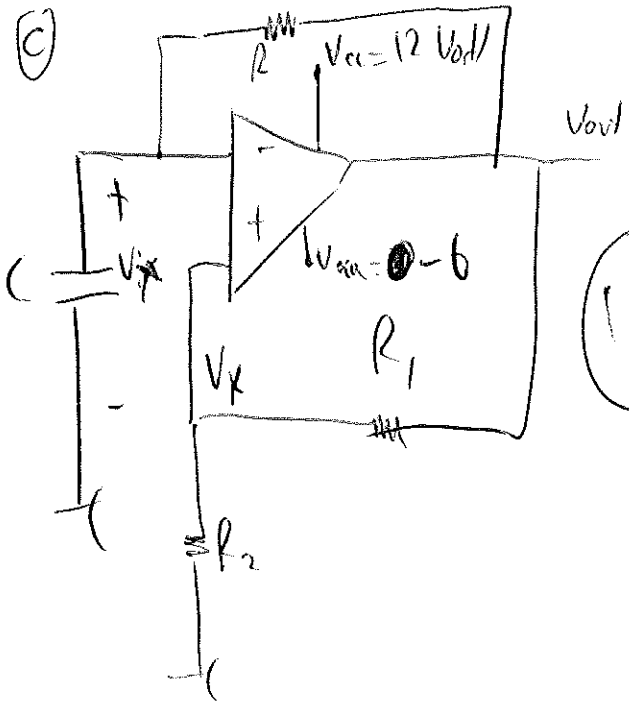

$$C \frac{dV_x}{dt} + \frac{V_x - V_{out}}{R} = 0$$

(pure) Limits of V_{out} 12 Volt and 6 Volt

V_x will oscillate between 6 Volt and -3 Volt

Let $V_{out} = 12$ Volt $V_x = 6$ Volt $V_x = -3$ Volt (initial condition)


$$C \frac{dV_x}{dt} + \frac{V_x - V_{out}}{R} = 0 \quad R = 1 \Omega \quad C = 1 \text{ F}$$

$$\frac{dV_x}{dt} + V_x = 12 \quad V_x(0) = -3 \text{ Volt} \quad (V_x \text{ should increase until it becomes } V_x = 6 \text{ Volt})$$

$$V_x = 12 + k e^{-t} \quad V_x(0) = -3 = 12 + k e^0 \quad k = -15$$

$$V_x = 12 - 15 e^{-t} \quad \text{let } t = t_m \quad V_x(t_m) = 6 = 12 - 15 e^{-t_m}$$
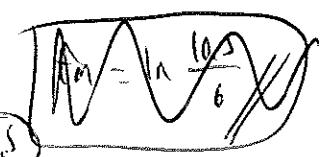
$$15 e^{-t_m} = 6 \quad 2.5 = e^{t_m} \quad t_m = 1.7 \text{ s}$$



When $t = t_m$ V_x becomes 6 Volt $\Rightarrow V_{out} = -6$ Volt $V_x = 3$ Volt

$$C \frac{dV_x}{dt} + \frac{V_x - V_{out}}{R} = 0 \quad R = 1 \Omega \quad C = 1 \text{ F}$$

$$\frac{dV_x}{dt} + V_x = -6 \quad V_x(t_m) = 6 \text{ Volt}$$

$$V_x = -6 + k e^{-(t-t_m)} \quad V_x(t_m) = 6 = -6 + k e^0 \quad k = 12 \quad V_x(t) = -6 + 12 e^{-(t-t_m)}$$

$$V_x(t_m) = 3 + 3 = 6$$

$$V_x(t) = 1.5 \text{ Volt} = 3 + 3e^{-(t-t_m)}$$

$$1.5 = 3 + 3e^{-(t-t_m)}$$

Spesifikasi

$$\frac{dV_x}{dt} + V_x = -6, \quad V_x(t_m) = 6 \text{ Volt}$$

$$V_x(t) = -6 + M e^{-(t-t_m)}$$

$$V_x(t_m) = 6 = -6 + M e^{-(t_m-t_m)}$$

$$12 = M$$

$$V_x(t) = -6 + 12 e^{-(t-t_m)}$$

$$V_x(t_k) = -3 = -6 + 12 e^{-(t_k-t_m)}$$



$$3 = 12 e^{-(t_k-t_m)}$$

$$e^{-(t_k-t_m)} = \frac{1}{4}$$

(1 poin)


$$t_k - t_m = \ln 4$$

$$t_k = \ln 4 + \ln 2.5 = \ln 10$$

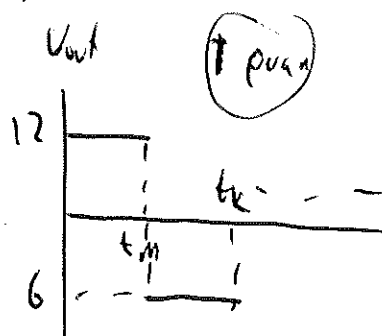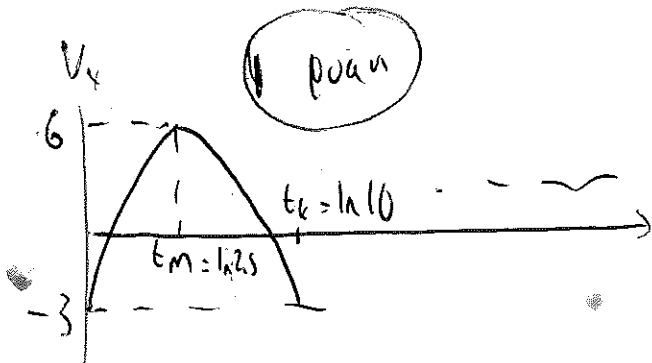


Q.3 :

(2)

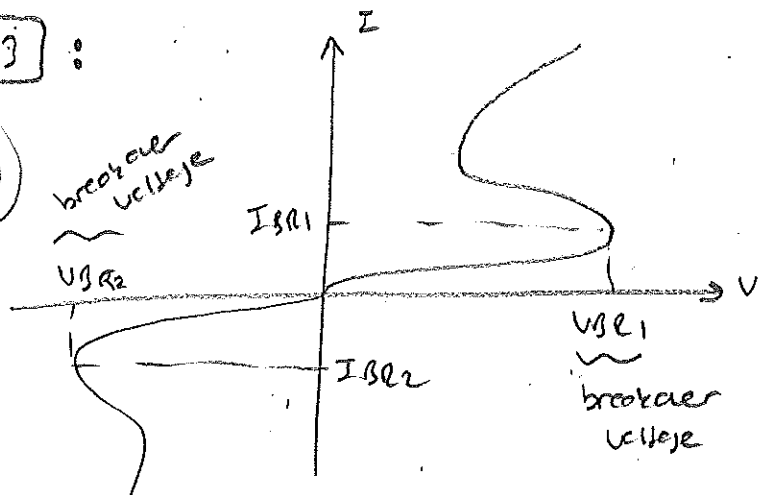

(2)

Q4 :

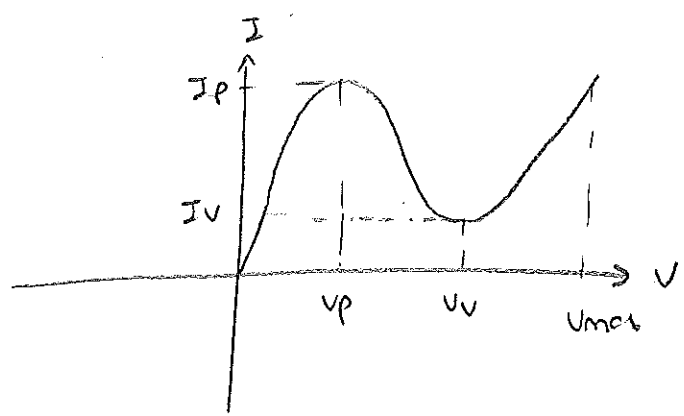


(6)

Q-5 :

If $R_L \uparrow$, $V_{out} \uparrow$, $V_S \uparrow$ and $I_{L1} \uparrow$
 V_S is constant due to zero diode. Thus $V_{S5} \downarrow$. If $V_{S5} \downarrow$
 then I_{L1} decreases so $V_S \downarrow$, $I_{L1} \downarrow$, $V_{out} \downarrow$. Thus R_L decreases.

In Laplace

(10)

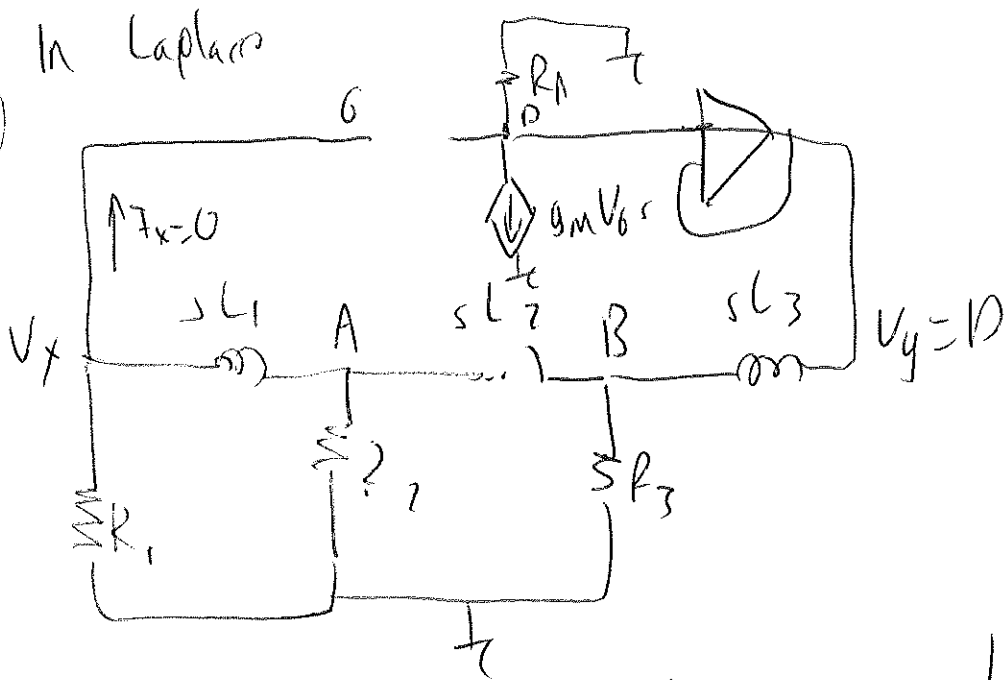

$$\frac{A - V_x}{sL_1} = \frac{V_x}{R_1}$$

$$AR_1 = (R_1 + sL_1)V_x$$

$$A = \frac{R_1 + sL_1}{R_1} V_x$$

$$\frac{A - V_x}{sL_1} + \frac{A}{R_2} = \frac{B - A}{sL_2}$$

$$A \left[\frac{1}{sL_1} + \frac{1}{R_2} + \frac{1}{sL_2} \right] = \frac{V_x}{sL_1} + \frac{B}{sL_2}$$

Let $R_1 = 1000 = R_2$ - $L_1 = L_2 = 1$ Henry

$$A = \frac{1000 + s}{1000} V_x$$

$$A \left[\frac{1}{s} + \frac{1}{1000} + \frac{1}{s} \right] = \frac{V_x}{s} + \frac{B}{s}$$

$$A(s + 2000) = 1000V_x + 1000B$$

$$A = \frac{1000[V_x + B]}{s + 2000}$$

$$\frac{V_y - B}{sL_3} = \frac{B}{R_3} + \frac{B - A}{sL_2} \rightarrow \frac{V_y - B}{s} = \frac{B}{1000} + \frac{B - A}{s}$$

$$1000V_y - 1000B = sB + 1000B - 1000A$$

$$\left[(s+2000)^2 (s+1000) - 10^6 (s+2000) \right] V_x = 10^8 V_y + 10^6 (1000+s) V_y$$

$$\left[(s+2000)^2 (s+1000) - 10^6 (s+2000) - 10^6 (s+1000) \right] V_x = 10^9 V_y$$

$$\left[(s+2000)^2 (s+1000) - 10^6 (1000+1000) \right] V_x = 10^9 V_y$$

$$\left[(s^2 + 4000s + 4 \times 10^6) (s+1000) - 10^9 \right] V_x = 10^9 V_y$$

$$\cancel{s^3 + (4 \times 10^6 + 4 \times 10^6) s^2}$$

$$\left[s^3 + 5000s^2 + 8 \times 10^6 s + 4 \times 10^9 - 10^9 \right] V_x = 10^9 V_y$$

$$\left[s^3 + 5000s^2 + 8 \times 10^6 s + 3 \times 10^9 \right] V_x = 10^9 V_y$$

$$\frac{V_x}{V_y} = \frac{10^9}{s^3 + 5000s^2 + 8 \times 10^6 s + 3 \times 10^9}$$

$$H(j\omega) = \frac{V_x(j\omega)}{V_y(j\omega)} = \frac{10^9}{(3 \times 10^9 - 5000\omega^2) + 8 \times 10^6 (j\omega) - j\omega^3} = \frac{10^9}{(3 \times 10^9 - 5000\omega^2) + j\omega(8 \times 10^6 - \omega^2)}$$

Let the imaginary part of $H(j\omega)$ be equal to zero

$$8 \times 10^6 - \omega^2 = 0$$

$$\omega^2 = 8 \times 10^6$$

$$\omega = 2\sqrt{2} \times 10^3 \Rightarrow f = \frac{2\sqrt{2} \times 10^3}{2\pi}$$

$$1000(V_y + A) = (s + 2000)B$$

$$B = \frac{1000(V_y + A)}{s + 2000} \quad \text{***}$$

* and **

$$\frac{1000+s}{1000} V_x = \frac{1000(V_x + B)}{s + 2000}$$

$$(s + 2000)(s + 1000) V_x = 10^6 (V_x + B) \rightarrow \text{put *** inside}$$

$$(s + 2000)(s + 1000) V_x = 10^6 \left(V_x + \frac{1000(V_y + A)}{s + 2000} \right)$$

$$(s + 2000)^2 (s + 1000) V_x = 10^6 \left[(s + 2000) V_x + 1000(V_y + A) \right]$$

$$\left[(s + 2000)^2 (s + 1000) - 10^6 (s + 2000) \right] V_x = 10^9 (V_y + A)$$

$$\left[(s + 2000)^2 (s + 1000) - 10^6 (s + 2000) \right] V_x = \cancel{10^9 V_x} + \cancel{10^9 \frac{1000+s}{1000} V_x} + \cancel{10^9 \frac{1000 A}{1000}}$$

$$= 10^9 \left(V_y + \frac{1000+s}{1000} V_x \right)$$

$$\omega = 2\sqrt{2} \times 10^3 \frac{\text{rad}}{\text{sec}} \Rightarrow f = \frac{2\sqrt{2} \times 10^3}{2\pi} \text{ Hz} \rightarrow \text{frequency of oscillation}$$

$$\text{if } \omega = 2\sqrt{2} \times 10^3 \frac{\text{rad}}{\text{sec}}$$

$$\textcircled{1} \left| \frac{V_x(j\omega)}{V_y(j\omega)} \right| = \frac{10^9}{(3 \times 10^9 - 5000\omega^2)} \Bigg|_{\omega = 2\sqrt{2} \times 10^3} = \frac{10^9}{3 \times 10^9 - 5000 \times 8 \times 10^6}$$

$$= \frac{10^9}{3 \times 10^9 - 40 \times 10^9} = \frac{10^9}{-37 \times 10^9} = \frac{1}{-37}$$

$$\text{Hence } \left| \frac{V_x(j\omega)}{V_y(j\omega)} \right| = \frac{1}{37}$$

$$\text{Due to Barkhausen criteria } \left| \frac{V_{o2}}{V_{i1}} \right| \times A = 1$$

$$\frac{1}{37} \times A = 1 \quad A = 37 = (-g_m R_D)$$

$$V_{in} = \left[\left(7 + \frac{1}{sCR} \right) \left(7 + \frac{1}{sCR} \right) - 1 \right] V_{out} - \left(7 + \frac{1}{sCR} \right) V_{out}$$

put *** inside

$$V_{in} = \left[\left(7 + \frac{1}{sCR} \right) \left(7 + \frac{1}{sCR} \right) - 1 \right] \left(1 + \frac{1}{sCR} \right) V_{out} - \left(7 + \frac{1}{sCR} \right) V_{out}$$

$$V_{in} = \left[4 + \frac{1}{s^2 C^2 R^2} + \frac{4}{sCR} - 1 \right] \left(1 + \frac{1}{sCR} \right) V_{out} - \left(7 + \frac{1}{sCR} \right) V_{out}$$


$$V_{in} = \left[\left(3 + \frac{1}{s^2 C^2 R^2} + \frac{4}{sCR} \right) \left(1 + \frac{1}{sCR} \right) - \left(7 + \frac{1}{sCR} \right) \right] V_{out}$$

$$V_{in} = \left[3 + \frac{7}{sCR} + \frac{5}{s^2 C^2 R^2} + \frac{1}{s^3 C^3 R^3} - 2 - \frac{1}{sCR} \right] V_{out}$$


$$V_{in} = \left[1 + \frac{6}{sCR} + \frac{5}{s^2 C^2 R^2} + \frac{1}{s^3 C^3 R^3} \right] V_{out}$$

$$V_{in} = \left[\frac{s^3 C^3 R^3 + 6s^2 C^2 R^2 + 5sCR + 1}{s^3 C^3 R^3} \right] V_{out}$$
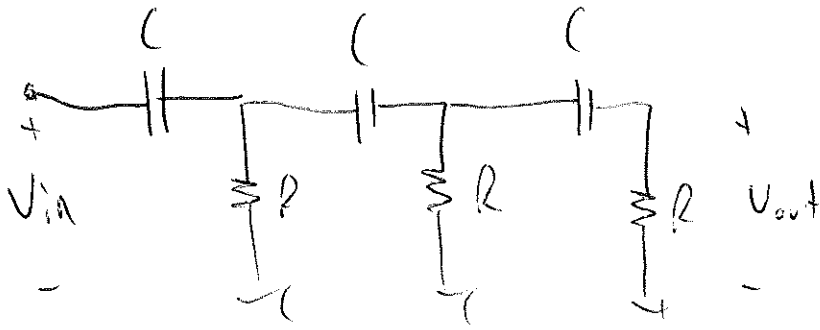
$$\frac{V_{out}}{V_{in}} = \frac{s^3 C^3 R^3}{s^3 C^3 R^3 + 6s^2 C^2 R^2 + 5sCR + 1}$$



{ Laplace

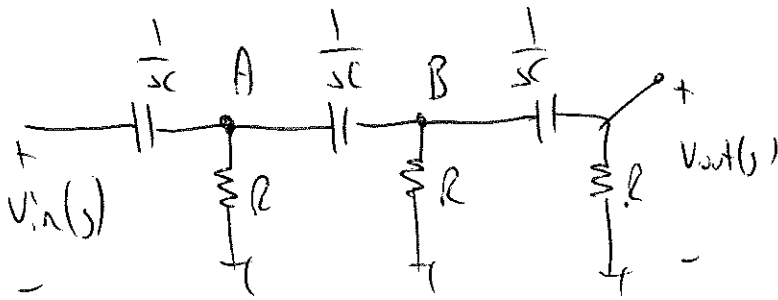

$$\frac{V_{in} - A}{\frac{1}{sC}} = \frac{A}{R} + \frac{A - B}{\frac{1}{sC}}$$

$$\frac{A - B}{\frac{1}{sC}} = \frac{B}{R} + \frac{B - V_{out}}{\frac{1}{sC}}$$

$$* \quad sC V_{in} = \left[2sC + \frac{1}{R} \right] A - sC B$$

$$* \quad sC A = \left[2sC + \frac{1}{R} \right] B - sC V_{out}$$

**

$$A = \left[2 + \frac{1}{sCR} \right] B - V_{out}$$

$$\frac{B - V_{out}}{\frac{1}{sC}} = \frac{V_{out}}{R}$$

$$B sC = \left[sC + \frac{1}{R} \right] V_{out}$$

* and **

$$sC V_{in} = \left[2sC + \frac{1}{R} \right] \left\{ \left[2 + \frac{1}{sCR} \right] B - V_{out} \right\} - sC B$$

$$B = \left[1 + \frac{1}{sCR} \right] V_{out}$$

$$sC V_{in} = \left(2sC + \frac{1}{R} \right) \left(2 + \frac{1}{sCR} \right) B - \left[2sC + \frac{1}{R} \right] V_{out} - sC B$$

$$V_{in} = \left[2 + \frac{1}{sCR} \right] \left(2 + \frac{1}{sCR} \right) B - \left[2 + \frac{1}{sCR} \right] V_{out} - B$$

out $s = j\omega$

$$H(j\omega) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{-j\omega^3 C^3 R^3}{(1 - \omega^2 6 C^2 R^2) + (5j\omega CR - j\omega^3 C^3 R^3)}$$

$$\angle H(j\omega) = 180^\circ \Rightarrow \text{for oscillation}$$

$$1 - \omega^2 6 C^2 R^2 = 0$$

$$\omega_0^2 = \frac{1}{6 C^2 R^2}$$

$$\omega_0 = \frac{1}{\sqrt{6} CR}$$

$$f_0 = \frac{1}{2\pi \sqrt{6} CR}$$

Let's find

$$|H(j\omega)|$$

$$\omega = \omega_0 = \frac{1}{\sqrt{6} CR}$$

$$|H(j\omega)| = \frac{\omega^3 C^3 R^3}{\sqrt{[(-\omega^2 6 C^2 R^2)]^2 + [5\omega CR - \omega^3 C^3 R^3]^2}}$$

$$|H(j\omega)| \Big|_{\omega = \omega_0 = \frac{1}{\sqrt{6} CR}} = \frac{\frac{C^3 R^3}{6\sqrt{6} C^3 R^3}}{\sqrt{0 + \left[5 \frac{1}{\sqrt{6} CR} CR - \left(\frac{1}{\sqrt{6} CR}\right)^3 C^3 R^3\right]^2}}$$

$$= \frac{\frac{1}{6\sqrt{6}}}{\sqrt{0 + \left[\frac{5}{\sqrt{6}} - \frac{1}{6\sqrt{6}}\right]^2}} = \frac{\frac{1}{6\sqrt{6}}}{\frac{24}{6\sqrt{6}}} = \frac{1}{24}$$