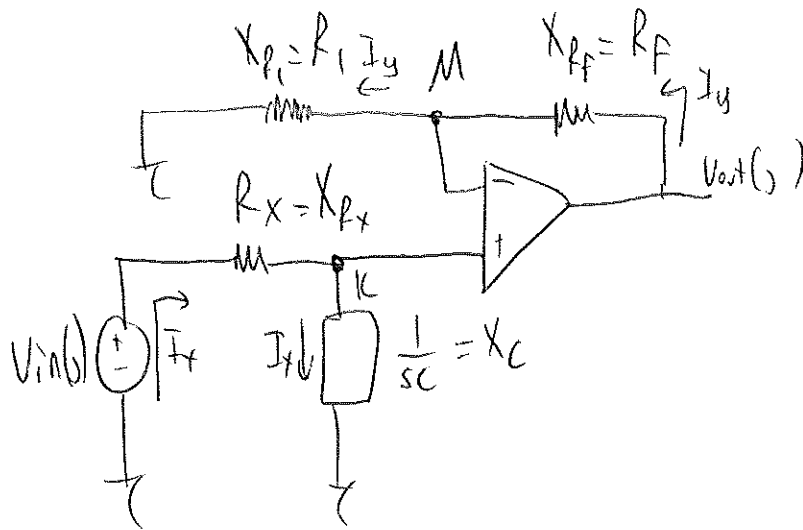


Q1 In Laplace domain

Sayfa 1



$$\frac{V_{in} - K}{R_x} = \frac{K}{X_C} \quad \frac{V_{in} - K}{R_x} = \frac{K}{\frac{1}{sC}} \quad V_{in} = K[1 + sCR_x]$$

$$K = \frac{V_{in}}{1 + sCR_x} \quad (\text{para.})$$

$$\frac{V_{out} - M}{R_f} = \frac{M}{R_1} \quad \frac{V_{out} - M}{R_f} = \frac{M}{R_1} \quad V_{out} R_1 = M[R_1 + R_f]$$

$$M = \frac{V_{out} R_1}{R_1 + R_f}$$

$$M = K \Rightarrow \frac{V_{in}}{1 + sCR_x} = V_{out} \frac{R_1}{R_1 + R_f}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_1 + R_f}{R_1} \frac{1}{1 + sCR_x} \quad (\text{2 para.})$$

$$\frac{V_{out}}{V_{in}} = \frac{R_1 + R_f}{R_1} \frac{1}{1 + sCR_x} \quad (\text{5 para.})$$

$$= \frac{V_{out}}{V_{in}} = \frac{R_1 + R_f}{R_1} \frac{1}{s + \frac{1}{CR_x}} \quad H(s) = \frac{V_{out}}{V_{in}} = \frac{R_1 + R_f}{R_1} \frac{1}{s + \frac{1}{CR_x}} \quad (\text{1 para.})$$

This is a low pass filter

the maximum gain occurs when $\omega = 0$

$$H(j\omega) = \frac{R_1 + R_f}{R_1} \frac{1}{j\omega + \frac{1}{CR_x}}$$


$$|H(j\omega)| = \frac{R_1 + R_f}{R_1} \frac{1}{\sqrt{\omega^2 + \left(\frac{1}{CR_x}\right)^2}}$$

if $\omega \uparrow$ $|H(j\omega)| \downarrow$

$$|H(j\omega)| \Big|_{\omega=0} = \frac{R_f R_f}{R_i} = \text{Max gain}$$

Sayfa 2

$|H(j\omega)|$

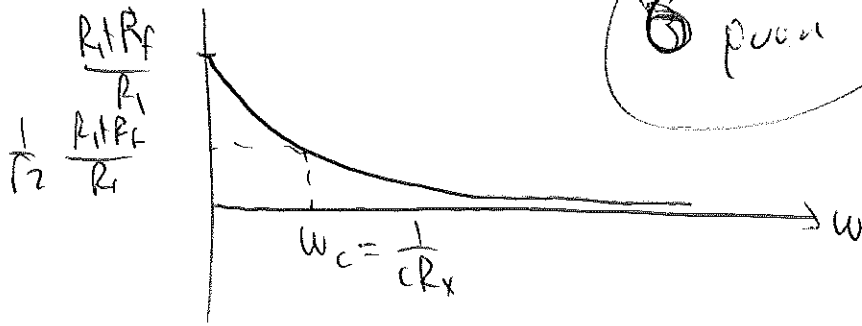


Hence Max gain $\frac{R_f R_f}{R_i} = 10$ $f_f = 9R_i$ should be found


Let $R_i = 1M\Omega$ $R_f = 9M\Omega$ 2 puan

Cut off frequency $= \omega_c = \frac{1}{CR_x}$ at $|H(j\omega)| \Big|_{\omega=\omega_c} = \frac{R_f R_f}{R_i} \frac{1}{\sqrt{2}} = \frac{\text{Gain-max}}{\sqrt{2}}$

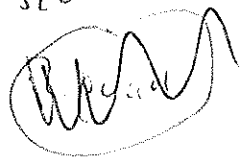hence $\frac{1}{CR_x} = 10000 \frac{\text{rad}}{\text{sec}}$ Let $R_x = 1000\Omega \Rightarrow C = 10^{-7} F$



(Q2) $V_{out} = -2 \frac{d^2}{dt^2} V_{out} + V_1 - 3V_2$

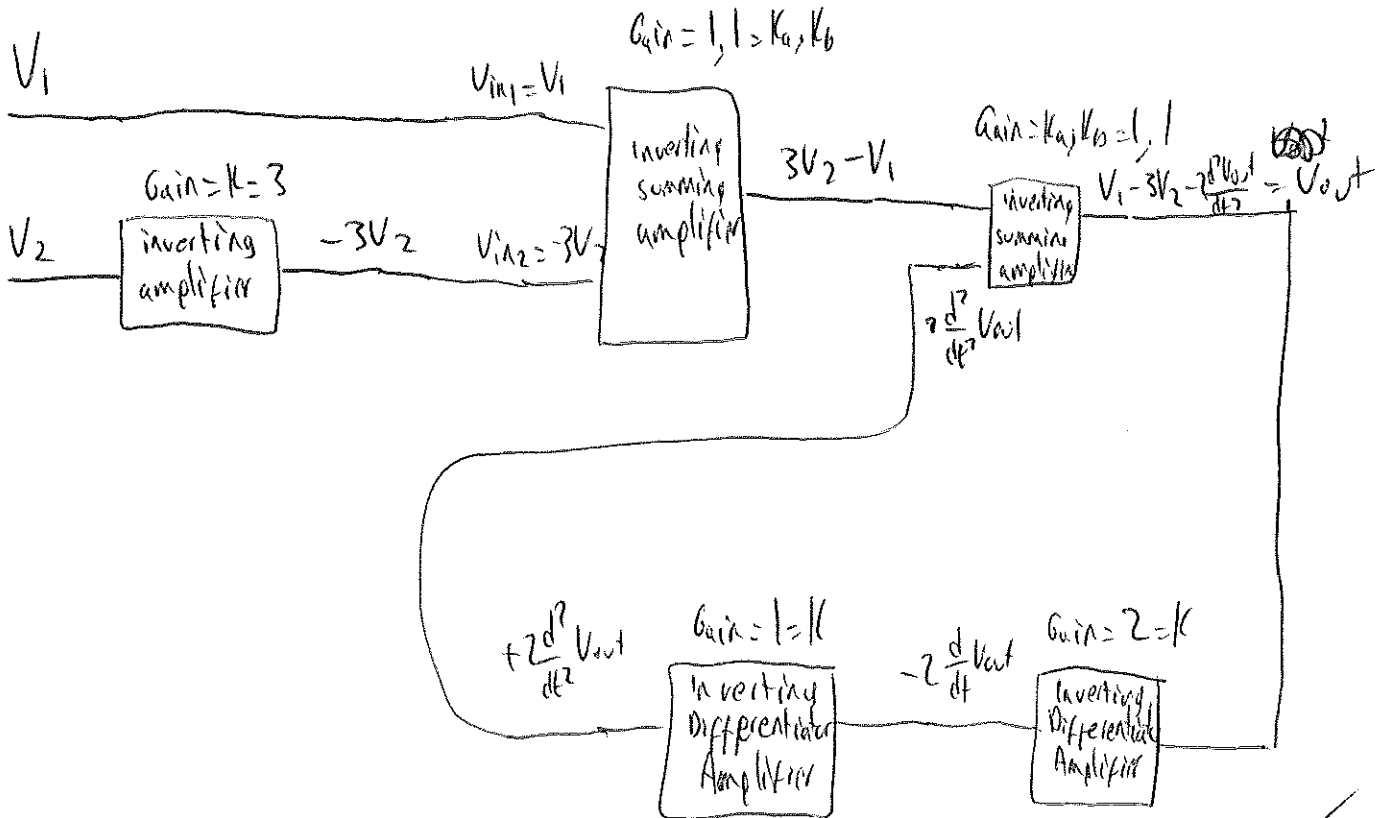


Skillor 13
Korany 20



Q3

When procedure is applied

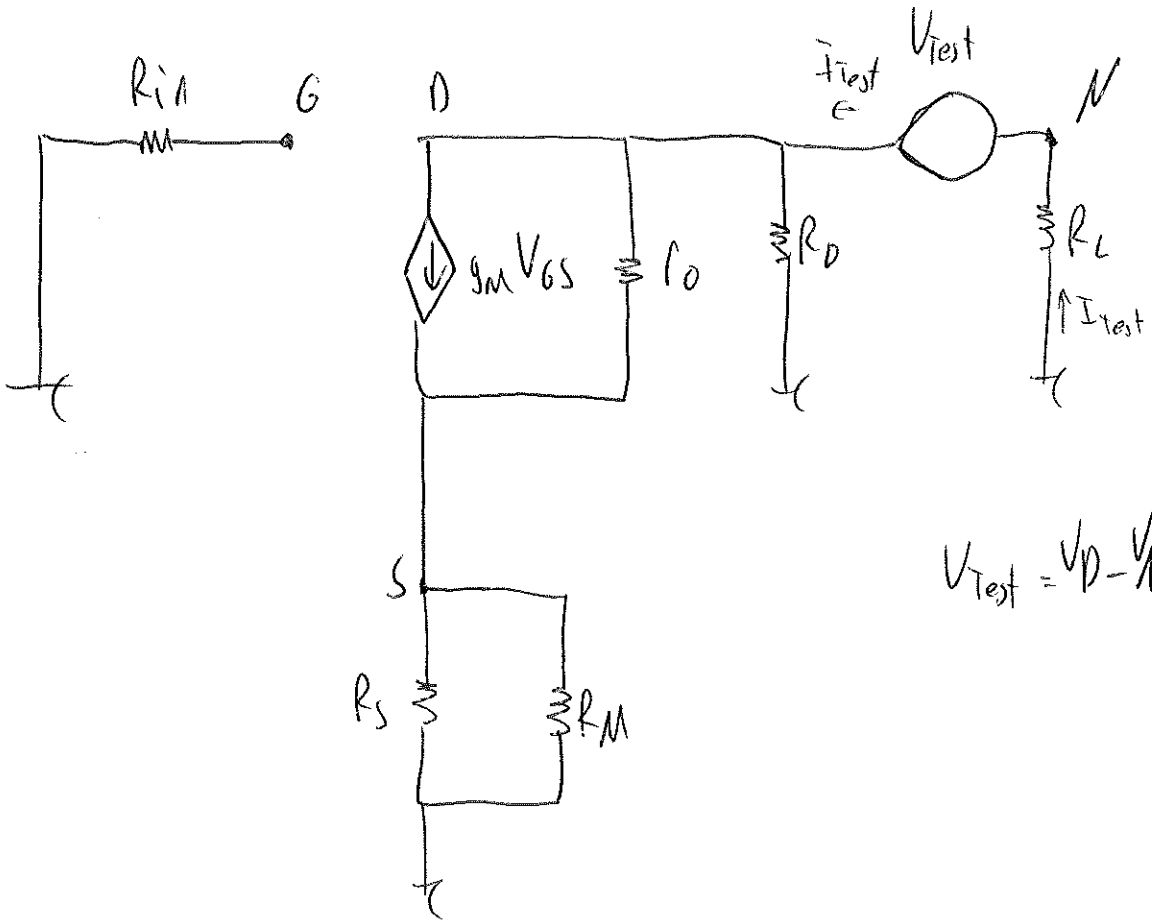

$$V_{Test} = V_D - V_S$$

$$V_G = 0$$

~~$I_{Test} = \frac{V_D - V_S}{R_L}$~~

$$I_{Test} = \frac{V_D}{R_D} + \frac{V_D - V_S}{r_o} + g_m V_{GS}$$

$$I_{Test} = \frac{V_D}{1000} + \frac{V_D - V_S}{1000} + \frac{1}{1000} (V_G - V_S)$$

$$I_{Test} = V_D \left[\frac{2}{1000} \right] - \frac{V_S}{1000} - \frac{V_S}{1000}$$

$$I_{Test} = V_D \left[\frac{2}{1000} \right] - V_S \left[\frac{2}{1000} \right]$$

$$g_m V_{GS} + \frac{V_D - V_S}{r_o} = \frac{V_S}{R_S} + \frac{V_S}{R_M} \quad V_D = 0$$

Sayfa 5

$$\frac{1}{1000} [V_D - V_S] + \frac{V_D - V_S}{1000} = \frac{V_S}{1000} + \frac{V_S}{1000}$$

$$\frac{V_D}{1000} = 4 \frac{V_S}{1000}$$

$$\boxed{V_D = 4V_S} \Rightarrow \boxed{V_S = \frac{V_D}{4}}$$

$$I_{Test} = V_D \left[\frac{2}{1000} \right] - \frac{V_D}{4} \left[\frac{2}{1000} \right]$$

$$\boxed{I_{Test} = \frac{3V_D}{4} \left[\frac{2}{1000} \right]}$$

$$V_D = \frac{4000}{6} I_{Test}$$

$$I_{Test} = \frac{0 - V_N}{R_L}$$

$$I_{Test} \times 1000 = -V_N$$

$$V_N = -1000 I_{Test}$$

$$V_D - V_N = V_{Test} = \frac{4000}{6} I_{Test} - (-1000) I_{Test}$$

$$= \frac{10000}{6} I_{Test}$$

$$R_{cd} = \frac{V_{Test}}{I_{Test}} = \frac{10000}{6} \Omega$$

$$f_{cut-off-Cd} = \frac{1}{2\pi C_d R_{cd}} = \frac{1}{2\pi \times 10^{-6} F \times \frac{10000}{6} \Omega} = \frac{6 \times 10^6}{2\pi \times 10000} = \frac{600}{2\pi} \text{ Hz}$$