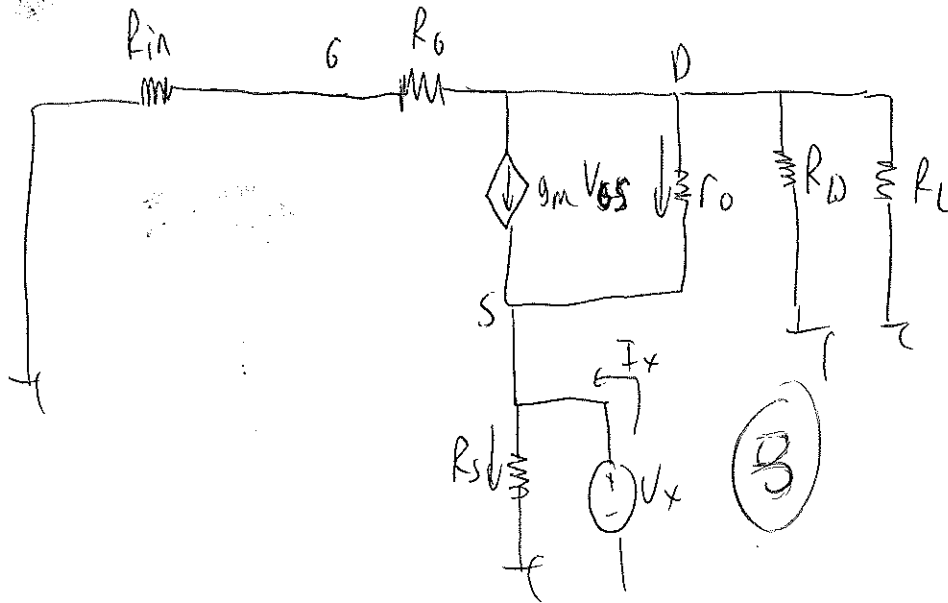


Q1) For cut-off frequency due to capacitor C_s short C_g and C_d . Put a test source V_x instead of C_s and calculate current I_x , short V_{in}



$$V_s = V_x \quad I_x = \frac{V_x}{R_s} - \frac{V_D - V_s}{r_o} - g_m V_{gs}$$

At node S

$$I_x = \frac{V_x}{1000} + \frac{V_s}{r_o} - \frac{V_D}{r_o} - g_m (V_D - V_s)$$

$$I_x = \frac{V_x}{1000} + \frac{V_x}{1000} - \frac{V_D}{1000} - \frac{1}{1000} (V_D - V_x)$$

$$I_x = \frac{3}{1000} V_x - \frac{V_D}{1000} - \frac{V_s}{1000} *$$

(10)

At node D

$$\frac{V_D - V_G}{R_G} + g_m V_{GS} + \frac{V_D - V_S}{r_o} + \frac{V_D}{R_D \parallel R_L} = 0$$

$$\frac{V_D - V_G}{500} + \frac{1}{1000} (V_G - V_S) + \frac{V_D - V_S}{1000} + \frac{V_D}{500} = 0$$

$$V_D \left[\frac{1}{500} + \frac{1}{500} + \frac{1}{1000} \right] + V_G \left[\frac{1}{1000} - \frac{1}{500} \right] - \frac{2}{1000} V_S = 0$$

$$V_D \left[\frac{5}{1000} \right] + V_G \left[\frac{1}{1000} - \frac{2}{1000} \right] - \frac{2}{1000} V_S = 0$$

$$\boxed{5V_D - V_G + 2V_S = 0} \quad \text{(*)} \quad \boxed{5V_D - V_G + 2V_S = 0} \quad \text{**}$$

At node G

$$\frac{D-G}{R_G} = \frac{G-O}{R_{in}}$$

$$\frac{D-G}{500} = \frac{G-O}{500}$$

$$\boxed{V_D = 2V_G} \quad \text{***}$$

~~Wrote wrong~~

put *** in **

$$5(2V_G) - V_G + 2V_S = 0$$

$$\boxed{9V_G + 2V_S = 0} \quad \text{(*)}$$

$$V_G = -\frac{2V_S}{9}$$

$$I_x = \frac{3}{1000} V_x - \frac{2V_G}{1000} - \frac{V_G}{1000}$$

$$I_x = \frac{3V_x}{1000} - \frac{3V_G}{1000}$$

$$I_x = \frac{3V_x}{1000} - \frac{3}{1000} \left(-\frac{2}{9} \right) V_x$$

$$I_x = \left[\frac{3}{1000} + \frac{2}{3000} \right] V_x \quad \text{(*)}$$


$$I_x = \left[\frac{9+2}{3000} \right] V_x \quad \frac{V_x}{I_x} = \frac{3000}{11} \Omega$$

$$R_x = \frac{3000}{11} \Omega$$

$$f_{\text{cut-off due to } C_s} = \frac{1}{2\pi \times C_s \times R_x} = \frac{1}{2\pi \times 1 \times 10^{-6} \times \frac{3000}{11}}$$
$$= \frac{11 \times 10^6}{2\pi \times 3000} = \frac{11000}{6\pi} \text{ Hertz}$$

(3)


Q2

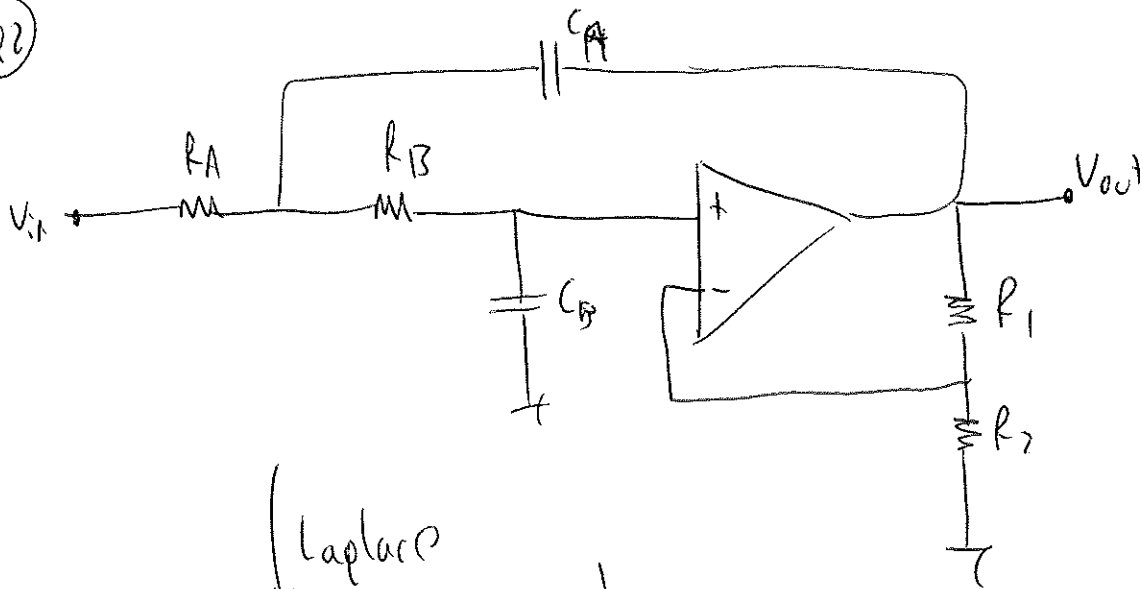

(a)

Laplace

(b)

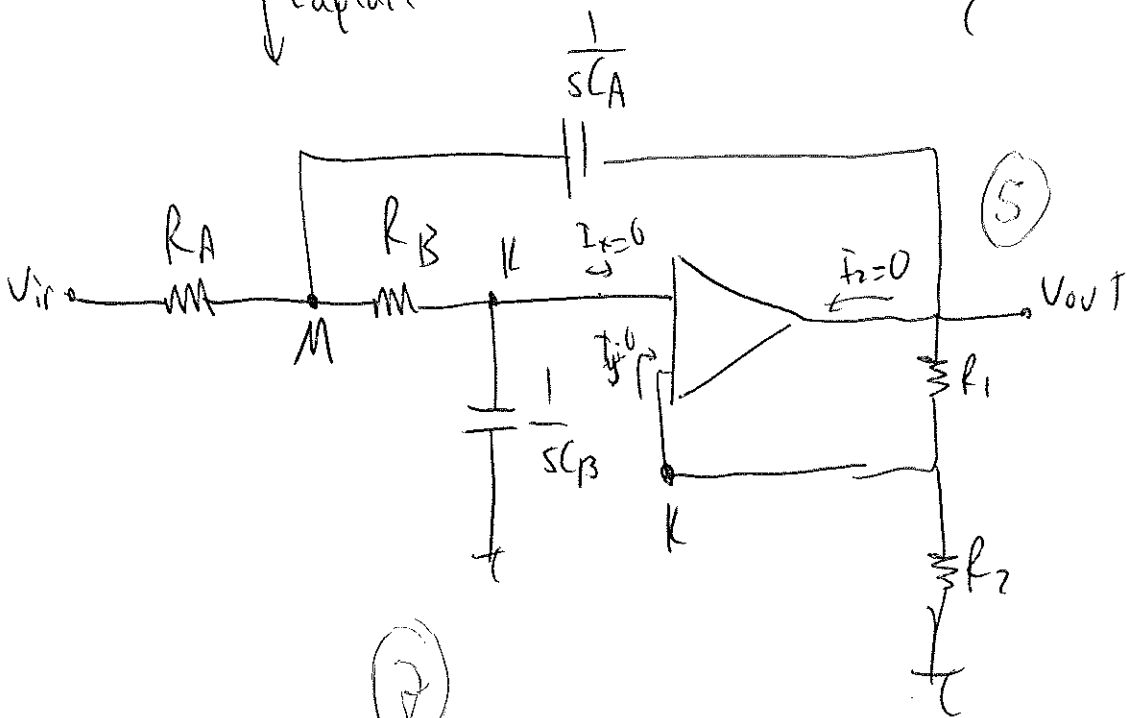

(c)

$$K = V_{out} \frac{R_2}{R_1 + R_2} \quad *$$

$$\frac{M}{R_B + \frac{1}{sC_B}} = \frac{K}{\frac{1}{sC_B}}$$

$$\frac{M s C_B}{s C_B R_B + 1} = K s C_B$$

$$M = [s C_B R_B + 1] K \quad **$$

(d)

$$\frac{V_{in} - M}{R_A} = \frac{M - K}{R_B} + \frac{M - V_{out}}{\frac{1}{sC_A}}$$

$$(V_{in} - M) R_B = (M - K) R_A + s C_A R_A R_B (M - V_{out})$$

$$V_{in} R_B + V_{out} (s C_A R_A R_B) = M [R_A + R_B + s C_A R_A R_B] - K R_A \quad ***$$

$$V_{in} R_B + V_{out} (s C_A R_A R_B) = (s C_B R_B + 1) (R_A + R_B + s C_A R_A R_B) K - K R_A$$

$$V_{in} R_B + V_{out} (s C_A R_A R_B) = (s^2 C_A C_B R_A R_B^2 + s (C_B R_B R_A + C_B R_B R_B + C_A R_A R_B) + R_B) K$$

$$V_{in} + V_{out} (s C_A R_A) = (s^2 C_A C_B R_A R_B + s (C_B R_A + C_B R_B + C_A R_A) + 1) K$$

$$\ominus \quad V_{in} = \left[\frac{R_2}{R_1 R_2} \left[s^2 C_A C_B R_A R_B + s (R_A C_B + C_B R_B + C_A R_A) + 1 \right] - s C_A R_A \right] V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_1 R_2}{s^2 (R_2 C_A C_B R_A R_B) + s R_2 (R_A C_B + C_B R_B + C_A R_A) - (R_1 R_2) s C_A R_A + R_2}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_1 R_2}{R_2} \frac{1}{s^2 (C_A C_B R_A R_B) + s (R_A C_B + C_B R_B + C_A R_A) - \frac{R_1 R_2}{R_2} s C_A R_A + 1}$$

⑥ ~~XXXXXXXXXXXX~~ $C_A = C_B = C$ $R_A = R_B = R$ Let $R_1 = 0$
 $R_2 = \infty$

$$\frac{V_{out}}{V_{in}} = \frac{R_1 R_2}{R_2} \frac{1}{s^2 (C^2 R^2) + s (3RC - \frac{R_1 R_2}{R_2} RC) + 1}$$

Let $R_1 = 0$ $R_2 = \infty$

$$\frac{V_{out}}{V_{in}} = \frac{1}{s^2 C^2 R^2 + s (2CR) + 1}$$

$$(c) \frac{V_{out}}{V_{in}} = \frac{1}{s^2 C^2 R^2 + s(2CR) + 1} = H(s) = \frac{1}{[sCR + 1]^2}$$

$$H(j\omega) = \frac{1}{(1 - C^2 R^2 \omega^2) + j\omega(2CR)} \quad |H(j\omega)| = \frac{1}{\left[(1 - C^2 R^2 \omega^2)^2 + (\omega 2CR)^2 \right]^{\frac{1}{2}}}$$

$$\begin{aligned} |H(j\omega)|_{dB} &= 20 \log 1 - 20 \log \left[(1 - C^2 R^2 \omega^2)^2 + (\omega 2CR)^2 \right]^{\frac{1}{2}} \\ &= -20 \log \left[(1 - \omega^2 R^2 C^2)^2 + (2R\omega)^2 \right]^{\frac{1}{2}} \end{aligned}$$

Approximation 1
 $0 < \omega < \frac{1}{CR}$

$$|H(j\omega)|_{dB} \approx -20 \log 1 = 0 \text{ dB}$$


$$\frac{1}{CR} < \omega$$

$$\begin{aligned} |H(j\omega)|_{dB} &\approx -20 \log (\omega^2 R^2 C^2) = -20 \log \omega^2 - 20 \log R^2 C^2 \\ &= -40 \log \omega - 20 \log R^2 C^2 \end{aligned}$$

Real Value

let $\omega = RC$

$$\begin{aligned} |H(j\omega)|_{dB} &= -20 \log \left[\left(1 - \frac{1}{R^2 C^2} R^2 C^2\right)^2 + (2RC \frac{1}{RC})^2 \right]^{\frac{1}{2}} \\ &= -20 \log [0 + 4]^{\frac{1}{2}} = -20 \log 2 \end{aligned}$$

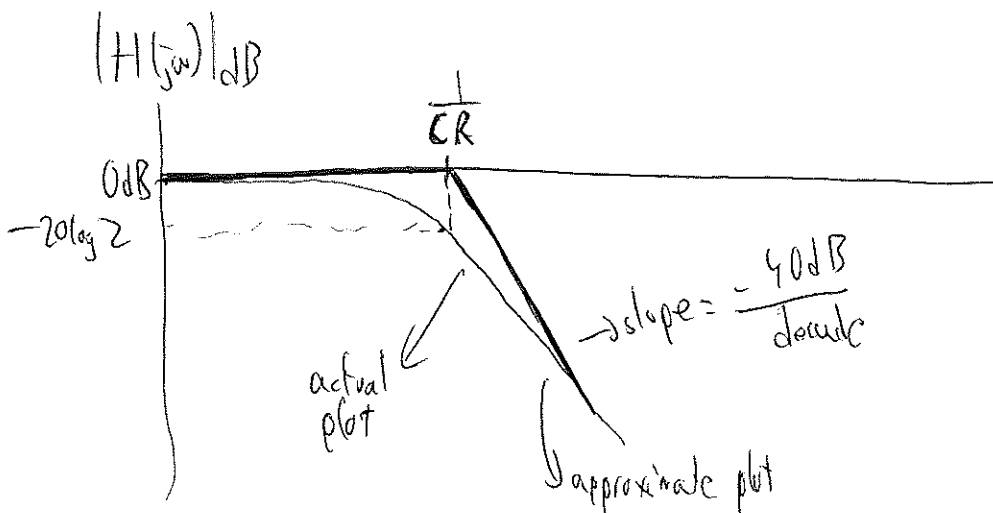

(d) actual cut off frequency (low pass filter)

$$|H(j\omega)|_{\max} = |H(j\omega)|_{\omega=0} = 1 //$$

$$\frac{|H(j\omega)|_{\max}}{\sqrt{2}} = |H(j\omega)|_{\omega=\text{cut-off}} = \frac{1}{\sqrt{2}} // \quad \omega CR = x$$

$$\frac{1}{\left[(1 - C^2 R^2 \omega^2)^2 + (\omega CR)^2 \right]^{\frac{1}{2}}} = \frac{1}{\sqrt{2}}$$

$$2 = (1 - C^2 R^2 \omega^2)^2 + (\omega CR)^2$$

$$2 = (1 - x)^2 + (2x)^2$$

$$2 = 1 + x^2 - 2x + 4x^2$$

$$5x^2 - 2x - 1 = 0 //$$

$$x = \frac{2 \pm \sqrt{4 + 20}}{2 \times 5} = \frac{2 \pm \sqrt{24}}{10} = \frac{2 \pm 2\sqrt{6}}{10} = \frac{1 \pm \sqrt{6}}{5} //$$

$x \rightarrow \frac{1 - \sqrt{6}}{5}$ (not possible as $\frac{1 - \sqrt{6}}{5} < 0$ and x should be greater than 0)
 $x \rightarrow \frac{1 + \sqrt{6}}{5}$ (possible)

$$\omega CR = x \quad \omega CR = \frac{1 + \sqrt{6}}{5} \quad \omega = \frac{1 + \sqrt{6}}{5CR} = \frac{1 + \sqrt{6}}{5} \left(\frac{1}{CR} \right) \frac{\text{rad}}{\text{sec}}$$