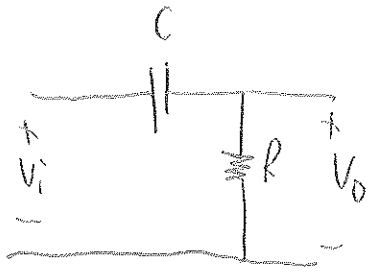


RC circuit (not a) Low frequency analysis - bode plot



impedance of $C \rightarrow X_C = \frac{1}{j2\pi fC} = \frac{-j}{2\pi fC}$

if $f \rightarrow 0$ $|X_C| \rightarrow \infty \Omega$

if $f \rightarrow \infty$ $|X_C| \rightarrow 0 \Omega$

if frequency is low $|X_C| \rightarrow \infty$ (open circuit)

if frequency is high $|X_C| \rightarrow 0$ (short circuit)


This is a high pass filter

$\frac{V_o}{V_i} = A_V \rightarrow \text{gain}$ $\frac{V_o}{V_i} = \frac{R}{R + X_C}$ $\left| \frac{V_o}{V_i} \right| = \frac{R}{\sqrt{R^2 + X_C^2}}$

if $X_C = R \Rightarrow \left| \frac{V_o}{V_i} \right| = |A_V| = \frac{1}{\sqrt{2}} = 0.707$

\downarrow
 $X_C = \frac{1}{2\pi f_i C} = R$ $f_i = \frac{1}{2\pi RC}$ (corner frequency)
 (half power frequency)


$A_V = \left| \frac{V_o}{V_i} \right|$

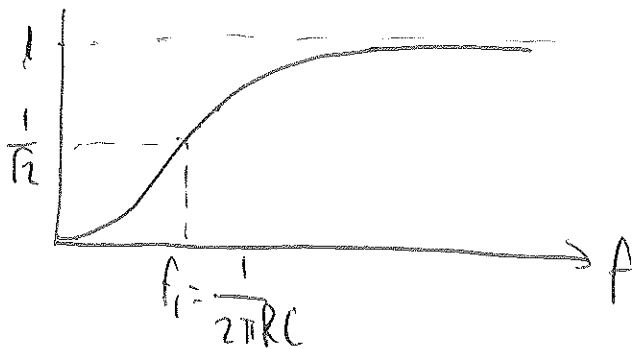

Low frequency response of RC circuit

$A_V = \frac{V_o}{V_i} = \frac{R}{R - \frac{j}{2\pi fC}} = \frac{1}{1 - j\left(\frac{f_i}{f}\right)}$

$|A_V| = \left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{1 + \left(\frac{f_i}{f}\right)^2}}$ (magnitude)

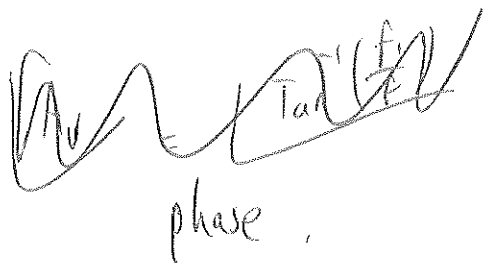


$$\theta = \text{Tan}^{-1} \left(\frac{f_i}{f} \right) = \angle A_v = \angle \frac{V_o}{V_i} = \angle V_o - \angle V_i$$

phase

$$A_{v,dB} = 20 \log_{10} \frac{1}{\sqrt{1 + \left(\frac{f_i}{f}\right)^2}} \quad (\text{The gain in dB})$$

if $f < f_i$ $A_{v,dB} \approx -10 \log_{10} \left(\frac{f_i}{f}\right)^2 = -20 \log_{10} \frac{f_i}{f}$

if $f > f_i$ $A_{v,dB} \approx 0$

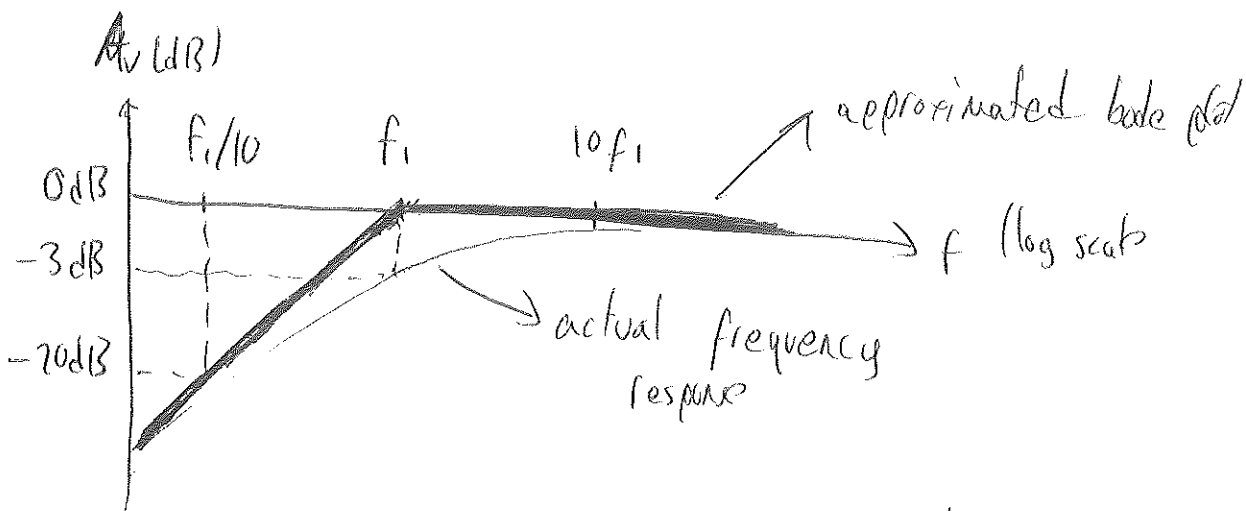

put $f = f_i$ $A_{v,dB} \Big|_{f=f_i} = 20 \log_{10} \frac{1}{\sqrt{1 + \left(\frac{f_i}{f_i}\right)^2}} \approx -3dB$


$$\text{phase} = \theta = \text{Tan}^{-1} \frac{f_i}{f}$$

- if $f \ll f_i$ $\theta \rightarrow 90^\circ$
- if $f = f_i$ $\theta = 45^\circ$
- if $f \gg f_i$ $\theta \rightarrow 0^\circ$

$$\angle V_o - \angle V_i = \angle A_v$$


if positive V_o leads V_i
if negative V_o lags V_i

Phase response of RC circuit

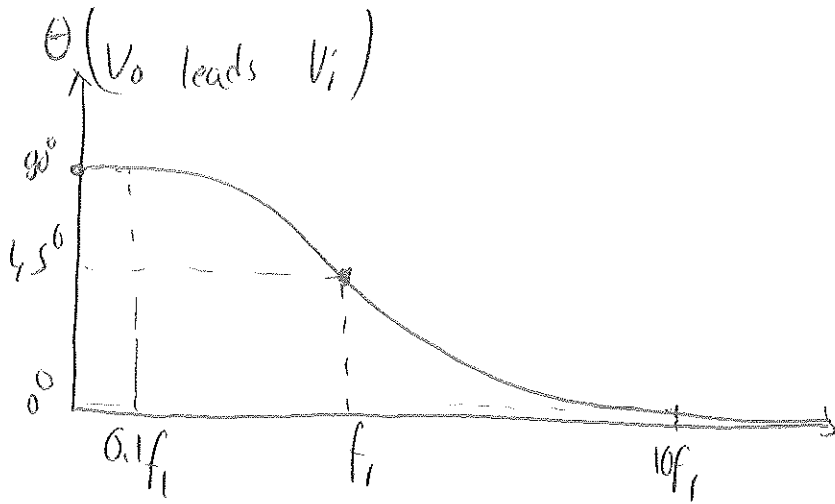


If we add RC coupled network with an amplifier which also introduces a phase shift of 180° we will observe

RC coupled amplifier phase diagram

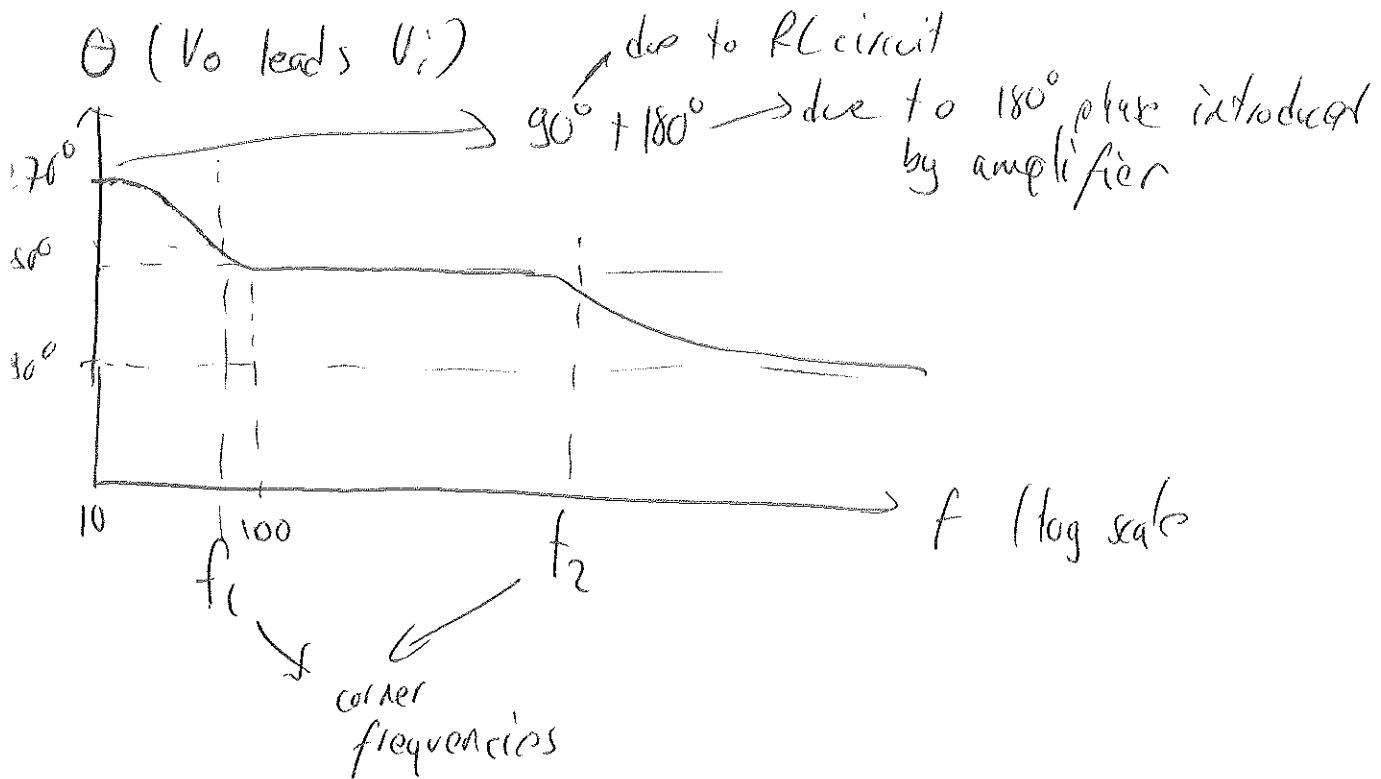

Low frequency response (BJT) amplifier

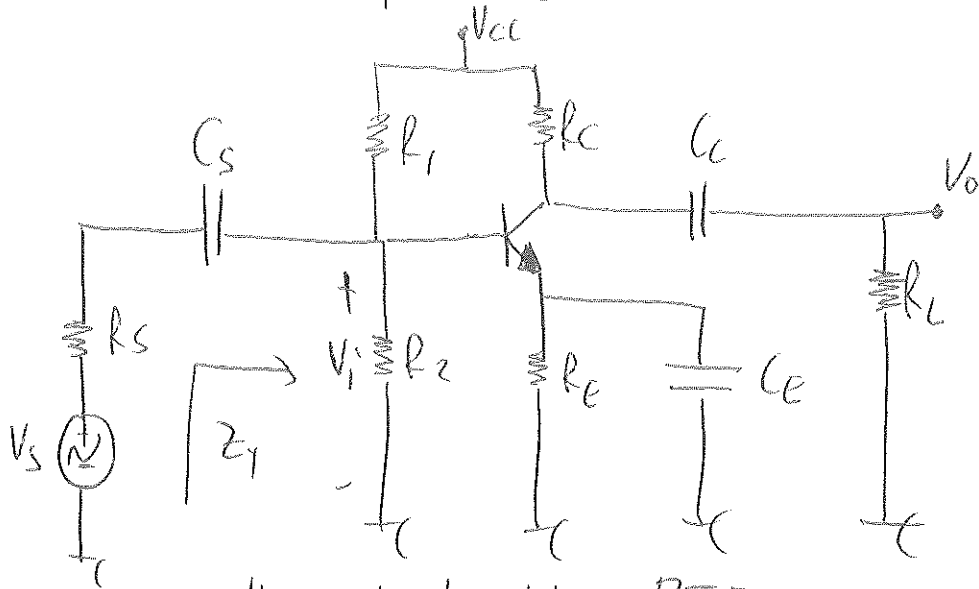


voltage divider bias BJT configuration

C_s → source coupling capacitance

C_e, C_c → Collector and Emitter by-pass capacitors

C_s, C_c, C_e → determines the low frequency response

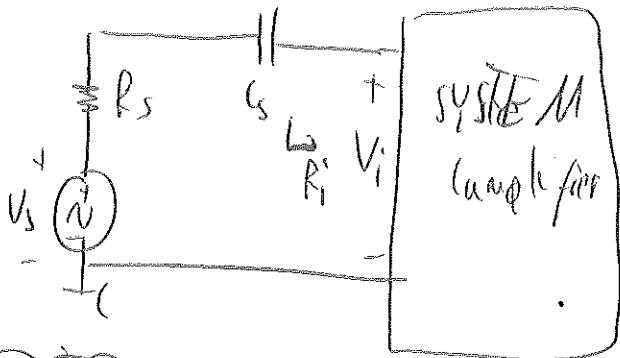C_s : normally connected between the applied source and the active device (amplifier)




→ Circuit to determine effect of C_s on low-frequency response

R_i → input resistance of system (amplifier)


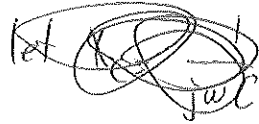
$$V_i = \frac{R_i V_s}{R_s + R_i - jX_c}$$



$$X_c = \frac{1}{2\pi f C}$$

→ impedance of capacitor

$$\frac{V_i}{V_s} = \frac{R_i}{R_s + R_i - jX_{Cs}} = \frac{1}{1 + \frac{R_s}{R_i} - j \frac{X_{Cs}}{R_i}} = \frac{1}{\left(1 + \frac{R_s}{R_i}\right) \left(1 - j \frac{X_{Cs}}{R_i R_s}\right)}$$

$$\frac{X_{Cs}}{R_i R_s} = \frac{1}{2\pi f C_s (R_i + R_s)} \quad f_i = \frac{1}{2\pi (R_i + R_s) C_s} \rightarrow \text{define}$$

hence

$$\frac{V_i}{V_s} = \frac{1}{\left(1 + \frac{R_s}{R_i}\right) \left(1 - j \frac{1}{2\pi f C_s (R_i + R_s)}\right)}$$

$$= \frac{1}{\left(1 + \frac{R_s}{R_i}\right) \left(1 - j \frac{f_i}{f}\right)}$$

$$A_{V_i} = \frac{V_i}{V_s} = \frac{R_i}{R_i + R_s} \left[\frac{1}{1 - j \left(\frac{f_i}{f}\right)} \right]$$


at midband the gain is $A_{V_{mid}} = \frac{V_o}{V_i} = \frac{R_i}{R_i + R_s}$

$$\text{and } \frac{A_V}{A_{V_{mid}}} = \frac{1}{1 - j \left(\frac{f_i}{f}\right)}$$




cut-off frequency $f_c = f_i = \frac{1}{2\pi (R_i + R_s) C_s}$

at cut-off frequency V_o will be $\frac{1}{\sqrt{2}}$ of midband gain value $A_{V_{mid}}$

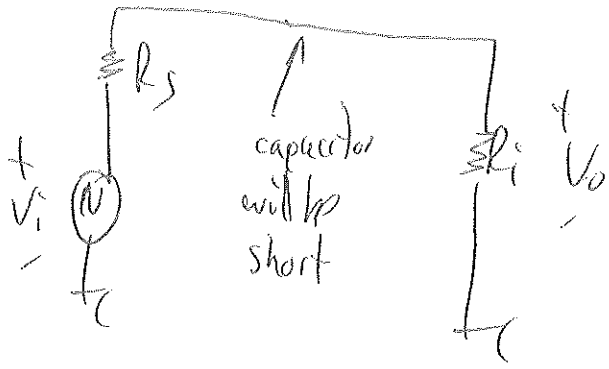at high frequency (high frequency equivalent circuit)



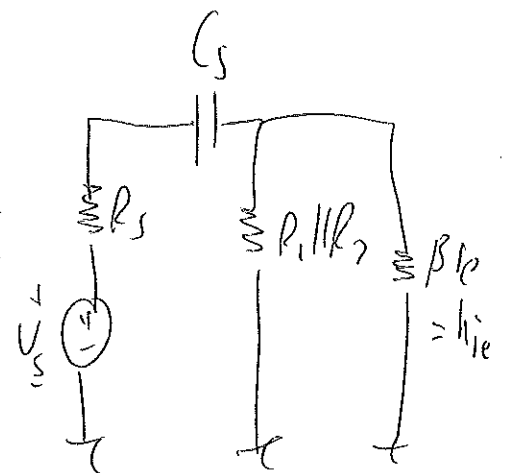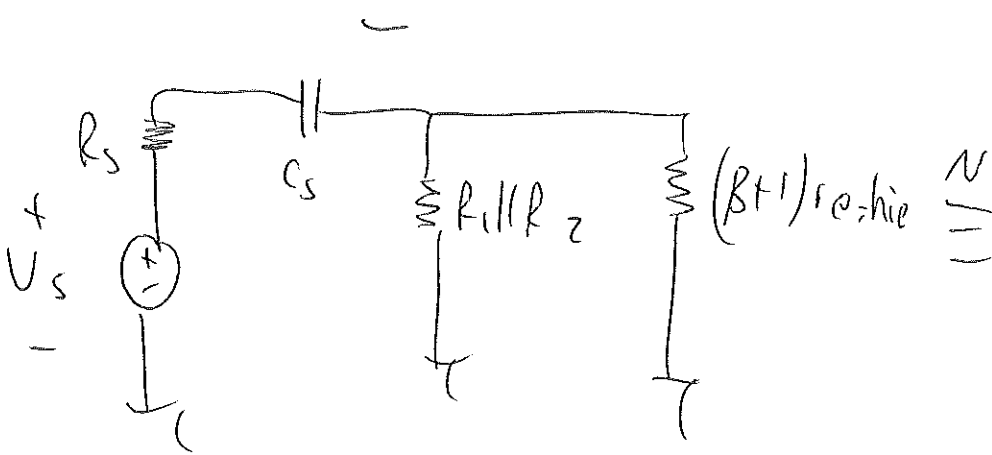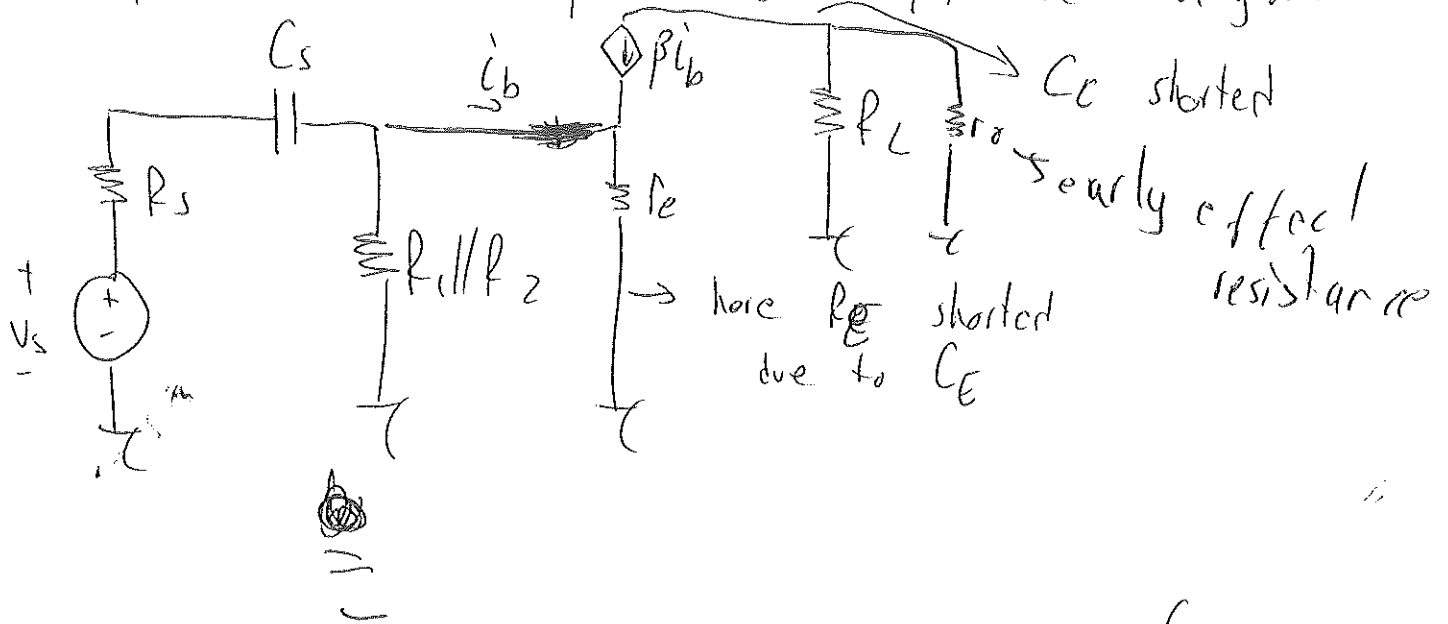While analysing the effects of C_s we assume C_E and C_C behave perfectly short circuit (since they are by-pass capacitors) using this hypothesis and putting ac equivalent network for transistor (npn) we nearly obtain





β is very large hence
 $\beta r_e \approx (\beta+1)r_e //$

* The value of R_i for $f_{L_s} = \frac{1}{2\pi(R_s + R_i)C_s}$ is $R_i = R_1 \parallel R_2 \parallel (\beta + 1)r_e \approx R_1 \parallel R_2 \parallel \beta r_e$

$C_c \rightarrow$ collector coupling capacitor (connected between output of active device and applied load)

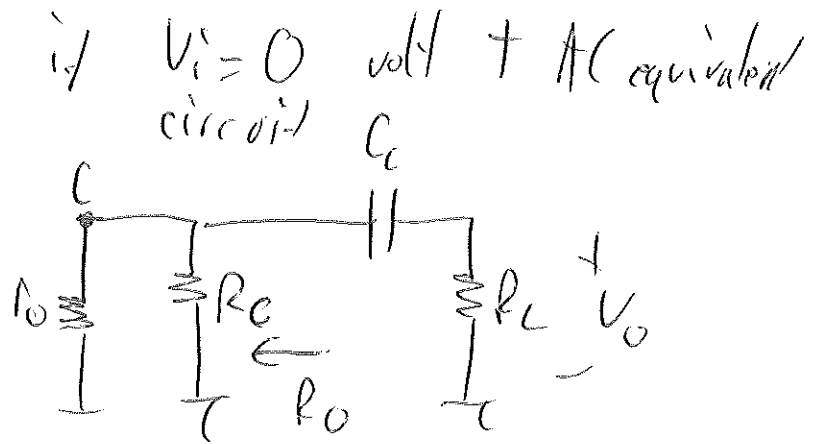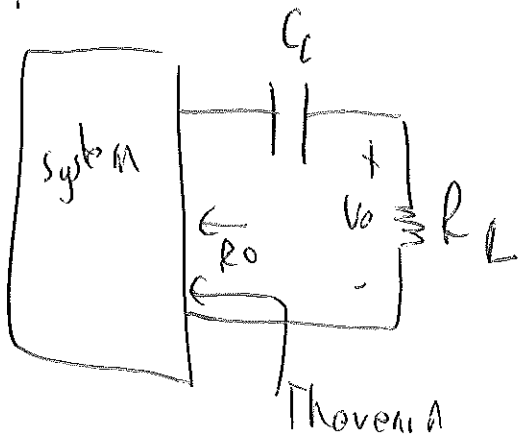hence f_{L_c} (low cut-off frequency due to C_c) has following circuit characteristics



$$f_{L_c} = \frac{1}{2\pi(R_o \parallel R_L)C_c}$$

cut off frequency due to C_c



$$R_o = R_c \parallel R_o$$

To determine f_{LE} → The cut-off frequency due to C_E

$$f_{LE} = \frac{1}{2\pi R_o C_E}$$


↓
cut-off frequency due to C_E

The circuit to obtain R_o

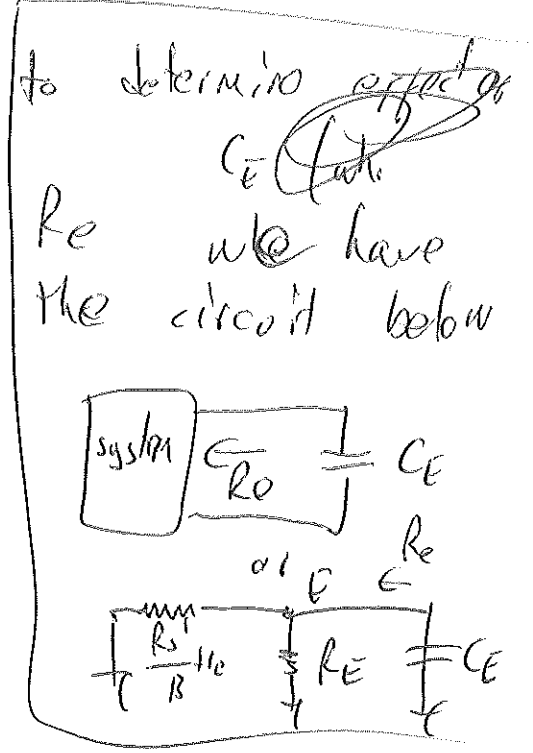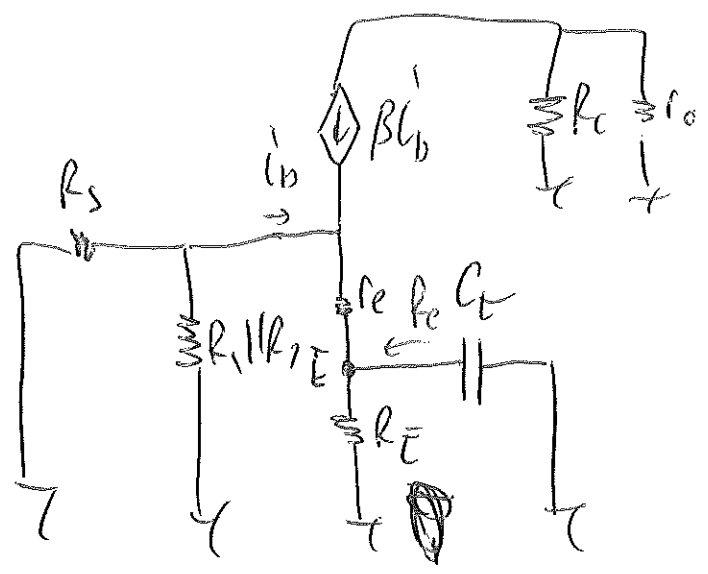

$$R_s' = R_s // R_1 // R_2$$
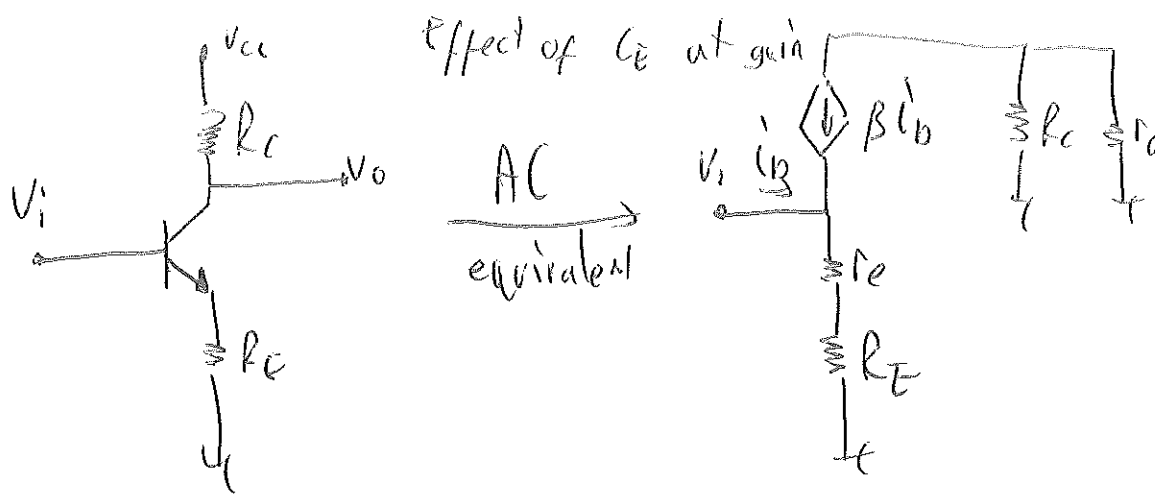
$$R_o = R_E // \left[\frac{R_s'}{(B+1)} + r_e \right] = R_E // \left[\frac{R_s'}{B} + r_e \right]$$



$$A_v = \text{Gain} = \frac{-\beta(R_C \parallel r_o)}{(\beta+1)(r_e + R_E)} \approx \frac{-R_C}{r_e + R_E}$$


if $R_E = 0$ $A_v = \text{Gain} \approx \frac{-R_C}{r_e}$ (nearly maximum gain)

At low frequencies bypass capacitor C_E is open-circuit and for gain we use $A_v = \frac{-R_C}{r_e + R_E} \rightarrow$ (minimum gain)


As frequency increases reactance of C_E decreases reducing parallel impedance of R_E and C_E until the resistor R_E is effectively shorted out by C_E that results in maximum midband gain $A_v \approx \frac{-R_C}{r_o}$

at f_{L_E} the gain will be 3dB below the midband gain with R_E "shorted out"

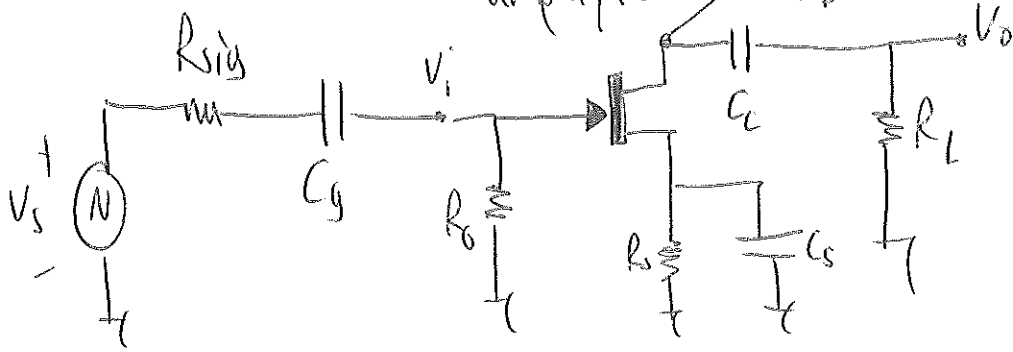Low frequency amplifier v_{DS} response of FET



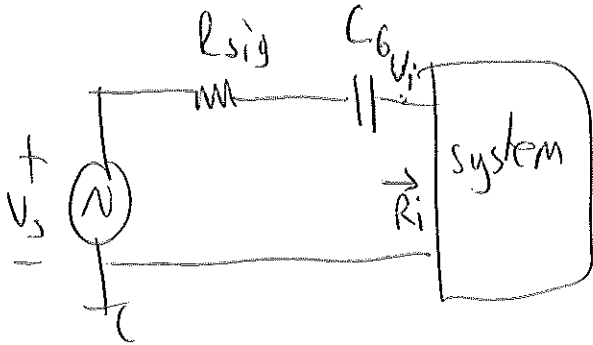For C_g circuit to determine effect of C_g on the low frequency response




$$f_{Lc} = \frac{1}{2\pi (R_{sig} + R_i) C_g}$$

$$R_i = R_D \left[\begin{array}{l} \text{due to} \\ \text{ac analysis} \end{array} \right]$$

generally $R_D \gg R_{sig}$

since R_i is large f_{Lc} is small

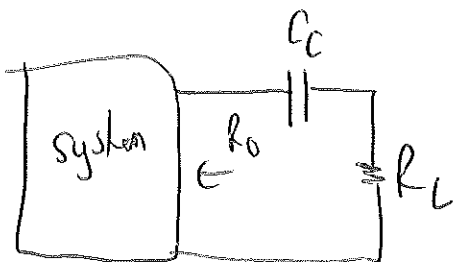For C_c circuit to determine effect of C_c on low-frequency response



$$f_{Lc} = \frac{1}{2\pi (R_o + R_L) C_c}$$

$$R_o = R_D // r_d$$


C_s = Effect of C_s on the low frequency response



$$R_{eq} = \frac{R_s}{1 + R_s (1 + g_m r_d) / (r_d + R_D \parallel R_L)}$$

if $r_d \rightarrow \infty$ $R_{eq} = R_s \parallel \frac{1}{g_m}$

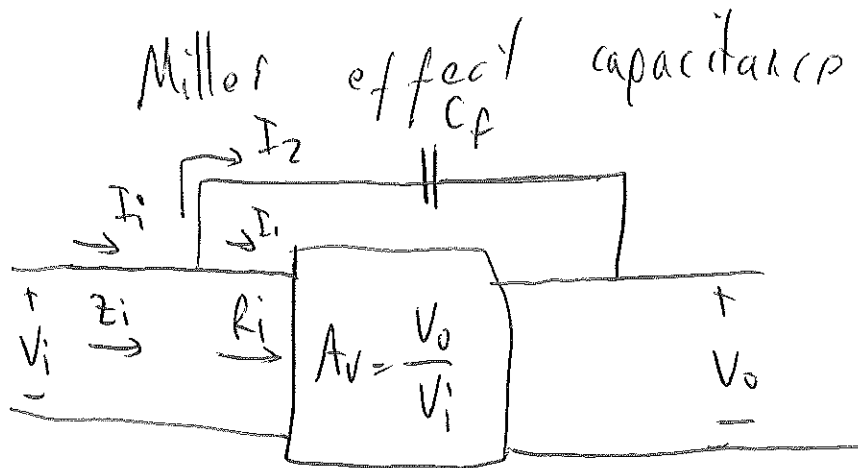check examples g.11 for low frequency response of BJT and g.12 for low frequency response of FET



$$I_i = I_1 + I_2 \quad I_i = \frac{V_i}{Z_i} \quad I_1 = \frac{V_i}{R_i}$$

$$I_2 = \frac{V_i - V_o}{X_{Cf}} = \frac{V_i - A_v V_i}{X_{Cf}} = \frac{(1 - A_v) V_i}{X_{Cf}}$$

$$\frac{V_i'}{Z_i} = \frac{V_i}{R_i} + \frac{(1-A_v)V_i}{X_{cf}}$$

$$X_{cf} = \frac{1}{\omega C_f}$$

$$\frac{1}{Z_i} = \frac{1}{R_i} + \frac{(1-A_v)}{X_{cf}}$$

$$\frac{1}{Z_i} = \frac{1}{R_i} + \frac{1}{\frac{X_{cf}}{(1-A_v)}}$$


$$\frac{X_{cf}}{1-A_v} = \frac{1}{\omega(1-A_v)C_f} = X_{CM}$$

$$\frac{1}{Z_i} = \frac{1}{R_i} + \frac{1}{X_{CM}}$$

Miller effect capacitors


$$C_{M_i} = (1-A_v)C_f$$

new model circuit

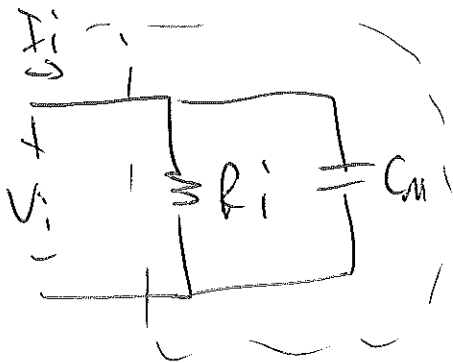

$$C_M = (1-A_v)C_f$$

Miller output capacitance

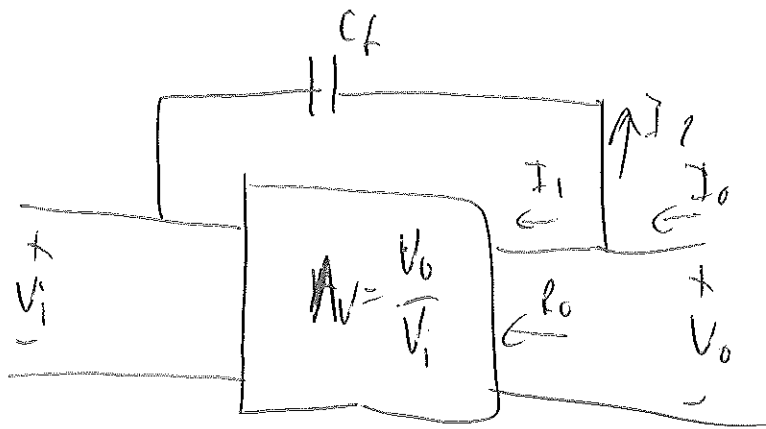

$$I_0 = \frac{V_o - \frac{V_o}{A_v}}{X_{Cf}} = \frac{V_o \left[1 - \frac{1}{A_v} \right]}{X_{Cf}}$$

$$\frac{I_0}{V_o} = \frac{1 - \frac{1}{A_v}}{X_{Cf}}$$

$$\frac{V_o}{I_0} = \frac{X_{Cf}}{1 - \frac{1}{A_v}} = \frac{1}{\omega C_f \left(1 - \frac{1}{A_v} \right)}$$

$$= \frac{1}{\omega C_{M_0}}$$

Miller output capacitance

$$C_{M_0} = \left(1 - \frac{1}{A_v} \right) C_f$$

if $A_v \gg 1$ $C_{M_0} \approx C_f$