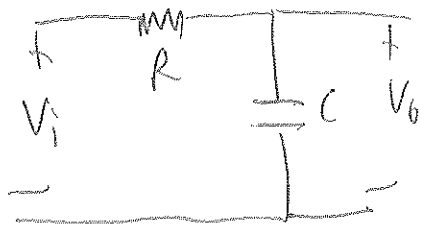


High Frequency Response of -BJT amplifier

At high-frequency there are two factors that define the [3dB] cut-off points (nearly the half-power frequency)

- 1- The network capacitance (parasitic and introduced)
- 2- The frequency dependence of h_{fe} (β)


RC network in high frequency



$$G_{in} = \frac{V_o}{V_{in}} = \frac{1}{1 + j \frac{f}{f_2}} = \frac{1}{1 + \frac{j 2\pi f C}{R}} = \frac{1}{R + j 2\pi f C}$$


phase

phasor

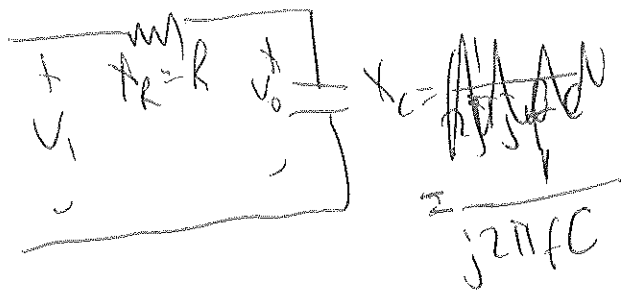


$$2\pi f C = \frac{1}{R} \Rightarrow 2\pi f_2 R C = \frac{1}{f_2}$$

$$f_2 = \frac{1}{2\pi R C}$$

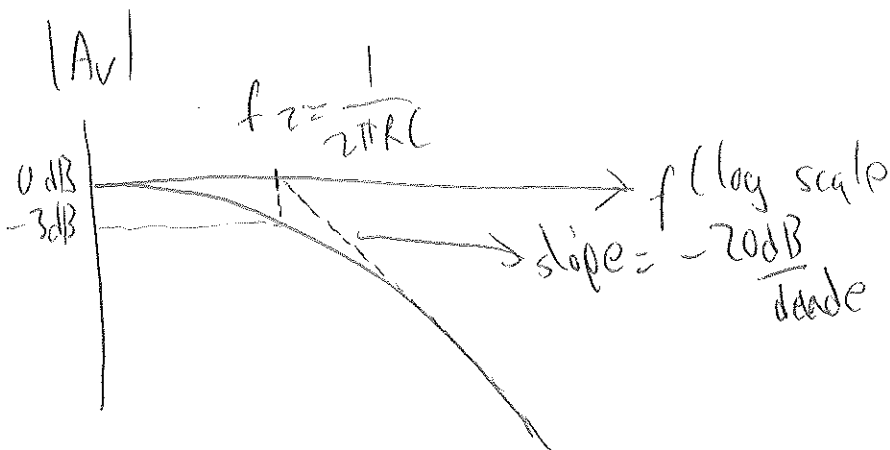

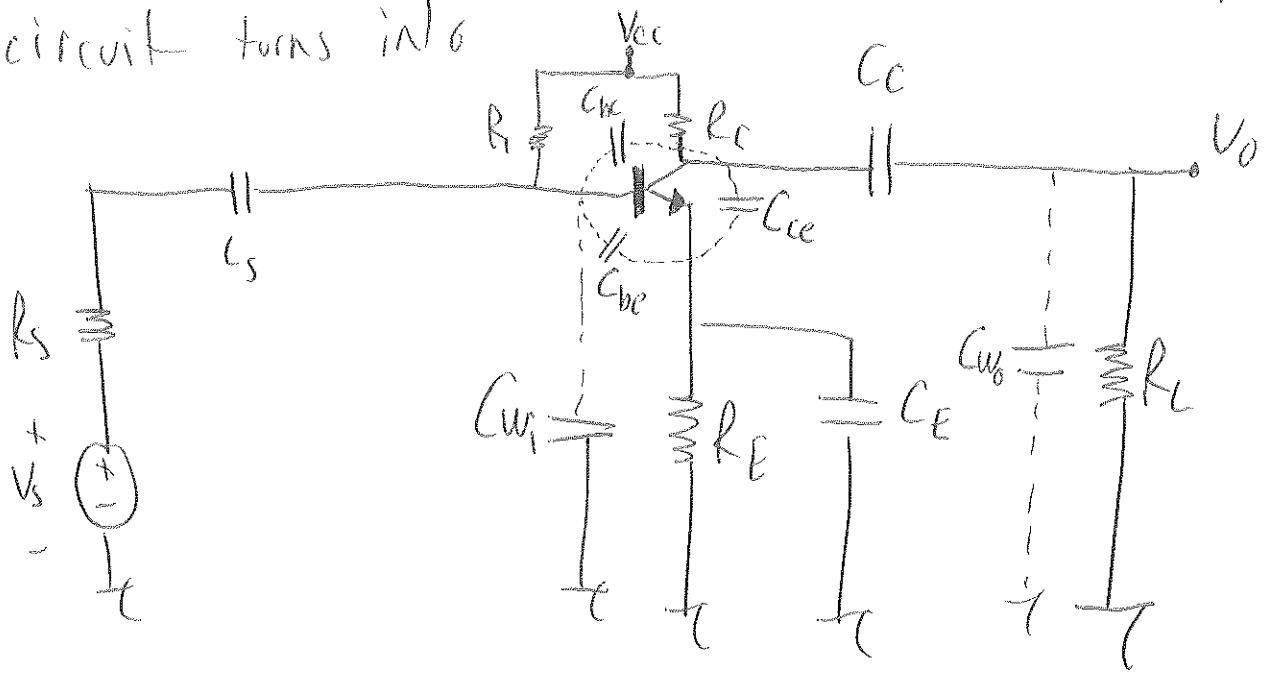
At high frequency various parasitic capacitances (C_{be} , C_{bc} , C_{ce}) of the transistor are ~~included~~ included with wiring capacitances (C_{wi} , C_{wo}) introduced during construction. Hence the ~~the~~ BJT amplifier circuit turns into



- C_{bc} → parasitic high frequency capacitance between base and collector
- C_{be} → " " " " " " base and emitter
- C_{ce} → " " " " " " collector and emitter

- C_{wi} → Capacitance due to wiring in the input part of transistor
- C_{wo} → " " " " " " output part of transistor

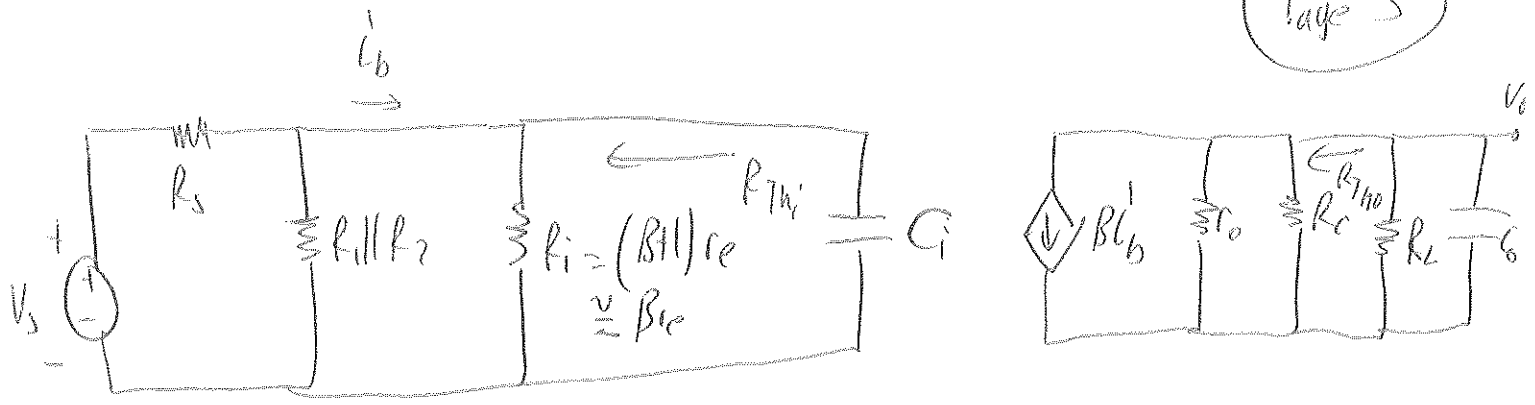In high frequency C_s , C_c and C_E are shorted. Due to these capacitive effects at high frequency the ~~linear~~ equivalent circuit model of the circuit becomes



where


$$C_i = C_{w_i} + C_{be} + C_{M_i} \quad \text{and} \quad C_o = C_{w_o} + C_{ce} + C_{M_o}$$

C_i includes: input wiring capacitance C_{w_i} , the transition capacitance C_{be} and the miller capacitance C_{M_i}

C_o includes: output wiring capacitance C_{w_o} , the parasitic capacitance C_{ce} , and the output miller capacitance C_{M_o}

To order parasitic capacitances $C_{be} > C_{bc} > C_{ce}$

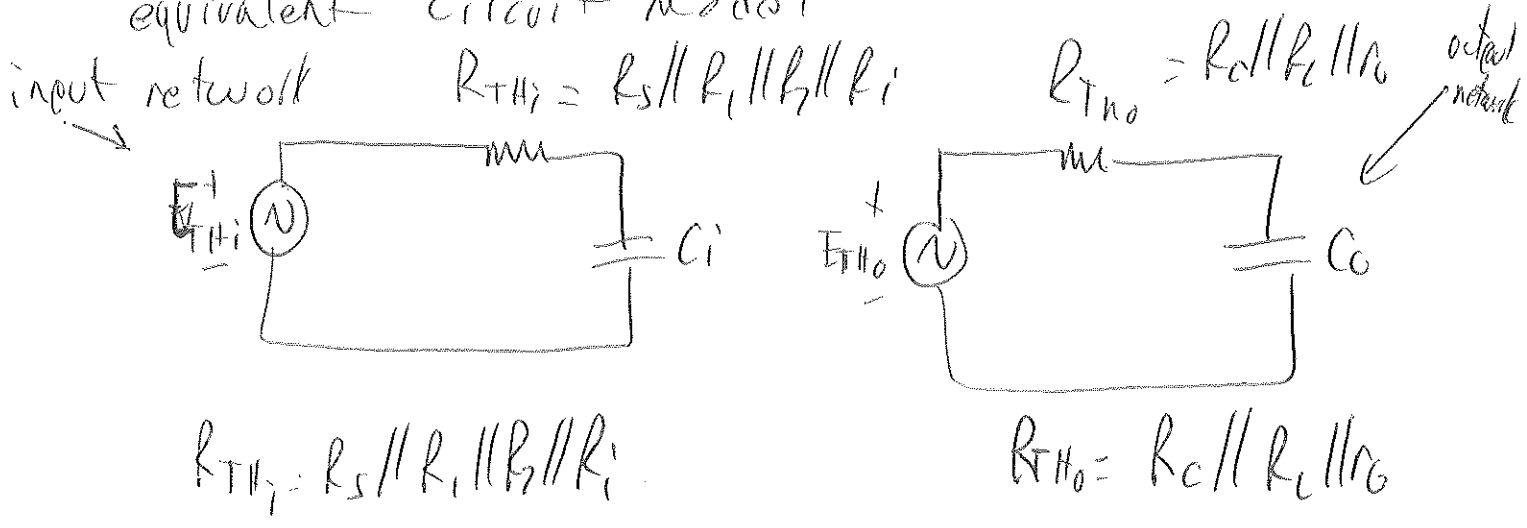The Thevenin equivalent circuit of equivalent circuit model



For the input network part -3dB frequency is defined by

$$f_{Hi} = \frac{1}{2\pi R_{THi} C_i} \rightarrow \text{high input part cut-off frequency}$$

and $C_i = C_{w_i} + C_{c_{ot}} + C_{M_i} = C_{w_i} + C_{c_{ot}} + (1 - A_v) C_{bc}$

For the output network

$$f_{Ho} = \frac{1}{2\pi R_{THo} C_o} \rightarrow \text{high output part cut-off frequency}$$

with $R_{THo} = R_c \parallel R_L \parallel R_o$

$$C_o = C_{w_o} + C_{c_{ot}} + C_{M_o} = C_{w_o} + C_{c_{ot}} + \left(1 - \frac{1}{A_v}\right) C_{bc}$$

since $\frac{1}{A_v} \ll 1$

$$C_o \approx C_{w_o} + C_{c_{ot}} + C_{bc}$$

At high frequencies C_o will decrease and consequently reduce to impedance of output parallel branches

Hence V_o will become zero as $f \rightarrow \infty$, since the reactance of C_{bc} becomes smaller.


The lowest of f_{Hi} and f_{Ho} is the actual ~~cut-off~~ cut-off frequency of the network at high frequencies

h_{fe} (or β) variation

$$h_{fe} = \frac{h_{fe_{mid}}}{1 + j\left(\frac{f}{f_{\beta}}\right)} \rightarrow \text{nearly this equality will hold with increasing frequency}$$

The use of h_{fe} rather than β is due to the fact that manufacturers typically use the hybrid parameters.

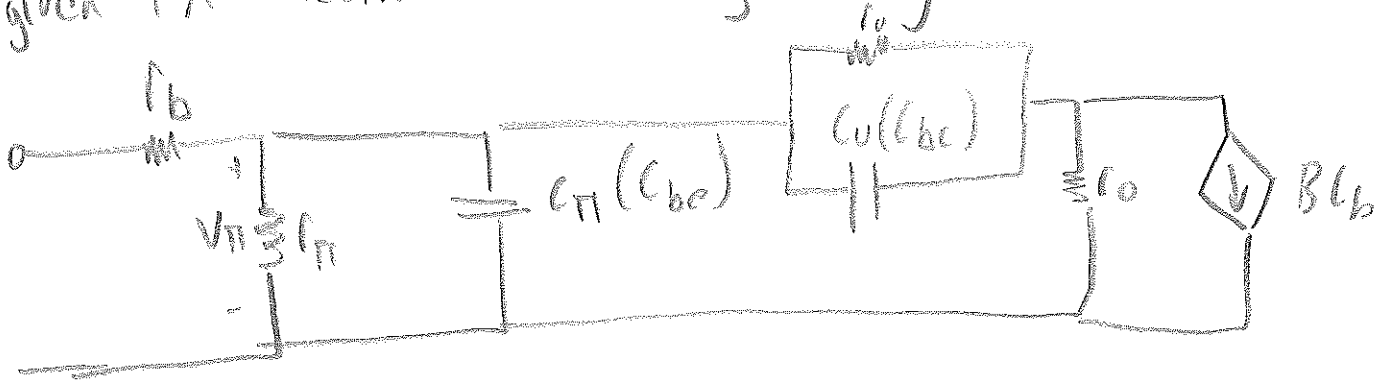Hybrid Π or Giocolotto model
 (given in Section 5.2.2 Boylestad)




f_{β} (sometimes appearing as $f_{\beta fo} = \frac{1}{2\pi r_{\pi} (C_{\pi} + C_{\mu})}$)

as $r_{\pi} = \beta I_{E} = h_{fe} I_{E}$

$$f_{\beta} = \frac{1}{h_{fe} I_{E} (2\pi) r_e (C_{\pi} + C_{\mu})}$$

$$f_{\beta} \approx \frac{1}{2\pi \beta_{mid} I_{E} (C_{\pi} + C_{\mu})}$$

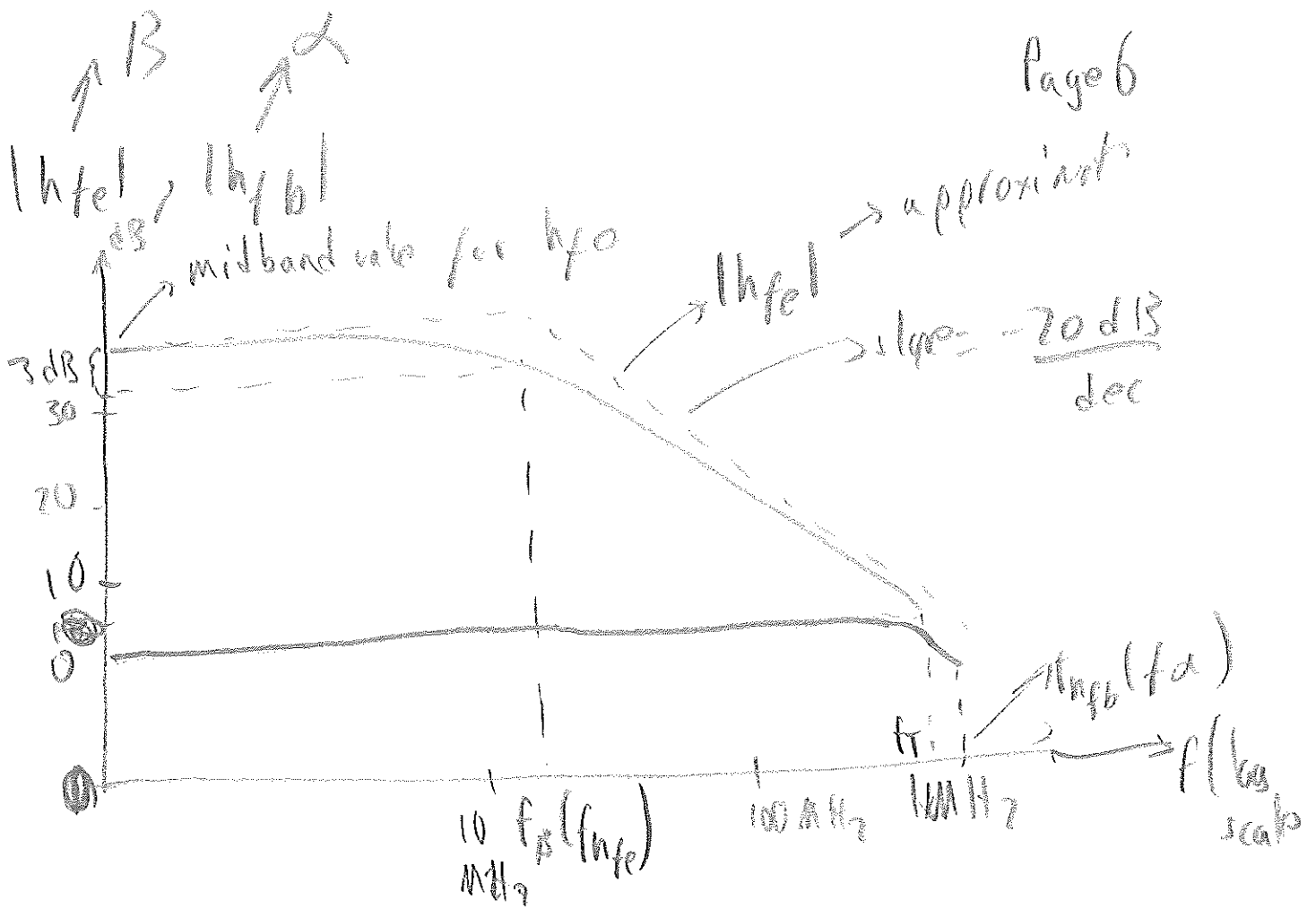Since r_e is a function of the network design,
 f_{β} is a function of the bias configuration



$$f_{\beta} = f_{\alpha} (1 - \alpha)$$

$$f_T = h_{fe_{mid}} f_{\beta}$$

$$f_T = \beta_{mid} f_{\beta}$$

$$f_{\beta} = \frac{f_T}{\beta_{mid}}$$

$$f_T \approx \beta_{mid} \frac{1}{2\pi \beta_{mid} (C_{in} + C_u) \omega}$$

$$f_T = \frac{1}{2\pi C_u (C_{in} + C_u)}$$