

Name _____

Date _____

Instructor _____

EXPERIMENT
21

Multistage Amplifiers: *RC* Coupling

OBJECTIVE

To measure DC and AC voltages in a multistage FET amplifier. To obtain measured values of voltage amplification (A_v), input impedance (Z_i), and output impedance (Z_o).

EQUIPMENT REQUIRED

Instruments

Oscilloscope
DMM
Function generator
DC supply

Components

Resistors

(2) 510- Ω
(1) 1-k Ω
(2) 2.4-k Ω
(1) 10-k Ω
(3) 1-M Ω

Capacitors

(3) 15- μ F
(2) 100- μ F

Transistors

(2) 2N3823, or equivalent

EQUIPMENT ISSUED

Item	Laboratory serial no.
DC power supply	
Function generator	
Oscilloscope	
DMM	

RÉSUMÉ OF THEORY

The DC bias of a JFET is determined by the device transfer characteristic (V_P and I_{DSS}) and the external circuit connected to it. The AC voltage gain at this DC bias point is then dependent on the device parameters (g_m or g_{fs}) and circuit drain resistance.

AC Voltage Gain: The voltage gain of an amplifier stage as in Fig. 21.1 can be calculated from

$$A_v = \frac{V_o}{V_i} = -g_m R_D = -g_m (R_D || R_L) \quad (21.1)$$

where

$$g_m = g_{m0} \left(1 - \frac{V_{GSQ}}{V_P} \right) \quad \text{with } g_{m0} = \frac{2I_{DSS}}{|V_P|} \quad (21.2)$$

AC Input Impedance: The AC input impedance is

$$Z_i = R_G \quad (21.3)$$

AC Output Impedance: The AC output impedance is

$$Z_o = R_D \quad (21.4)$$

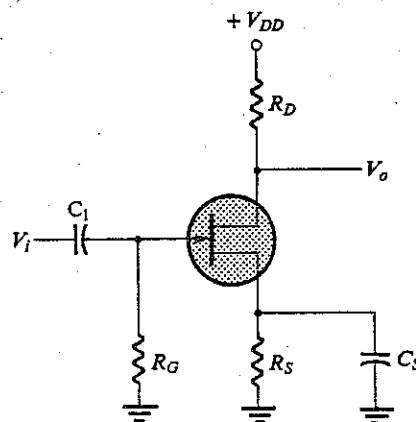


Figure 21-1

PROCEDURE

Part 1. Measurement of I_{DSS} and V_P

It is necessary to obtain values of I_{DSS} and V_P for both Q_1 and Q_2 . Use a characteristic curve tracer, if available, to determine the values of I_{DSS} and V_P . Obtain readings at $V_{DS} = +10$ V.

For Q_1 :

$I_{DSS} =$ _____
 $V_P =$ _____

For Q_2 :

$I_{DSS} =$ _____
 $V_P =$ _____

Go on to Part 2.

Otherwise, use the following steps to obtain these values.

- a. Construct the circuit of Fig. 21.2 with $R_D = 510 \Omega$ but with $R_S = 0 \Omega$. Measure and record.

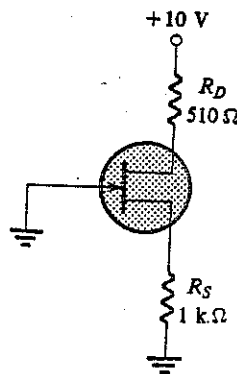


Figure 21-2

V_D (measured) = _____

Calculate the value of drain current, I_D .

$$I_D = \frac{V_{DD} - V_D}{R_D}$$

I_D (calculated) = _____
 since this is the drain current at $V_{GS} = 0$ V

$I_{DSS}(Q_1) = I_D =$ _____
 (using the value of I_D just calculated).

Replace Q_1 and repeat measurement with Q_2 .

V_D (measured) = _____
 Calculate the value of drain current, I_D

$$I_D = \frac{V_{DD} - V_D}{R_D}$$

I_D (calculated) = _____
 since this is the drain current at $V_{GS} = 0$ V

$I_{DSS}(Q_2) = I_D =$ _____
 (using the value of I_D just calculated).

b. Now connect $R_S = 1 \text{ k}\Omega$. Measure and record the values of

$$V_{GS} \text{ (measured)} = \underline{\hspace{2cm}}$$

$$V_D \text{ (measured)} = \underline{\hspace{2cm}}$$

Using the measured values just obtained, calculate V_P as follows.

$$I_D = \frac{V_{DD} - V_D}{R_D}$$

$$I_D \text{ (calculated)} = \underline{\hspace{2cm}}$$

$$V_P = \frac{V_{GS}}{1 - \sqrt{\frac{I_D}{I_{DSS}}}}$$

$$V_P(Q_2) \text{ (calculated)} = \underline{\hspace{2cm}}$$

Replace transistor Q_2 and repeat step 1(b) measurements.

$$V_{GS} \text{ (measured)} = \underline{\hspace{2cm}}$$

$$V_D \text{ (measured)} = \underline{\hspace{2cm}}$$

Using the measured values just obtained, calculate V_P as follows.

$$I_D = \frac{V_{DD} - V_D}{R_D}$$

$$I_D \text{ (calculated)} = \underline{\hspace{2cm}}$$

$$V_P = \frac{V_{GS}}{1 - \sqrt{\frac{I_D}{I_{DSS}}}}$$

$V_P(Q_1)$ (calculated) = _____

Part 2. DC Bias of Common-Source Circuit

- a. Calculate the DC bias expected in the circuit of Fig. 21.3, using I_{DSS} and V_P obtained in Part 1 for each transistor.

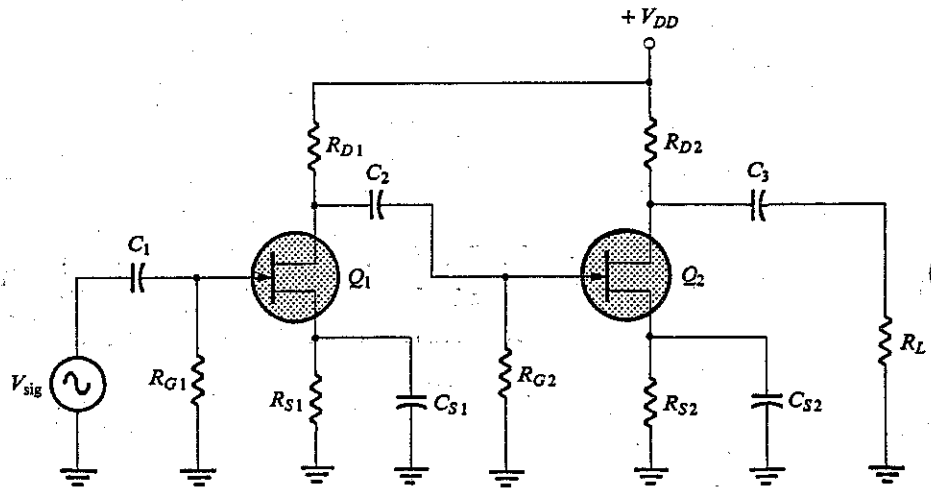


Figure 21-3

Draw graphs of the equations

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \text{ and } V_{GS} = -I_D R_S$$

to obtain the equations intersection.

Or use a computer or programmable calculator to solve the simultaneous equations.

The calculated DC bias values are:

V_{GS1} (calculated) = _____

using I_{D1} (calculated) = _____

$$V_{D1} = V_{DD} - I_{D1}R_{D1}$$

The calculated DC bias values are: V_{D1} (calculated) = _____

$$V_{GS2}$$
 (calculated) = _____

using I_{D2} (calculated) = _____

$$V_{D2} = V_{DD} - I_{D2}R_{D2}$$

$$V_{D2}$$
 (calculated) = _____

- b. Build the circuit of Fig. 21.3 using $R_{G1} = R_{G2} = 1 \text{ M}\Omega$, $R_{S1} = R_{S2} = 510 \Omega$, and $R_{D1} = R_{D2} = 2.4 \text{ k}\Omega$. Set $V_{DD} = +20 \text{ V}$.
- c. Measure the DC bias voltages.

$$V_{G1}$$
 (measured) = _____

$$V_{S1}$$
 (measured) = _____

$$V_{D1}$$
 (measured) = _____

$$V_{GS1}$$
 (measured) = _____

Calculate the value of I_D under DC bias conditions (using nominal resistor values)

$$I_{D1} = \frac{V_{S2}}{R_{S2}}$$

$$I_{D1}$$
 = _____
 V_{G2} (measured) = _____
 V_{S2} (measured) = _____
 V_{D2} (measured) = _____
 V_{GS2} (measured) = _____

Calculate the value of I_{D_2} under DC bias conditions

$$I_{D_2} = \frac{V_{S1}}{R_{S1}}$$

$$I_{D_2} = \underline{\hspace{2cm}}$$

Compare the DC bias values calculated in step 2(a) with those measured in step 2(c).

Part 3. AC Voltage Gain of Amplifier

- a. Calculate the voltage gain of the common-source amplifier of Fig. 21.3.

For stage 2:

$$A_{v_2} = -g_m(R_{D2} || R_L)$$

$$\text{with } g_m(Q_2) = \frac{2I_{DSS}(Q_2)}{|V_p(Q_2)|} \left(1 - \frac{V_{GS_2}}{V_p(Q_2)} \right)$$

Using $V_p(Q_2)$, $I_{DSS}(Q_2)$ from Part 1, and V_{GS_2} calculated in Part 2

$$A_{v_2} \text{ (calculated)} = \underline{\hspace{2cm}}$$

For stage 1:

$$A_{v_1} = -g_{m_1}(R_{D1} || Z_{i_2})$$

$$\text{with } g_m(Q_1) = \frac{2I_{DSS}(Q_1)}{|V_p(Q_1)|} \left(1 - \frac{V_{GS_1}}{V_p(Q_1)} \right)$$

Using $V_p(Q_1)$, $I_{DSS}(Q_1)$ from Part 1, and V_{GS_1} calculated in Part 2

$$A_{v_1} \text{ (calculated)} = \underline{\hspace{2cm}}$$

Calculate the overall amplifier gain:

$$A_v = A_{v1} \times A_{v2}$$

$$A_v \text{ (calculated)} = \underline{\hspace{2cm}}$$

- b. Connect input of $V_{\text{sig}} = 10 \text{ mV}$, rms at $f = 1 \text{ kHz}$. Use the oscilloscope to obtain an undistorted output voltage, adjusting V_{sig} if necessary. Measure and record:

$$V_{\text{sig}} \text{ (measured)} = \underline{\hspace{2cm}}$$

$$V_L \text{ (measured)} = \underline{\hspace{2cm}}$$

Calculate the voltage gain of the overall amplifier

$$A_v = \frac{V_L}{V_{\text{sig}}}$$

$$A_v = \underline{\hspace{2cm}}$$

Measure and record:

$$V_{o1} \text{ (measured)} = \underline{\hspace{2cm}}$$

Calculate the gain of each stage:

$$A_{v1} = \frac{V_{o1}}{V_{\text{sig}}}$$

$$A_{v1} \text{ (calculated)} = \underline{\hspace{2cm}}$$

$$A_{v_2} = \frac{V_L}{V_{o1}}$$

$$A_{v_2} \text{ (calculated)} = \underline{\hspace{2cm}}$$

Part 4. Input and Output Impedance Measurements

- a. The input impedance is

$$Z_i = R_{G1}$$

$$Z_i = \underline{\hspace{2cm}}$$

- b. The output impedance is

$$Z_o = R_{D2}$$

$$Z_o = \underline{\hspace{2cm}}$$

- c. Connect a 1-M Ω resistor, R_x in series with the input signal, $V_{sig} = 10$ mV, rms at $f = 100$ Hz. Measure V_{i1} .

$$V_{i1} \text{ (measured)} = \underline{\hspace{2cm}}$$

Calculate the input impedance using

$$Z_i = \frac{V_{i1}}{V_{sig} - V_{i1}} R_x$$

$$Z_i = \underline{\hspace{2cm}}$$

Remove measurement resistor, R_x .

d. Measure V_L

V_L (measured) = _____
Disconnect load $R_L = 10 \text{ k}\Omega$. Measure output voltage, V_o .

V_o (measured) = _____
Calculate the AC output impedance using

$$Z_o = \frac{V_o - V_{i1}}{V_L} R_L$$

$Z_o =$ _____

Compare the input impedance calculated in step 4(a) with that determined from measurements in step 4(c).

Compare the output impedance calculated in step 4(b) with that determined from measurements in step 4(d).