

Name \_\_\_\_\_  
Date \_\_\_\_\_  
Instructor \_\_\_\_\_

EXPERIMENT  
**30**

# Comparator Circuits Operation

## OBJECTIVE

*To measure DC and AC operation using comparator IC circuits.*

## EQUIPMENT REQUIRED

### Instruments

Oscilloscope  
DMM  
Function generator  
DC power supply

### Components

#### *Resistors*

(1) 1-k $\Omega$   
(1) 3.3-k $\Omega$   
(3) 10-k $\Omega$   
(1) 20-k $\Omega$   
(3) 100-k $\Omega$   
(1) 50-k $\Omega$  potentiometer

#### *Capacitors*

(2) 15- $\mu$ F  
(1) 100- $\mu$ F

**Transistors and ICs**

- (1) 2N3904
- (1) 741 Op-amp IC (or equivalent)
- (1) 339 Comparator IC (or equivalent)
- (1) LED (20 mA)

**EQUIPMENT ISSUED**

Item	Laboratory serial no.
DC power supply	
Function generator	
Oscilloscope	
DMM	

**RÉSUMÉ OF THEORY**

A comparator circuit is essentially a very high gain op-amp having a plus (+) and a minus (-) input. The output of the comparator is a logic level that provides an indication of when the plus input voltage is greater than the minus input or when the plus input is less than the minus input. Although an op-amp can be used for this purpose, special comparator ICs are available which are better suited for this operation.

Figure 30.1 shows a 741 op-amp used as a level detector. The reference level voltage  $V_{ref}$  is set at +5 V. The indicator LED goes on whenever the input  $V_i$  goes below  $V_{ref}$  and goes off whenever  $V_i$  goes above  $V_{ref}$ . Figure 30.2 shows a similar operation using a 339 comparator IC.

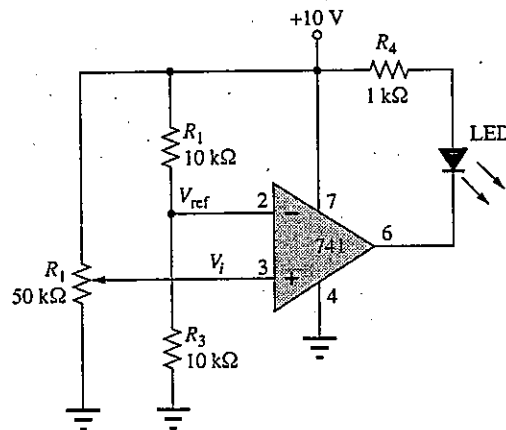


Figure 30-1

Figure 30.3 shows two comparator stages connected as a window detector—a circuit which provides indication of whenever the input voltage is within a specified range of voltage.

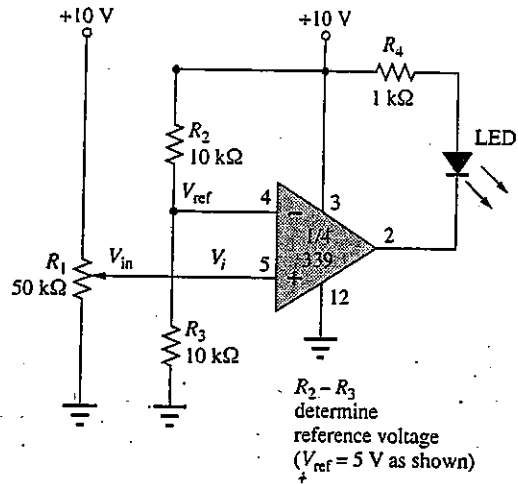


Figure 30-2

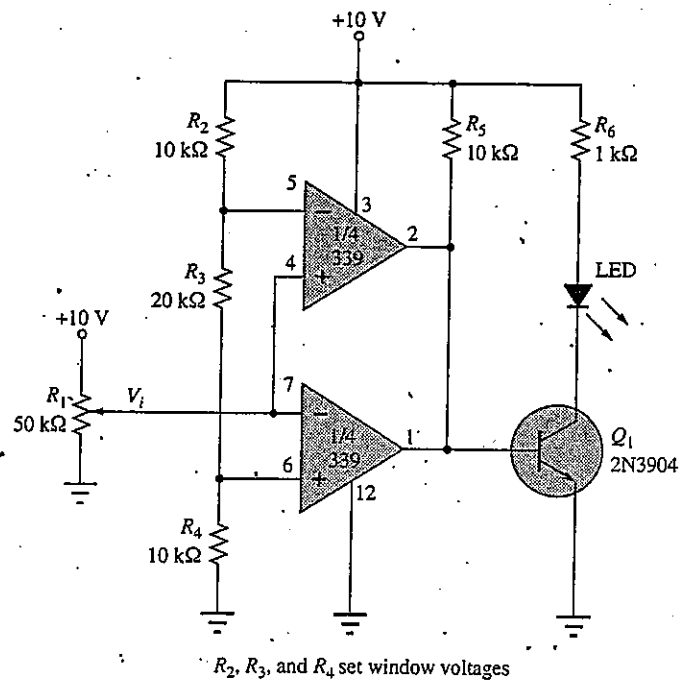


Figure 30-3

**PROCEDURE**

**Part 1. Comparator with 741C Used as a Level Detector**

- a. For the circuit of Fig. 30.1 verify that  $V_{ref} = 5\text{ volts}$ .

$V_{ref}$  (verified) = \_\_\_\_\_ ( $R_3 = 10\text{ k}\Omega$ )

- b. Construct the circuit of Fig. 30.1. (Measure and record resistor values in Fig. 30.1.)

- c. Using a DMM measure the reference voltage,  $V_{\text{ref}}$ .

$$V_{\text{ref}}(\text{measured}) = \underline{\hspace{2cm}}$$

- d. Adjust potentiometer  $R_1$  so that the LED just goes *on*\*, and then just goes *off*. Record the voltage  $V_i$  for each condition.

$$V_i(\text{measured}) (\text{LED goes on}) = \underline{\hspace{2cm}}$$

$$V_i(\text{measured}) (\text{LED goes off}) = \underline{\hspace{2cm}}$$

- e. Replace  $R_3$  with a 20-k $\Omega$  resistor and repeat steps 1(b) and 1(c).

$$V_{\text{ref}}(\text{measured}) = \underline{\hspace{2cm}}$$

$$V_i(\text{measured}) (\text{LED goes on}) = \underline{\hspace{2cm}}$$

$$V_i(\text{measured}) (\text{LED goes off}) = \underline{\hspace{2cm}}$$

Compare the values of  $V_{\text{ref}}$  calculated in step 1(a) with those measured in steps 1(c) and 1(e).

---

\*The potentiometer could be replaced by a rectified triangular wave at 100 Hz to provide the  $V_i$  input. The  $V_i$  signal and comparator  $V_o$  can then be observed simultaneously on the oscilloscope.

**Part 2. Comparator with 1/4 339IC Used as Level Detector**

- a. For the circuit of Fig. 30.2 calculate  $V_{ref}$ .

$$V_{ref}(\text{calculated}) = \underline{\hspace{2cm}} \quad (R_3 = 10 \text{ k}\Omega)$$

Repeat the calculation for  $R_3 = 20 \text{ k}\Omega$ .

$$V_{ref}(\text{calculated}) = \underline{\hspace{2cm}} \quad (R_3 = 20 \text{ k}\Omega)$$

- b. Construct the circuit of Fig. 30.2. (Measure and record resistor values in Fig. 30.2.)

- c. Using a DMM measure the reference voltage.

$$V_{ref}(\text{measured}) = \underline{\hspace{2cm}} \quad (R_3 = 10 \text{ k}\Omega)$$

- d. Adjust potentiometer  $R_1$  so that the LED just goes *on*\* and also just goes *off*. Measure the input voltage for each condition.

$$V_i(\text{measured}) = \underline{\hspace{2cm}} \quad (\text{LED goes on})$$

$$V_i(\text{measured}) = \underline{\hspace{2cm}} \quad (\text{LED goes off})$$

- e. Replace  $R_1$  with a 20-k $\Omega$  resistor. Repeat steps c and d.

$$V_{ref}(\text{measured}) = \underline{\hspace{2cm}} \quad (R_3 = 20 \text{ k}\Omega)$$

$$V_i(\text{measured}) = \underline{\hspace{2cm}} \quad (\text{LED goes on})$$

$$V_i(\text{measured}) = \underline{\hspace{2cm}} \quad (\text{LED goes off})$$

---

\*see footnote on page 322.

- f. Interchange connections at pins 4 and 5 so that  $V_i$  goes to the *minus* input and  $V_{ref}$  goes to the *plus* input. Repeat step 2(d).

$$V_i \text{ (measured)} = \underline{\hspace{2cm}} \text{ (LED goes on)}$$

$$V_i \text{ (measured)} = \underline{\hspace{2cm}} \text{ (LED goes off)}$$

Compare the calculated and measured voltages in steps 2(c) through 2(f) with that calculated in step 2(a).

### Part 3. Window Comparator

- a. For the circuit of Fig. 30.3 calculate  $V^+$  (pin 5) and  $V^-$  (pin 6).

$$V^+ \text{ (calculated) (pin 5)} = \underline{\hspace{2cm}}$$

$$V^- \text{ (calculated) (pin 6)} = \underline{\hspace{2cm}}$$

- b. Construct the circuit of Fig. 30.3. (Measure and record resistor values in Fig. 30.3.)

- c. Using a DMM measure the voltages at pins 1, 5, and 6.

$$V_i \text{ (measured) (pin 1)} = \underline{\hspace{2cm}}$$

$$V^+ \text{ (measured) (pin 5)} = \underline{\hspace{2cm}}$$

$$V^- \text{ (measured) (pin 6)} = \underline{\hspace{2cm}}$$

- d. Adjust  $V_i$  from 0 V to +10 V\*. Measure the voltage levels at which the LED goes *on* and then goes *off*.

$V_i$  (measured) = \_\_\_\_\_ (LED goes *on*)

$V_i$  (measured) = \_\_\_\_\_ (LED goes *off*)

- e. Adjust  $V_i$  from +10 V to 0 V. Measure the voltage levels at which the LED goes *on* and then goes *off*.

$V_i$  (measured) = \_\_\_\_\_ (LED goes *on*)

$V_i$  (measured) = \_\_\_\_\_ (LED goes *off*)

- f. Interchange resistors  $R_3$  and  $R_4$  and repeat step 3(d).

$V_i$  (measured) = \_\_\_\_\_ (LED goes *on*)

$V_i$  (measured) = \_\_\_\_\_ (LED goes *off*)

Compare the calculated values in step 3(a) with those measured in step 3(c).

---

\*see footnote on page 322.