

(1)

if  $S > V_{in}$   $V_x$  open circuit  
 if  $S < V_{in}$   $V_x = -9$  Volt

For IC399<sub>1</sub>  
 (upper IC)

if  $V_{in} > -S$   $V_x$  open circuit  
 if  $V_{in} < -S$   $V_x = -9$  Volt

For IC399<sub>2</sub>  
 (lower IC) → (2)

when  $-5 < V_{in} < 5$   $V_x$  open from both IC  
 if  $V_x$  is opens for Bot IC 399 then  $V_x = 9$  Volt


if  $S < V_{in}$   $V_x = -9$   
 if  $-S < V_{in} < S$   $V_x = 9$   
 if  $V_{in} < -S$   $V_x = -9$

$$I_c = \frac{9 - (-9)}{5000 \Omega} = \frac{18}{5000 \Omega} = 3.6 \text{ mA}$$


$$I_c = 0$$

$$I_c = \frac{9 - (-9)}{5000 \Omega} = 3.6 \text{ mA}$$


(a)

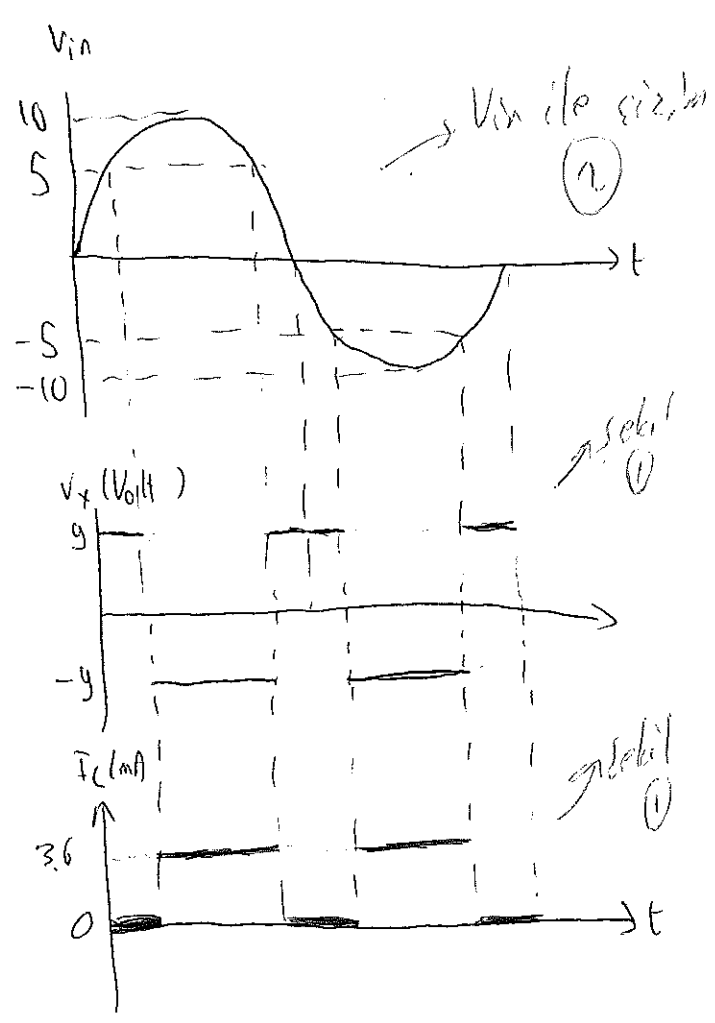

(b)

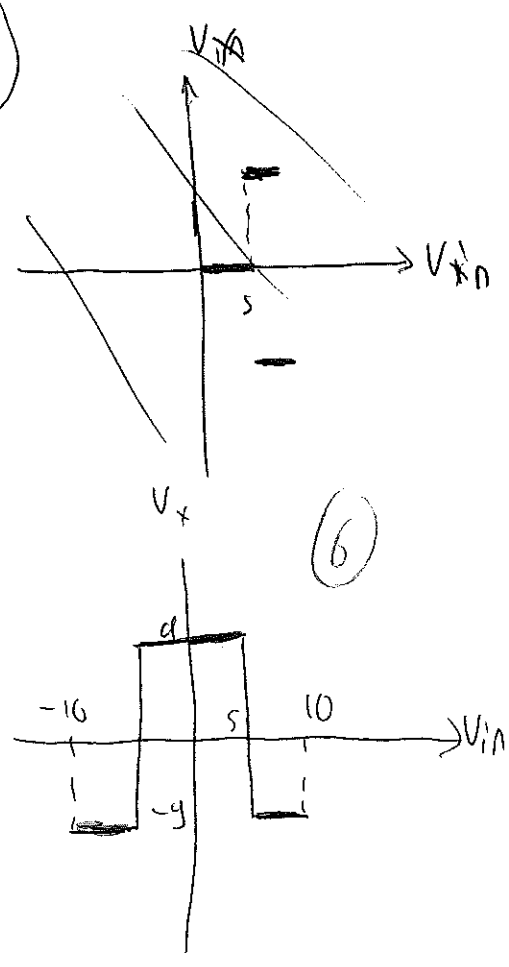

Q2

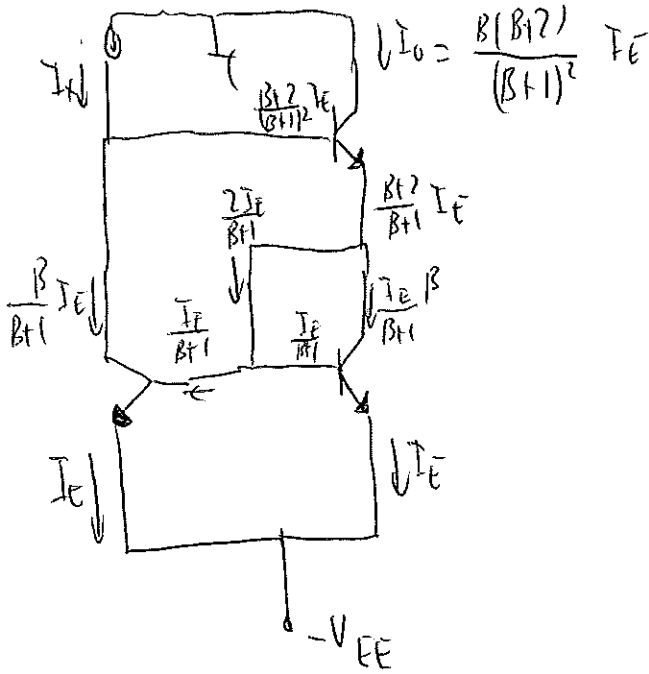

$$I_{O1} = \frac{B(B+2)}{(B+1)^2} I_E$$

gids 8

$$I_{X1} = \left( \frac{B+2}{(B+1)^2} + \frac{B}{(B+1)} \right) I_E$$


$$I_{X2} = \frac{B+2 + B(B+1)}{(B+1)^2} I_E$$

$$I_{X3} = \frac{B^2 + 2B + 2}{(B+1)^2} I_E$$

same 1

$$\frac{I_{O1}}{I_{X3}} = \frac{\frac{B(B+2)}{(B+1)^2}}{\frac{B^2 + 2B + 2}{(B+1)^2}} = \frac{B^2 + 2B}{B^2 + 2B + 2} = \frac{1}{1 + \frac{2}{B^2 + 2B}} = \frac{1}{1 + \frac{2}{B(B+2)}}$$

Q3

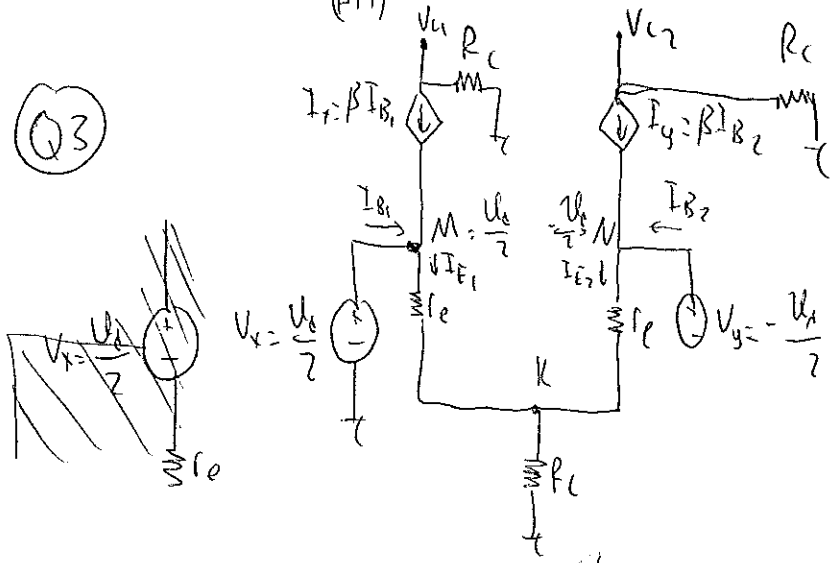

$$M = \frac{U_d}{2} \quad N = -\frac{U_d}{2}$$

$$\frac{M-k}{r_e} + \frac{N-k}{r_e} = \frac{k}{R_C} \quad \frac{U_d}{2} - k + \frac{-U_d}{2} - k = \frac{k}{R_C}$$

$$I_{E1} = \frac{\frac{U_d}{2} - k}{r_e} = \frac{U_d}{2r_e} \quad I_{B1} = \frac{U_d}{2r_e(\beta+1)}$$

$$I_{C1} = \frac{\beta U_d}{2r_e(\beta+1)} \quad 0 \rightarrow k=0$$

$$U_{C1} = -R_C [I_{C1}] = -R_C \left( \frac{\beta U_d}{(\beta+1) 2r_e} \right)$$

$$I_{E2} = \frac{-\frac{U_d}{2} - k}{r_e} = -\frac{U_d}{2r_e} \quad I_{B2} = -\frac{U_d}{2r_e(\beta+1)}$$

$$I_{C2} = -\frac{\beta U_d}{2r_e(\beta+1)} \quad U_{C2} = -R_C I_{C2} = -R_C \left( -\frac{\beta U_d}{2r_e(\beta+1)} \right) = \frac{\beta R_C U_d}{2r_e(\beta+1)}$$

$$V_{c1} - V_{c2} = - \frac{R_c \beta V_d}{r_{ie} (\beta + 1)} - \left( \frac{R_c \beta V_d}{r_{ie} (\beta + 1)} \right)$$

$$V_{c1} - V_{c2} = - \frac{R_c \beta V_d}{r_{ie} (\beta + 1)} \quad (Q4) \quad (Q5)$$

$$\frac{V_{c1} - V_{c2}}{V_d} = \text{Gain}_{\text{-diff}} = - \frac{R_c \beta}{r_{ie} (\beta + 1)} \quad (Q4) \quad (Q5)$$

(Q4)  $V_{in} = V_i + V_f$  (3 marks)  $V_i A = V_o$   $V_o B = V_f$

$$V_{in} = \frac{V_o}{A} + V_o B$$

$$V_{in} = V_o \left[ \frac{1}{A} + B \right]$$

$$V_{in} = V_o \left[ \frac{1 + BA}{A} \right]$$

$$\frac{V_o}{V_{in}} = \frac{A}{1 + BA}$$

(Q5)  $V_f + V_{in} = V_{in}$   $V_{in} = V_i - V_f$   $V_i A = V_o$   $V_o B = V_f$




$$V_{in} = \frac{V_o}{A} - BV_o$$

$$V_{in} = V_o \left[ \frac{1}{A} - B \right] = V_o \left[ \frac{1 - AB}{A} \right]$$


$$\frac{V_o}{V_{in}} = \frac{A}{1 - AB}$$

Q6

# Silicon Controlled Rectifier

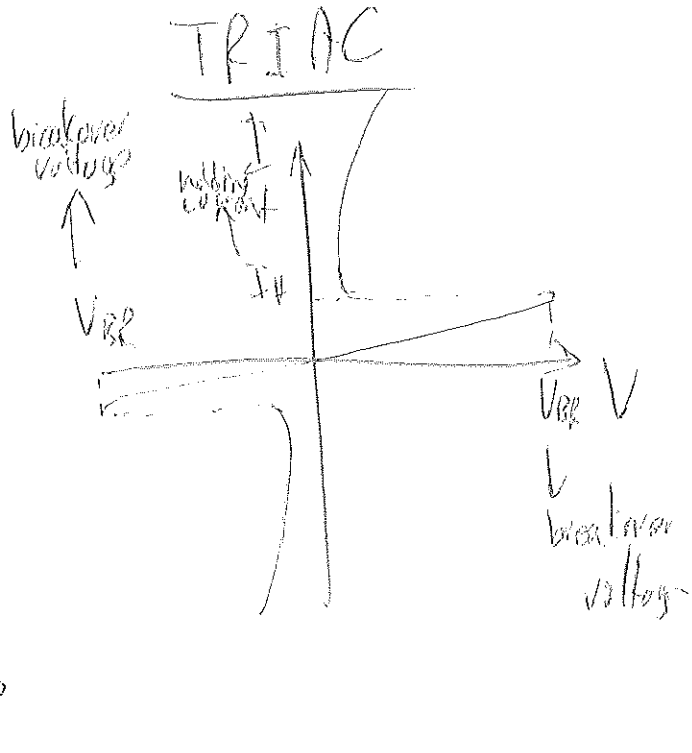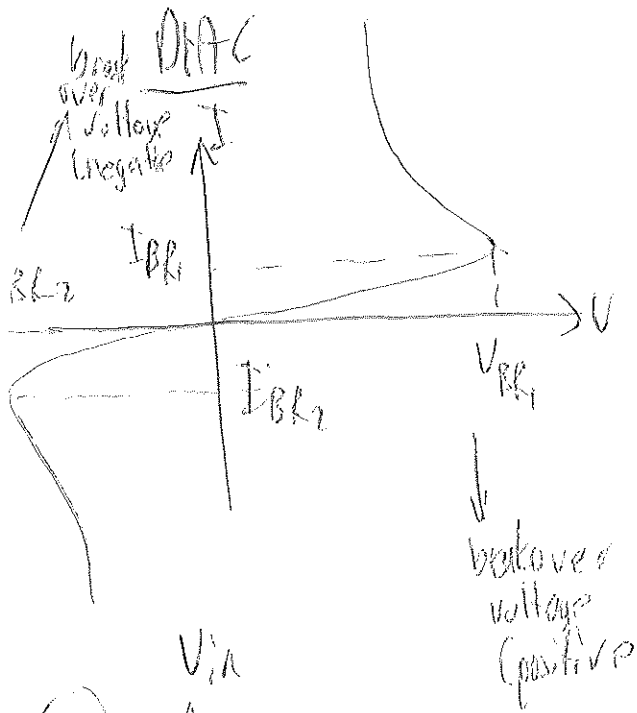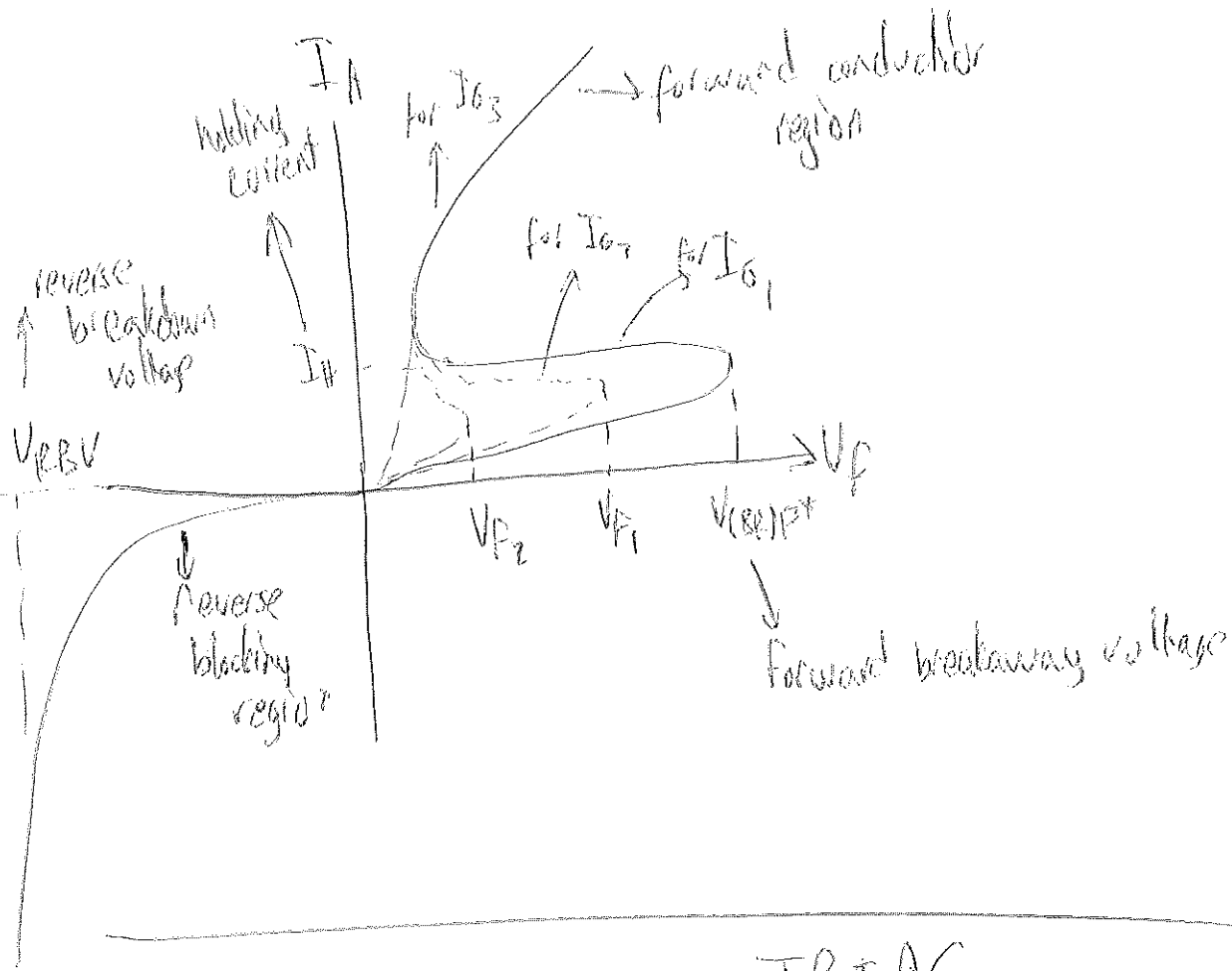

Q7

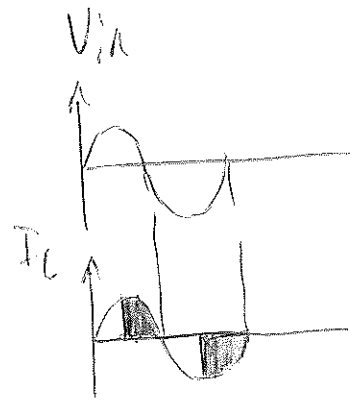

Q5  
 $V_i = V_{in} - V_f$

$$V_i = (B+1) I_b (1 + \beta R_E)$$

(a)  $\frac{V_o}{V_i} = \frac{R_E}{1 + \beta R_E} = A$   $V_f = -V_f$   
 10 points

$$\frac{V_o - V_f}{R_1} = \frac{V_f}{R_2} + I_{in} \quad (3)$$

$$\frac{V_o - V_f}{R_1} = \frac{V_f}{R_2} + \frac{V_i}{R_B} + I_B$$

$$\frac{V_o}{R_1} = V_f \left[ \frac{1}{R_1} + \frac{1}{R_2} \right] + \frac{V_i}{R_B} + \frac{V_i}{(B+1)(1 + \beta R_E)}$$

$$I_{in} = \frac{V_i}{R_B} + I_B \quad (2)$$

$$V_f = -V_o$$

$$V_i = \frac{1 + \beta R_E}{R_E} V_o$$

$$V_o = \frac{R_E}{1 + \beta R_E} V_i$$

$$\frac{V_o}{A} = V_i$$

$$\frac{V_o}{R_1} = -V_o \left[ \frac{R_1 + R_2}{R_1 R_2} \right] + V_i \left[ \frac{1}{R_B} + \frac{1}{(B+1)(1 + \beta R_E)} \right] \quad (1)$$

$$\frac{V_o}{R_1} = -V_o \left[ \frac{R_1 + R_2}{R_1 R_2} \right] + V_o \frac{1 + \beta R_E}{R_E} \left[ \frac{1}{R_B} + \frac{1}{(B+1)(1 + \beta R_E)} \right]$$

$$V_o \left[ \frac{1}{R_1} - \frac{1 + \beta R_E}{R_E} \left[ \frac{1}{R_B} + \frac{1}{(B+1)(1 + \beta R_E)} \right] \right] = -V_o \left[ \frac{R_1 + R_2}{R_1 R_2} \right]$$

$$V_o \left[ \frac{1}{R_1} - \frac{1 + \beta R_E}{R_E} \left[ \frac{1}{R_B} + \frac{1}{(B+1)(1 + \beta R_E)} \right] \right] = -V_o \left[ \frac{R_1 + R_2}{R_1 R_2} \right] \quad (1)$$

~~M~~ M

(c) (2)  $V_i = V_{in} - V_f \Rightarrow V_{in} = V_{in} - V_o \Rightarrow \frac{V_o}{A} = V_{in} - V_o$

$$V_o \left[ \frac{1}{A} + 1 \right] = V_{in} \quad \frac{V_o}{V_{in}} = \frac{A}{1 + A} \quad (5)$$

$$\frac{V_o}{V_{in}} = \frac{\frac{R_E}{1 + \beta R_E}}{1 + \left[ \frac{R_E}{1 + \beta R_E} \right] \left[ \frac{\frac{1}{R_1} - \frac{1 + \beta R_E}{R_E} \left[ \frac{1}{R_B} + \frac{1}{(B+1)(1 + \beta R_E)} \right]}{- \left[ \frac{R_1 + R_2}{R_1 R_2} \right]} \right]} \quad (3)$$

(Q9) Assume  $V_{out}$  is decreased (by decreasing  $R_L$ )

If  $R_L$  decreases  $V_{out} = V_E$  decreases

If  $V_E$  decreases  $V_{BE}$  increases as  $V_B$  is nearly kept constant due to zener diode (nearly at 12 Volts)

If  $V_{BE}$  increases more current passes from Q transistor hence  $I_C \rightarrow$  collector current,  $I_B \rightarrow$  base current and  $I_E = I_C \rightarrow$  emitter current increases

As  $I_E$  increase  $V_{out}$  increases at regulation is provided.