
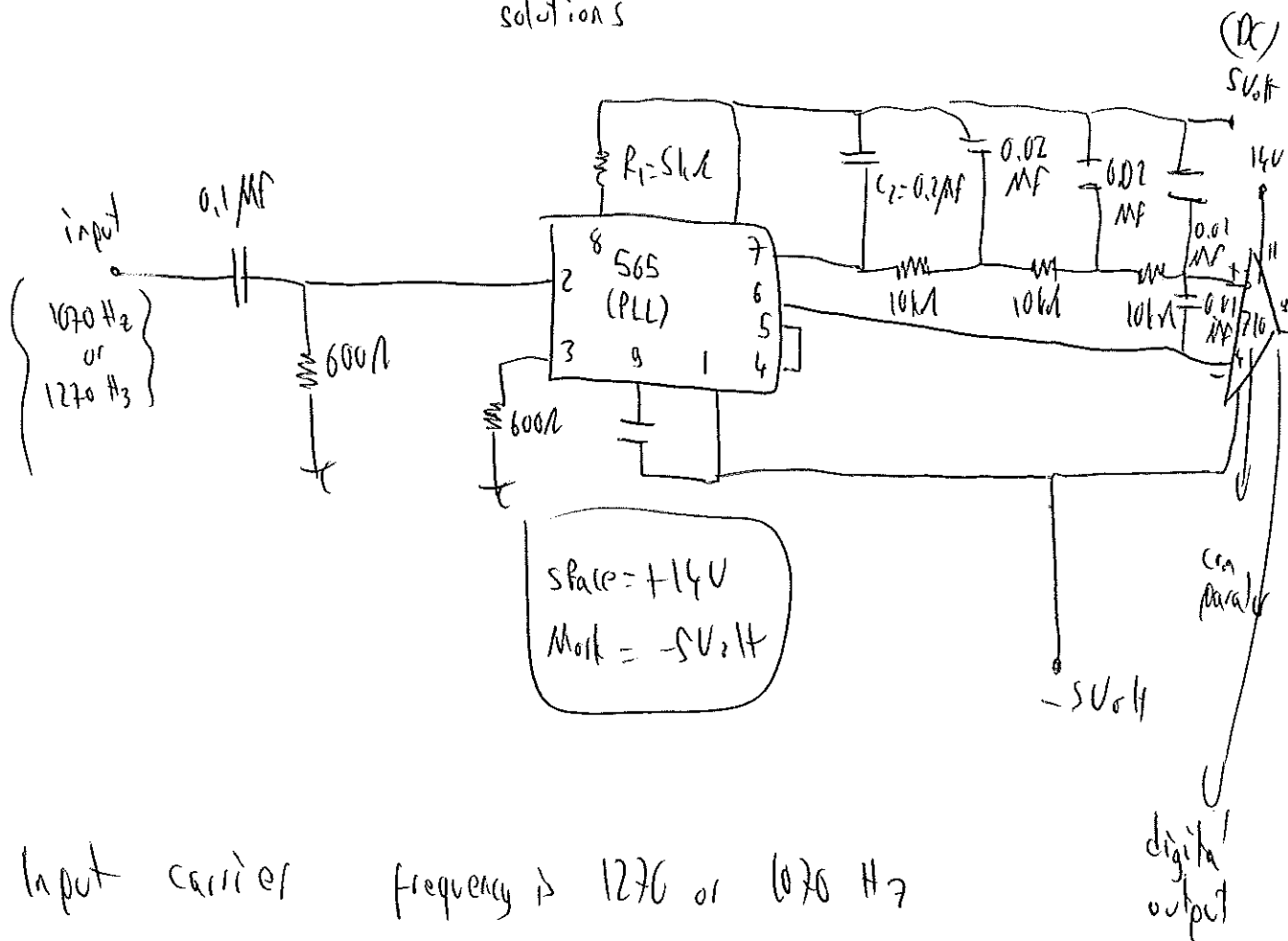


Q1

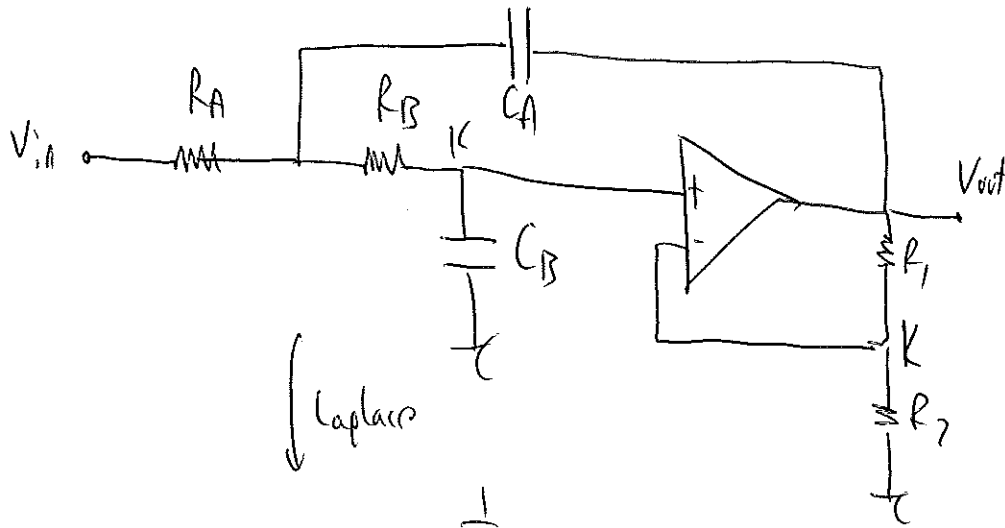


- Input carrier frequency is 1270 or 1070 Hz
- Loop locks to the input frequency and tracks it between two possible frequencies with a corresponding DC shift at the output
- RC ladder filter (three sections of  $C = 0.02 \mu F$  and  $R = 10k$ ) removes the sum-frequency component
- Free-running frequency adjusted with  $R_1$  so that the DC voltage level at pin 7 (output) of PLL S65 is the same as that of at pin 6.
- Then an input at frequency 1070 Hz will drive the divider output voltage to a more positive voltage level, driving the digital output to the high level (space or 14 Volt)
- An input at the 1270 Hz will correspondingly drive S65 DC output less positive, which the digital output drops to the low level -5 Volt

Q2 The Sallen-Key Low-Pass Filter



Laplace

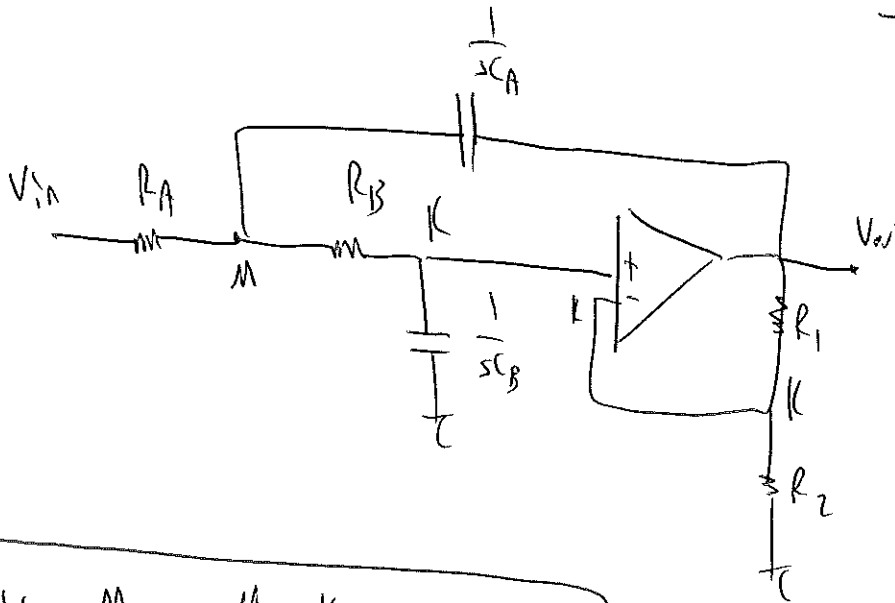

$$\frac{K}{V_{out}} = \frac{R_2}{R_1 + R_2} \Rightarrow X$$

$$K = X V_{out}$$

$$\frac{V_{in} - M}{R_A} = \frac{M - K}{R_B} + \frac{M - V_{out}}{\frac{1}{sC_A}}$$

$$\frac{M}{R_B + \frac{1}{sC_B}} = \frac{K}{\frac{1}{sC_B}}$$

$$\frac{M sC_B}{sR_B C_B + 1} = \frac{K sC_B}{1}$$

$$\frac{M}{sR_B C_B + 1} = K$$

$$\frac{V_{in}}{R_A} = M \left[ \frac{1}{R_A} + \frac{1}{R_B} + sC_A \right] - \frac{K}{R_B} - \frac{V_{out} s C_A}{1}$$

$$\frac{V_{in}}{R_A} = \left[ \frac{1}{R_A} + \frac{1}{R_B} + sC_A \right] (sR_B C_B) - \frac{K}{R_B} - \frac{V_{out} s C_A}{1}$$

$$\frac{V_{in}}{R_A} = K \left[ \frac{1}{R_A} + \frac{1}{R_B} + sC_A - \frac{1}{R_B} + s^2 C_A R_B C_B + sC_B + s \frac{R_B}{R_A} C_B \right] - \frac{V_{out} s C_A}{1}$$

$$\frac{V_{in}}{R_A} = X V_{out} \left[ \frac{1}{R_A} + s \left( C_A + C_B + \frac{R_B}{R_A} C_B \right) + s^2 C_A R_B C_B \right] - \frac{V_{out} s C_A}{1}$$

$$\frac{V_{in}}{R_A} = \left[ \frac{X}{R_A} + \left[ X \left( C_A + C_B + \frac{R_B}{R_A} C_B \right) - C_A \right] s + s^2 X C_A R_B C_B \right] V_{out}$$



$$V_{in} = \left[ X + s \left[ X \left( C_A R_A + C_B R_A + C_B R_B \right) - C_A R_A \right] + s^2 X C_A R_B C_B \right] V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{s^2 X C_A R_B C_B + s \left[ X \left( C_A R_A + C_B R_A + C_B R_B \right) - C_A R_A \right] + X}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{X C_A R_B C_B} \frac{1}{s^2 + s \left( \frac{1}{C_B R_B} + \frac{1}{C_A R_B} + \frac{1}{C_A R_A} - \frac{1}{X C_B R_B} \right) + \frac{1}{C_A C_B R_A R_B}}$$

Q3

Page 4

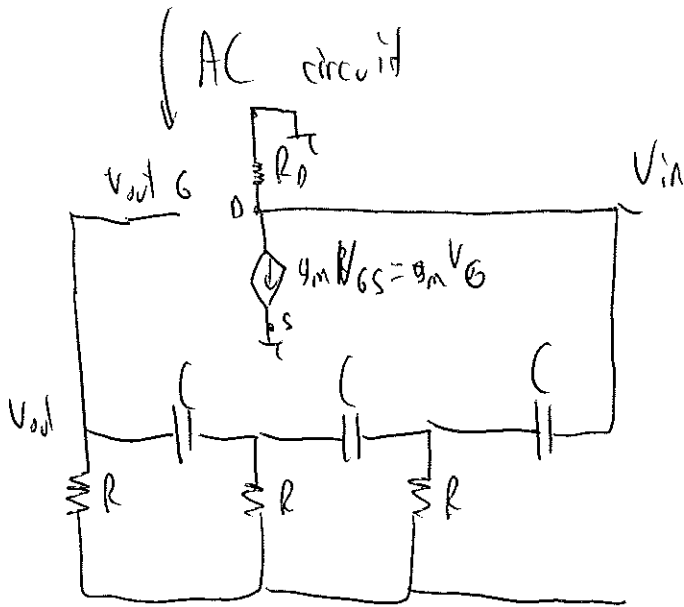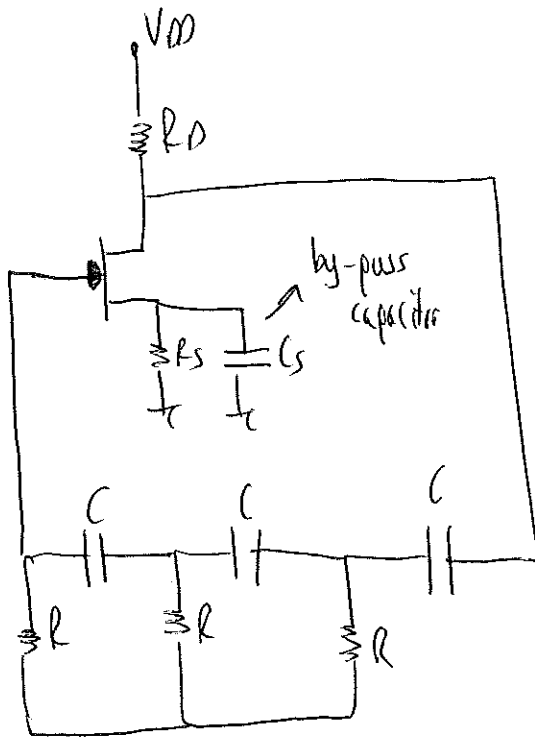

$$V_{in} = V_D$$

$$V_{out} = V_S$$

$$V_D = [-g_m V_G] R_D$$

$$V_D = -g_m R_D V_G$$

$$\downarrow$$

$$V_{in} = -g_m R_D V_{out}$$


$$V_{in} = A V_{out}$$

$$A = -g_m R_D$$


$f = \frac{1}{2\pi R C \sqrt{6}} \rightarrow$  frequency that results with undamped oscillations

Barkhausen criteria

$$\frac{V_{out}}{V_{in}} \times A = 1$$

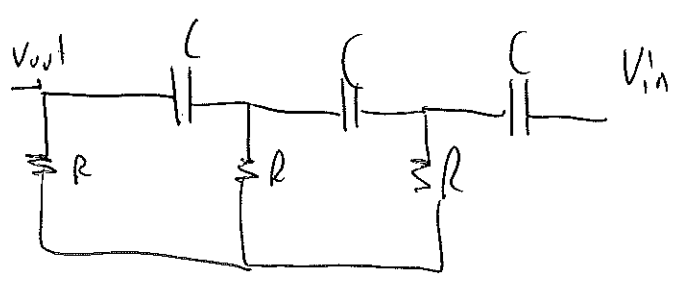

↓ Laplace

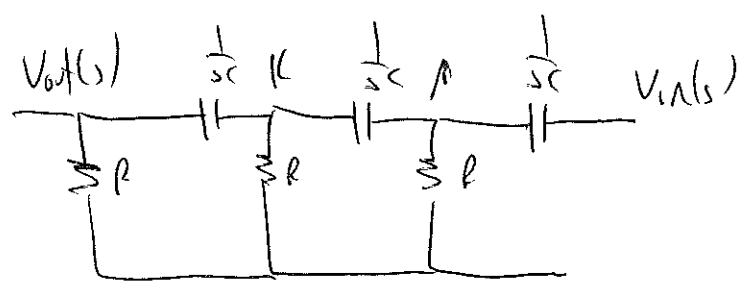

$$K = \frac{sCR + 1}{sCR} V_{out}$$

$$\frac{V_{out}}{K} = \frac{R}{R + \frac{1}{sC}}$$

$$\frac{V_{out}}{K} = \frac{sCR}{sCR + 1}$$

$$\frac{K - K}{\frac{1}{sC}} = \frac{K}{R} + \frac{K - V_{out}}{\frac{1}{sC}}$$

$$sCM = \left[ sC + \frac{1}{R} \right] K + KsC - sC V_{out}$$

$$sCM = \left[ 2sC + \frac{1}{R} \right] K + \frac{-sC V_{out}}{1}$$

$$sCM = \left[ 2sC + \frac{1}{R} \right] \frac{sCR + 1}{sC} V_{out} - sC V_{out}$$

$$s^2 C^2 M = \left[ 2s^2 C^2 R + \frac{sC}{R} \right] (sCR + 1) V_{out} - s^2 C^2 V_{out}$$

$$s^2 C^2 M = [2s^2 C^2 R + 3sCR + 1 - s^2 C^2 R] V_{out}$$

$$sCM = \left[ 2sC + \frac{1}{R} \right] \frac{sCR + 1}{sC} V_{out} - sC V_{out}$$

~~$$s^2 C^2 M = 2s^2 C^2 R$$~~

~~$$s^2 C^2 M = \left[ 2sC + \frac{1}{R} \right] [sCR + 1] V_{out} - s^2 C^2 V_{out}$$~~

~~$$s^2 C^2 M = \left[ 2sC + \frac{1}{R} \right] [sCR + 1] V_{out} - s^2 C^2 V_{out}$$~~

~~$$M = \frac{[s^2 C^2 R + 3sCR + 1]}{s^2 C^2 R} V_{out}$$~~

~~$$\frac{M}{V_{out}} = \frac{[s^2 C^2 R + 3sCR + 1]}{s^2 C^2 R}$$~~

$$\frac{V_{out}}{M} = \frac{s^2 C^2 R^2}{s^2 C R + 3 s C R + 1}$$

$$\frac{V_{in} - M}{\frac{1}{sC}} = \frac{M}{R} + \frac{M - K}{\frac{1}{sC}}$$

$$sC V_{in} - sCM = \frac{M}{R} + sCM - sCK$$

$$sC V_{in} = \left(2sC + \frac{1}{R}\right) M - sCK$$

$$sCR V_{in} = [2sCR + 1] M - sCRK$$

$$sCR V_{in} = [2sCR + 1] M - sCR \frac{[sCR + 1]}{sCR} V_{out}$$

$$s^2 C^2 R^2 V_{in} = [2sCR + 1] M - [sCR + 1] V_{out}$$

$$s^2 C^2 R^2 V_{in} = [2sCR + 1] \left[ \frac{s^2 C^2 R^2 + 3sCR + 1}{s^2 C^2 R^2} \right] V_{out} - [sCR + 1] V_{out}$$

$$s^2 C^2 R^2 V_{in} = [2sCR + 1] [s^2 C^2 R^2 + 3sCR + 1] V_{out} - s^2 C^2 R^2 [sCR + 1] V_{out}$$

$$s^2 C^2 R^2 V_{in} = [2s^3 C^3 R^3 + 7s^2 C^2 R^2 + 5sCR + 1 - s^3 C^3 R^3 - s^2 C^2 R^2] V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{s^3 C^3 R^3}{s^3 C^3 R^3 + 6s^2 C^2 R^2 + 5sCR + 1}$$

$$\left. \frac{V_{out}(s)}{V_{in}(s)} \right|_{s=j\omega} = (80^\circ) \quad (\text{for oscillation})$$

$$\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{j^3 \omega^3 C^3 R^3}{j^3 \omega^3 C^3 R^3 + 6j^2 \omega^2 C^2 R^2 + 5j\omega CR + 1}$$

$$sCM = \left[ 2sC + \frac{1}{R} \right] M + \frac{-sCV_{out}}{1} \quad (\text{Page 6})$$

$$sCRM = [2sCR + 1] M - sCRV_{out}$$

$$sCRM = [2sCR + 1] \frac{[sCR + 1]}{sCR} V_{out} - sCRV_{out}$$

$$s^2 C^2 R^2 M = [2sCR + 1] [sCR + 1] V_{out} - s^2 C^2 R^2 V_{out}$$

$$s^2 C^2 R^2 M = [s^2 C^2 R^2 + 3sCR + 1] V_{out}$$

$$M = \left[ \frac{s^2 C^2 R^2 + 3sCR + 1}{s^2 C^2 R^2} \right] V_{out}$$

only possible when

$$1 - 6\omega^2 C^2 R^2 = 0$$

$$\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{-j\omega^3 C^3 R^3}{-j\omega^3 C^3 R^3 + s_j \omega C R + (1 - 6\omega^2 C^2 R^2)}$$

if  $1 - 6\omega^2 C^2 R^2 = 0$        $\omega^2 = \frac{1}{6C^2 R^2}$        $\omega = \frac{1}{\sqrt{6} CR}$

$f = \frac{1}{2\pi CR\sqrt{6}}$

Hence if  $f = \frac{1}{2\pi CR\sqrt{6}}$  → oscillation

$$\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{-j\omega^3 C^3 R^3}{-j\omega^3 C^3 R^3 + s_j \omega C R} = \frac{-\omega^3 C^3 R^3}{-\omega^3 C^3 R^3 + s_j \omega C R}$$

$$\left| \frac{V_{out}(j\omega)}{V_{in}(j\omega)} \right| = \frac{\omega^2 C^2 R^2}{\omega^2 C^2 R^2 + 5}$$

$\omega = \frac{1}{\sqrt{6} CR}$

put  $\omega = \frac{1}{\sqrt{6} CR}$        $\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{\frac{1}{6C^2 R^2}}{\frac{1}{6C^2 R^2} - 5} = \frac{\frac{1}{6}}{\frac{1}{6} - 5} = \frac{1}{-29}$

Hence  $\left| \frac{V_{out}(j\omega)}{V_{in}(j\omega)} \right| = \frac{1}{29}$

Hence  $\left| \frac{V_{out}}{V_{in}} \right| \times A = 1$       hence  $A = 29 = | -g_m R_D |$